

FIRST SHOW "INPUT OUTPUT" SLIDES FROM DAY 1 AGAIN

- RC Circuit \rightarrow Differential Equations
- Differential Equations \rightarrow solutions
 - Euler method: simulation
 - Exact solutions
- Solutions \rightarrow INPUT-OUTPUT PROPERTIES

Response Kernel $K(t)$

Principle of superposition.

Impulse response + system characterization

- ABBOTT + DAYAN CH. 5.1-5.7
- GABBIANI + COX CH. 2-3

Equiv. circuit


model of single neuron dynamics

GABBIANI + COX FIG. 12.2

WPUT

e.g.

①

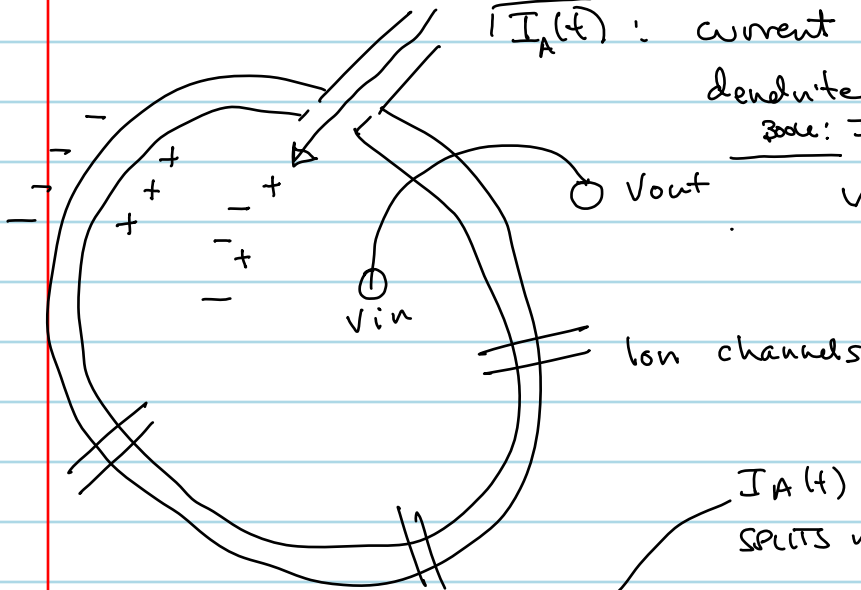

$I_A(t)$: current (net + change), from dendrite (or experimenter)
Note: $I_{stim}(t)$

$V = V_{in} - V_{out}$, voltage

②


$I_A(t)$ must go somewhere!

SPLITS into $I_c + I_1 + I_2 + \dots$

Capacitive current

ion channel currents

C

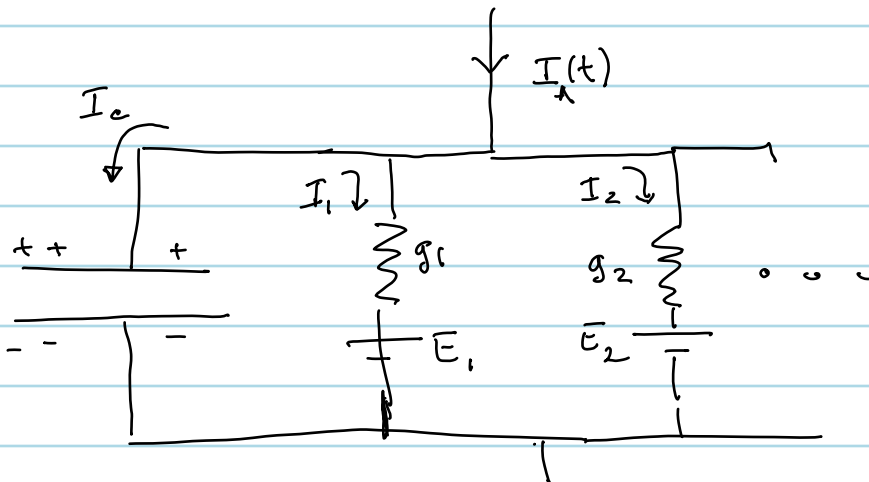

OUT

CAPACITOR:

$$Q = C V$$

$$\frac{dQ}{dt} = I_C$$

Q: Charge on "top" wall / plate
C: Capacitance


Current: Change in charge / unit time

$$\Rightarrow I_C = \frac{d}{dt}(C V) = C \frac{dV}{dt}$$

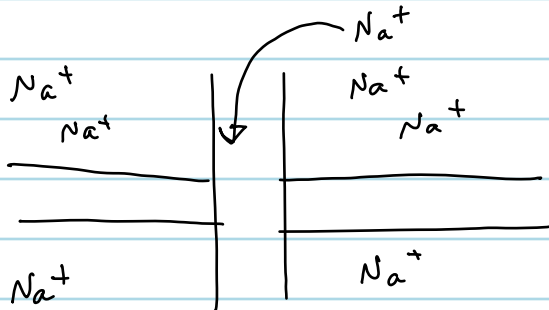(5.2, A+D)

Ohm's law

② Ion channel: $I_i = g_i (V - E_i)$. See Abb-Dayan Fig 5.1



• passes specific type or types of ions only, e.g. Na^+

• conductance $g = \frac{1}{R}$

"how open it is"

• Two "forces" drive current:

(1) Diffusion: is there more Na^+ inside or outside

(2) Voltage V , which pushes on charges

E_i is "reversal" potential where these balance.

• Repeat for other channels. Pass different ions \rightarrow different E_k

• $I_A(t) = I_C(t) + \sum_k I_k(t)$

$$I_A(t) = C \frac{dV}{dt} + \sum_k g_k (V - E_k) \quad \dots \text{so } \dots$$

(1) $C \frac{dV}{dt} = I_A(t) + \sum_k g_k (E_k - V)$

Griffiths
+ Cox (2.10)

A+Dayan (5.6)

- Passive Membrane / "RC Circuit" form of (1).

Combine all currents k that have g_k conductances that are approximately constant over time \rightarrow

"net" current

$$C \frac{dV}{dt} = I_A(t) + g_L (E_L - V) \dots$$

AND ignore other "spike generating," etc currents.

(Formally, redefine $V \rightarrow V - E_L$)

- For convenience, set $E_L = 0$.

\rightarrow RC circuit eq^s below

$$C \frac{dV}{dt} = I_A(t) - gV = I_A(t) - \frac{1}{R} V$$

$$\frac{dV}{dt} = -\frac{1}{RC} V + \frac{I_A(t)}{C}$$

- Differential equations + linear systems.

$$\frac{dy}{dt} = f(y, t)$$

[...rule / rate of change...]

$$\frac{y(t + \Delta t) - y(t)}{\Delta t} = f(y, t)$$

$$y(t + \Delta t) = y(t) + f(y, t) \cdot \Delta t \quad ; y(0) = y_0.$$

Euler method! Works for ANY fG2.
(often only option...)

• Example:

$$\frac{dv}{dt} = v \quad ; \quad v(0) = v_0 = 1.$$

$$\text{Solution: } v(t) = v_0 e^t \quad (\text{check}).$$

Euler - illustrate $v_0 = 1$

(use $\Delta t = 0.1, 0.001 + \text{zoom}$)

Accuracy?

Each timestep, make local error = $k \cdot \Delta t^2$

→ Challenge:
Use T-series
to show
this...

$$\text{Global error: } \frac{T_{\text{max}}}{\Delta t} \cdot k \Delta t^2 = k_2 \cdot \underline{\underline{\Delta t}}$$

↓
timesteps

"1st order accurate
method"

(R-K methods - like ode45 - get $k \Delta t^4$ - explain why important)

Write on Board. Students work on own.
Intermittently have students "give"
code / tell what to write..

LAB WORKSHOP EXERCISES:

(1) Let $T_{max} = 10$, find Δt that gives
Global error of
10% of True Solution
1%
0.1%.

What do you notice about how Δt varies
to achieve this?

Use code Euler-illustrate-v.m, provided.

(2) Modify your code to solve:

$$\frac{dV}{dt} = \sin(t) \quad ; \quad V(0) = 0$$

Compare numerical and exact answers.

SAVE CODE
w/ new
name!

(3) Modify your code to solve RC circuit
equation:

$$\frac{dV}{dt} = -\frac{V}{RC} + \frac{I_A(t)}{C} \quad ; \quad V(0) = 0$$

where $I_A(t) = \sin(t)$.

[Same code as euler_illustrate RC.m]

[show key euler step on board]

(OPTIONAL BONUS...)

(4) Modify again, to solve case where $I_A(t)$ is itself the solution of a differential equation:

$$\frac{dI_A}{dt} = -I_A + \sin(t) \quad ; \quad I_A(0) = 0$$

$$\frac{dV}{dt} = \frac{-V}{RC} + I_A(t) \quad ; \quad V(0) = 0$$

BONUS: Compare with analytical solution.

GAB. + CWX
SEC 3.1:

Back to our circuit ... solve for $v(t)$... ANALYTICALLY, for RC circuit example.

Goal: Insight into neural response!

Int. factor ... rewrite

$$e^{t/RC} \frac{dy}{dt} = e^{t/RC} \left(-\frac{y}{RC} \right) + e^{t/RC} \frac{I_A(t)}{C}$$

$$\frac{d}{dt} \left[y e^{t/RC} \right] = e^{t/RC} \frac{I_A(t)}{C} \quad ; \quad \int_0^t \text{ both sides}$$

$$y(t) e^{t/RC} - y(0) = \int_0^t e^{s/RC} \frac{I_A(s)}{C} ds$$

$$y(t) = y_0 e^{-t/RC} + \int_0^t \frac{e^{-(t-s)/RC}}{C} I_A(s) ds$$

$$= y_0 e^{-t/RC} + \int_0^t K(t-s) I_A(s) ds \quad ; \quad \text{let } t' = t-s$$

$$= y_0 e^{-t/RC} + \int_0^t K(t') I_A(t-t') dt'$$

Kernel: weight on inputs t' in past

$$K(t') = \frac{e^{-t'/RC}}{C}$$

RC Circuit obeys SUPERPOSITION ...
* (if $y_0 = 0$ or t is large)

$$[= K * I_A [t]]$$

That is ... input $I_A(t) = I_1(t) \rightarrow v_1(t)$
 $I_2(t) \rightarrow v_2(t)$

Then ... input $I_A = I_1(t) + I_2(t) \rightarrow V_1(t) + V_2(t)$.

• Check: plug into exact solution

• Euler-RC.m for... $I_A(t) = 1$ or $= \sin(t)$ or $= 1 + \sin(t)$ shows neur. doing $1+1=2$
[cut/paste solns in MATLAB]

Demo: euler-illustrateRC-two-inputs.m

• Generalize... if $I_A(t) = \sum_k C_k I_k(t)$ and each $I_k(t)$

gives response $V_k(t)$, then

$$I_A(t) \text{ gives } V(t) = \sum_k C_k V_k(t).$$

• CONSEQUENCES

(1) Predict response to complex stim. from simpler components

(2) SUMMATION:

Brief inputs at different times INTERACT...




! Simulate this in MATLAB!
euler-illustrateRC-two-inputs.m

(LAB ASSIGNMENT)


(Cooperate \rightarrow push over spike threshold \rightarrow exc./inh. impulses CANCEL.)

[Skip to (4), come back if time.]

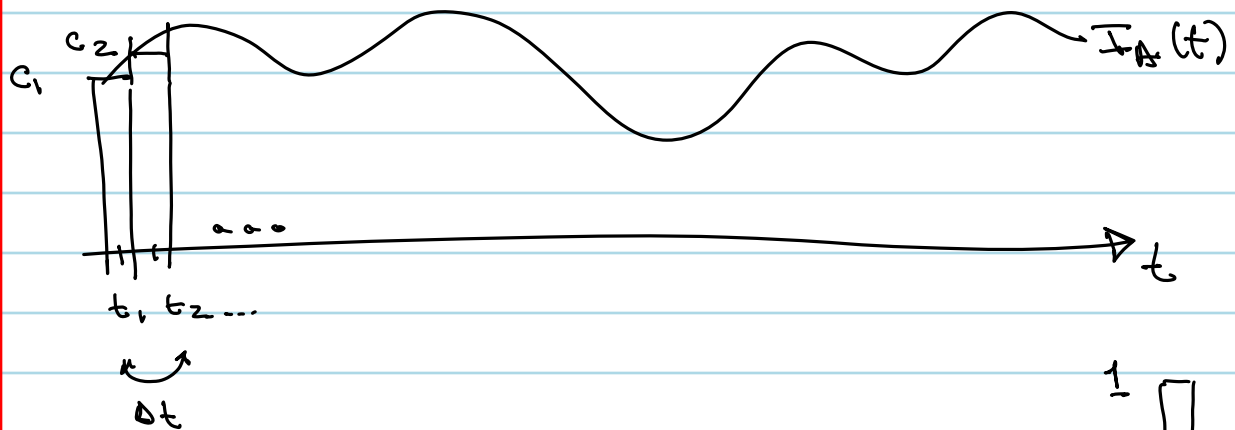
(3) This MPVCSF response provides complete description of response to Any input.



$$I_A(t) = \sum_k c_k \delta_k(t)$$

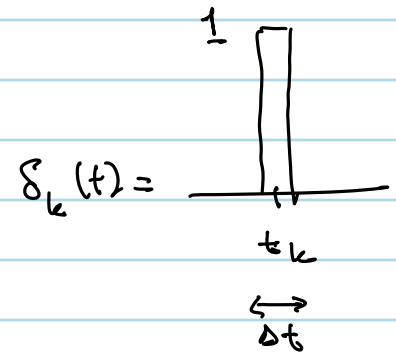

$$V(t) = \sum_k c_k v_k(t)$$

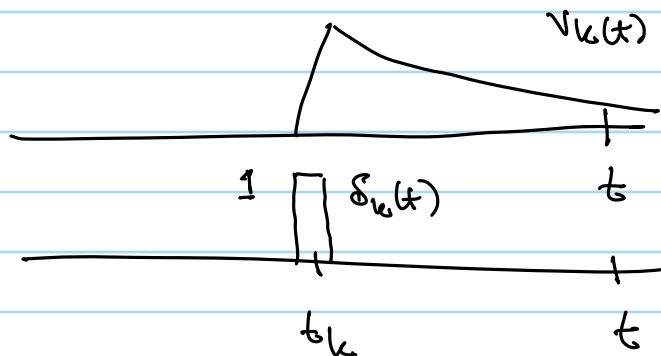

"Sum of Δt -impulses"


Relate to solution:

$$V_k(t) = \int_0^t k(t') \delta_k(t-t') dt'$$

[Think: pulse when argument
= $t_k \rightarrow t-t' = t_k$

$$t' = t - t_k$$

o.g.: $t - t_k$
into past]

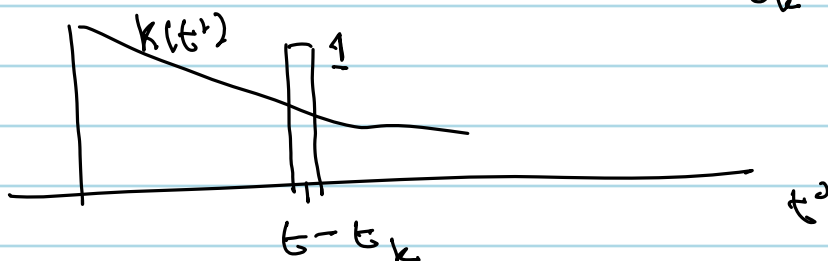

$$\approx \Delta t \cdot k(t - t_k)$$

\rightarrow impulse response related to kernel $k \dots$
but Δt in way!

• Get rid of pesky Δt : apply $\frac{1}{\Delta t} \delta_k(t')$

$$\rightarrow V_k(t) \approx k(t - t_k)$$

• What Δt should we use?

Small $\Delta t \rightarrow$ More accurate!

Definition: δ -function "at t_k ": $\delta(t' - t_k)$, is

$\frac{1}{\Delta t} \delta_k(t')$ in limit of small Δt .

Definition: Impulse response: Impulse $\delta(t)$

↖ impulse at time $t = 0$.


$y(t)$ in response to $\delta(t - 0)$

Fact: Impulse $\delta(t) = h(t)$.

- Consequence: We can discover our system response
Kernel FROM the impulse response - they
are the same.

4) The filter $K(\cdot)$ illustrates which components of the signal affect response $V(t)$... & which are ignored.

[E.g.

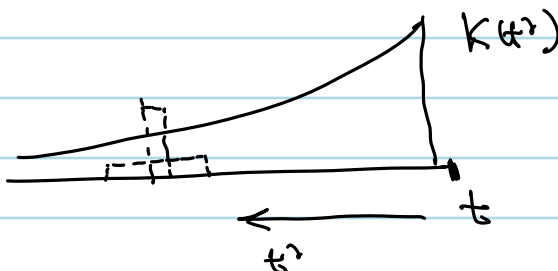

wide + short vs. tall + shury inputs give same responses...

→ Kernel NOT invertible!

... ! Add some more ...

... pos/neg cancellation example.

Hey! This is like the spike-triggered average and the optimal linear filter!

(2.7 Abbott - Dayan):

$$L(t) = \int_0^\infty d\tau D(\tau) s(t-\tau) \sim \sum_{\tau} D(\tau) s(t-\tau)$$

\downarrow \downarrow
 $K(\tau)$ $I_A(t-\tau)$

"D dot S"



Stamp filter D onto stimulus S

- If firing rate $\sim V$, then this gives firing rate in time.

- Connects Biophysics to COMPUTATION! Membrane biology shapes $K(t')$ and hence extracted stim. features.

Synaptic, or conductance-based, inputs.

CAB. +
CCK
SEC 2.5
ABB + DAYAN
5.7.

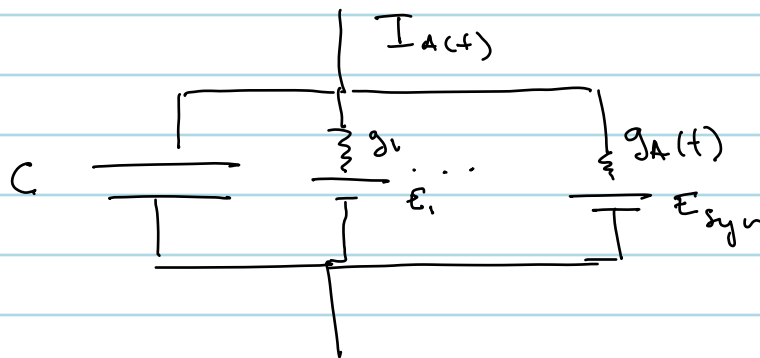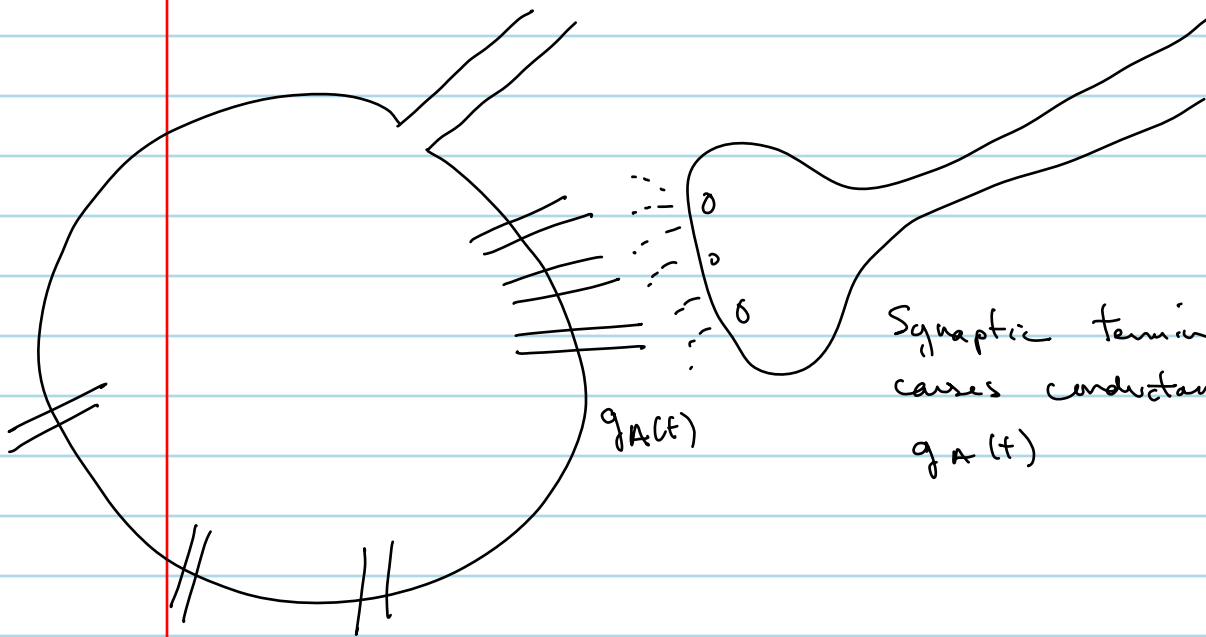

Simplest case for notation:

"RC circuit," $g_1 = \frac{1}{R}$, $E_i = 0$

$$C \frac{dV}{dt} = -\frac{V}{R} + g_A(t) [E_{syn} - V]$$

CAB. + CCK
(2.12)

Rewrite as

$$\frac{dV}{dt} = -\frac{V}{\tau} + g(t) [E - V]$$

Euler - illustrate RC - conduct. in

Conductance-Based inputs:

$$\frac{dv}{dt} = -\frac{v}{\tau} + g(t) (E - v) \quad \text{Reversal potential} \quad \times \exp\left(\int_0^t \frac{1}{\tau} + g(t') dt'\right)$$

$$\Rightarrow \frac{d}{dt} \exp(\sim) = g(t) E \cdot \exp(\sim)$$

$$v(t) \exp(\sim) - v(0) = E \int_0^t g(t') \cdot \exp \int_0^{t'} \left(\frac{1}{\tau} + g(s)\right) ds dt'$$

Assoc. $\int_0^{t'} - \int_0^t$

(*) JUST WRITE THIS!

$$V(t) = v_0 \exp - \int_0^t \left(\frac{1}{\tau} + g(s)\right) ds + E \int_0^t dt' g(t') \cdot \exp - \int_{t'}^t \left(\frac{1}{\tau} + g(s)\right) ds$$

$$\text{let } P(t) = \exp - \int_0^t \left(\frac{1}{\tau} + g(s)\right) ds$$

CHECK

Write solⁿ in easiest form: from (*)

$$V(t) = v_0 P(t) + P(t) \cdot E \int_0^t g(t') \int_0^{t'} \left(\frac{1}{\tau} + g(s)\right) ds dt'$$

$$\begin{aligned} V' = v_0 P(t) \left(-\frac{1}{\tau} - g(t)\right) + \left(-\frac{1}{\tau} - g(t)\right) P(t) \cdot E \int_0^t g(t') \int_0^{t'} \left(\frac{1}{\tau} + g(s)\right) ds dt' \\ + P(t) \cdot E \cdot g(t) \int_0^t \left(\frac{1}{\tau} + g(s)\right) ds \end{aligned}$$

// $E g(t)$

$$\Rightarrow V' = v \left(-\frac{1}{\tau} - g(t)\right) + E \cdot g(t) \quad \checkmark$$

Calculus aside:

$$\frac{d}{dt} \int_0^t f(t', t) dt' = \frac{1}{\Delta t} \left[\int_0^{t+\Delta t} f(t', t+\Delta t) dt' - \int_0^t f(t', t) dt' \right]$$

$$\approx \frac{1}{\Delta t} \left[\int_0^{t+\Delta t} \left[f(t', t) + \frac{\partial f}{\partial t} \cdot \Delta t \right] dt' - \int_0^t f \right]$$

$$\approx \int_0^t f(t', t) dt' + \int_0^t dt' \frac{\partial f}{\partial t}(t', t)$$

— — —

So...

$$\frac{d}{dt} \left[\int_0^t dt' f(t') \cdot \int_{t'}^t g(s) ds \right]$$

$$= f(t) \int_{t'}^t g(s) ds + \int_0^t dt' f(t') \cdot g(t)$$

Don't worry about specific form. Point. Say

input $g_A(t) = g_1(t) \rightarrow v_1(t)$

$$g_2(t) \rightarrow v_2(t)$$

THEN...

input $g_A(t) = g_1(t) + g_2(t)$ does NOT give $v_1(t) + v_2(t) \dots$

- Interaction among inputs
- Basic nonlinear computation. ie, one input "blocks" next, in demo.

DEMO:

Euler - illustrate RC - two-inputs - conductance. in

mm why?
 \rightarrow Nonlinear entrance of $g(t)$.

ie... take $g(t) = g_1(t) + g_2(t)$

$$\begin{aligned} \exp(g(t)) &\neq \exp(g_1(t)) + \exp(g_2(t)) \\ &= \exp(g_1(t)) \cdot \exp(g_2(t)) \end{aligned}$$