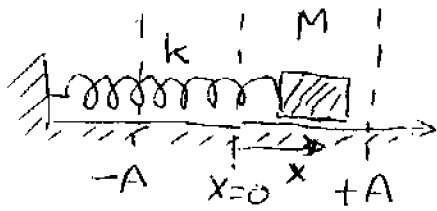


The ideal spring-mass system and the ideal capacitor-inductor circuit




Stretching spring to +A and then releasing the mass M leads to simple harmonic oscillations.

Starting from Newton's 2nd Law

$$F = ma$$

$$\boxed{-kx = ma = m \frac{\Delta v}{\Delta t}} \quad (1)$$

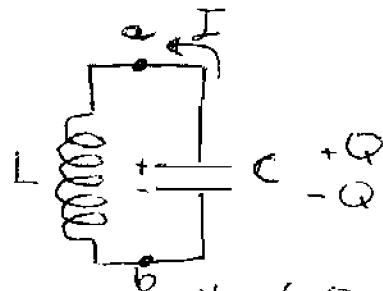with $a = \frac{\Delta v}{\Delta t}$ and $v = \frac{\Delta x}{\Delta t}$



Charging capacitor (+Q₀ and -Q₀) and then connecting to the inductor (or "coil") a current will start to flow to discharge the capacitor. A potential difference can be measured between points "a" and "b", which is the same if we travel along the circuit through L or through C. Thus one starts by

$$V_{ab}(\text{Inductor}) = V_{ab}(\text{capacitor})$$

$$-L \frac{\Delta I}{\Delta t} = \frac{Q}{C}, \text{ or}$$

writing it like (1)

$$\boxed{-\frac{Q}{C} = L \frac{\Delta I}{\Delta t}} \quad (2)$$

and $I = \frac{\Delta Q}{\Delta t}$

Equations (1) and (2), while representing different phenomena, have the same mathematical form if we use the equivalence

$$x \rightarrow Q$$

$$k \rightarrow \frac{1}{C}$$

$$M \rightarrow L$$

$$a = \frac{\Delta v}{\Delta t} \rightarrow \frac{\Delta I}{\Delta t}$$

$$v = \frac{\Delta x}{\Delta t} \rightarrow I = \frac{\Delta Q}{\Delta t}$$

It is not surprising then that both (1) and (2) lead to (2) mathematically identical solutions (let's neglect phase issues)

Spring - Mass

$$x = A \cos(\omega t)$$

$$v = -A\omega \sin(\omega t) = v_{\max} \sin \omega t$$

$$a = \frac{\Delta v}{\Delta t} = -A\omega^2 \cos(\omega t) = -v_{\max} \omega \cos(\omega t) = -a_{\max} \cos(\omega t)$$

We found out that in equation (1)

$$\frac{\Delta v}{\Delta t} = a = -\frac{k}{m} x = -\omega^2 x$$

with $\omega = \sqrt{\frac{k}{m}} = 2\pi f = \frac{2\pi}{T}$

Capacitor - Inductor

$$Q = Q_0 \cos(\omega t)$$

$$I = -Q_0 \omega \sin(\omega t) = -I_{\max} \sin \omega t$$

$$\frac{\Delta I}{\Delta t} = -Q_0 \omega^2 \cos(\omega t) = -I_{\max} \omega \cos(\omega t)$$

→ Similarly, from equation (2)

$$\frac{\Delta I}{\Delta t} = -\frac{1}{LC} Q = -\omega^2 x$$

so now $\omega = \sqrt{\frac{1}{LC}} = 2\pi f = \frac{2\pi}{T}$

A fundamental characteristic of the spring-mass system is that one can store energy in TWO places: (a) Potential Energy $\frac{1}{2} kx^2$, and (b) Kinetic Energy, $\frac{1}{2} M v^2$. The same is true for the capacitor-inductor system.

Energy can be stored in the Capacitor (electric field) and the Inductor (magnetic field)

- ⇒ Potential Energy $\frac{1}{2} kx^2$
- ⇒ Kinetic Energy $\frac{1}{2} Mv^2$

- ⇒ Energy in capacitor: $\frac{1}{2} \epsilon_0 E^2 \times \text{Volume of Capacitor}$
- ⇒ Energy in inductor: $\frac{1}{2} \frac{B^2}{\mu_0} \times \text{Volume of Inductor}$

$$\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{Coulomb}^2}{\text{Newtm}^2}$$

$$\mu_0 = 4\pi \times 10^{-7} \frac{\text{Newt s}^2}{\text{Coulomb}^2}$$

$$\sqrt{\frac{1}{\epsilon_0 \mu_0}} = 3 \times 10^8 \text{ m/s} = c$$

$u_E = \frac{1}{2} \epsilon_0 E^2$ is the energy density or energy per unit volume in any electric field.

$u_B = \frac{1}{2} \frac{B^2}{\mu_0}$ is the energy density, or energy per unit volume, in any magnetic field.

In simple harmonic oscillation, the energy goes back and forth from one pot to the other.