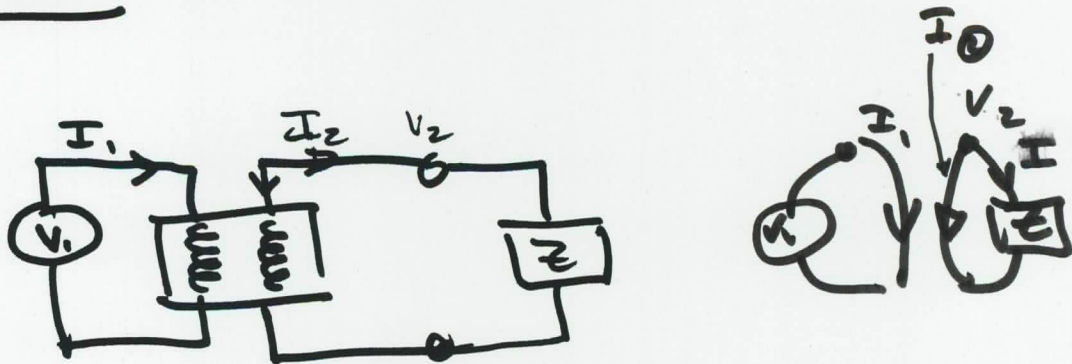


TRANSFORMERS and GYRATORS

Transformer:



What is the driving point impedance

$$Z_1 = \frac{V_1}{I_1} ?$$


Def : Transformer :
$$\begin{cases} V_1 = TF \cdot V_2 & \text{since } I_0 = -I_2 \\ I_1 = \frac{1}{TF} \cdot I_2 & \leftarrow \end{cases}$$

$$\text{so } Z_1 = \frac{V_1}{I_1} = \frac{TF \cdot V_2}{\frac{1}{TF} I_2} = (TF)^2 \frac{V_2}{I_2} = (TF)^2 \cdot Z$$


so the equivalent impedance is

$$Z_1 = (TF)^2 \cdot Z$$


so

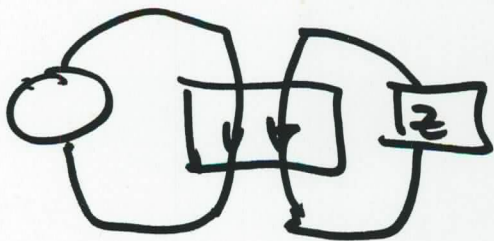

can be replaced by

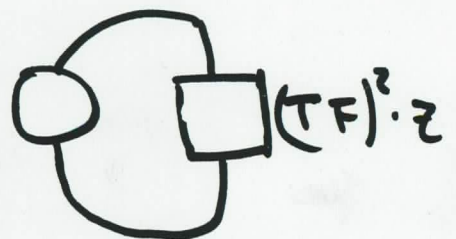


Gyrator

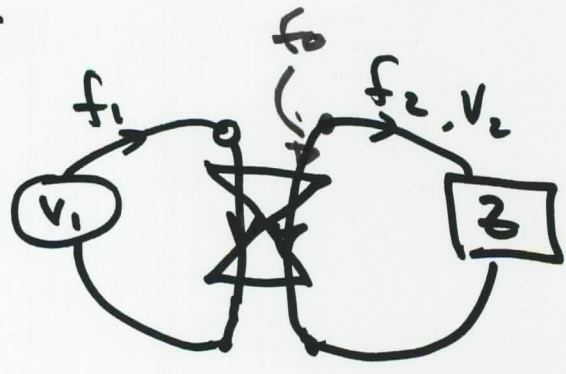

$$\begin{cases} v_1 = G_y \cdot f_2 \\ f_1 = +\frac{1}{G_y} \cdot v_2 \end{cases} \quad \text{since } f_0 = -f_2 \Rightarrow z_1 = \frac{v_1}{f_1} = (G_y)^2 \cdot \frac{1}{z_2}$$



so a gyrator can be replaced by

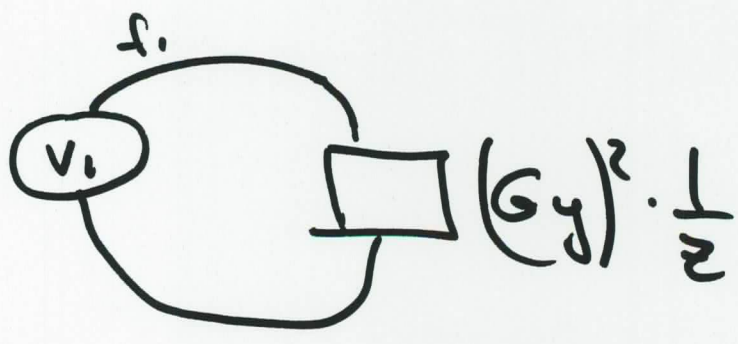


Source Representation

(3)

The Real Battery

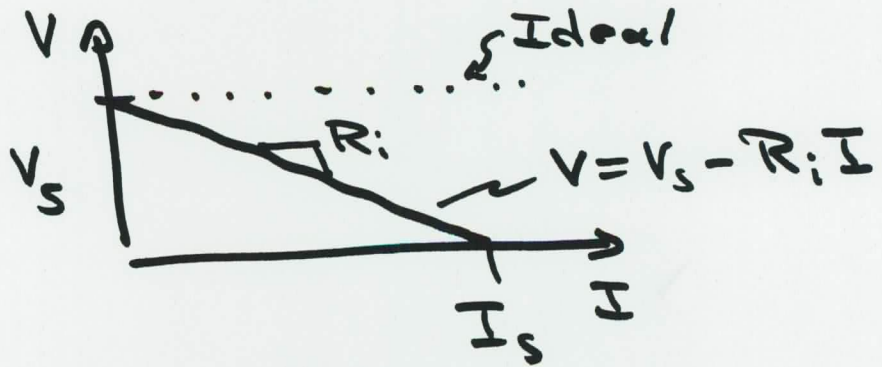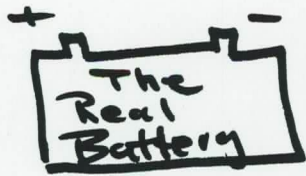


Linear Graph:

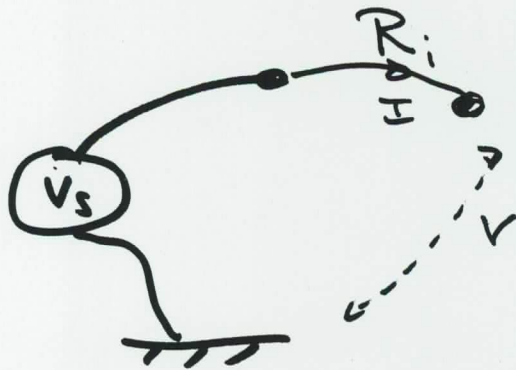

Loop $V_s = R_i I + V \Rightarrow V = V_s - I R_i$


Actual Battery Voltage.

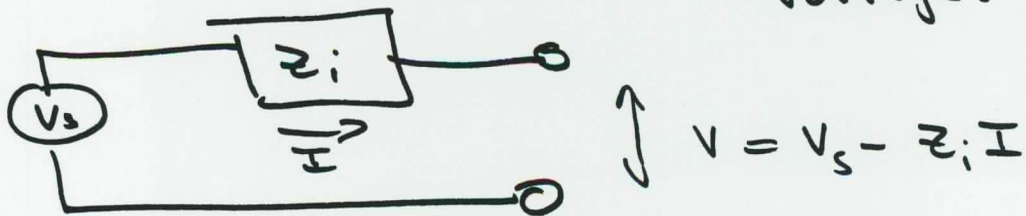

A Thevenin source representation

Electric Motor

(4)

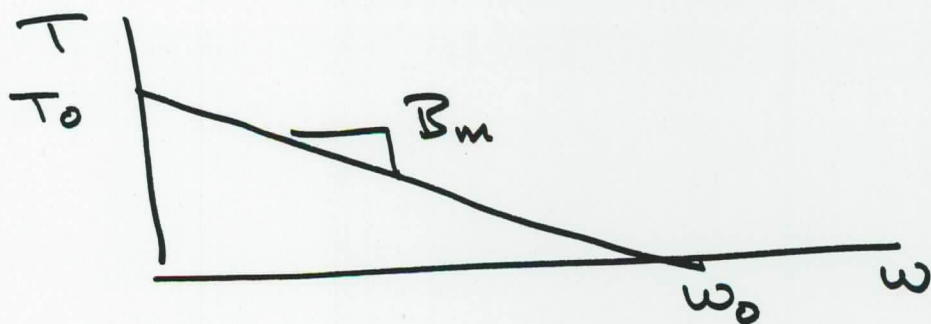


T_0 - stall torque


ω_0 - free running speed

$$T = T_0 - \left(\frac{T_0}{\omega_0}\right) \cdot \omega = T - B_m \omega$$
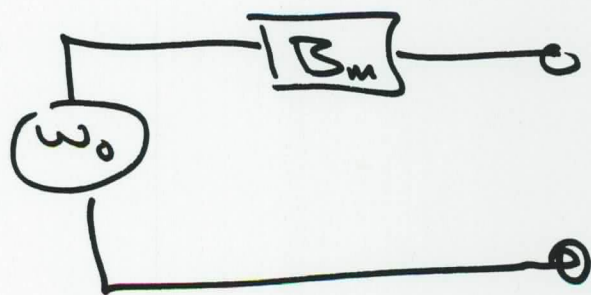
$$B_m = \text{internal damping} = \frac{T_0}{\omega_0}$$



Thevenin

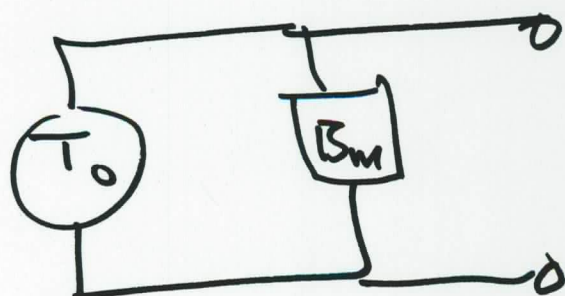

Norton