

Chapter 13

Impedance Methods

① Definition

Impedance :

$$Z(s) = \frac{\text{Across}(s)}{\text{Through}(s)} = \frac{V(s)}{I(s)} = \frac{V(s)}{F(s)}$$

$\swarrow$  Electrical       $\nearrow$  Mechanical


$$= \frac{P(s)}{Q(s)}$$

$\swarrow$  Fluid

Admittance :

$$Y(s) = \frac{1}{Z(s)} = \frac{\text{Through}(s)}{\text{Across}(s)}$$

② Impedance of Elements :

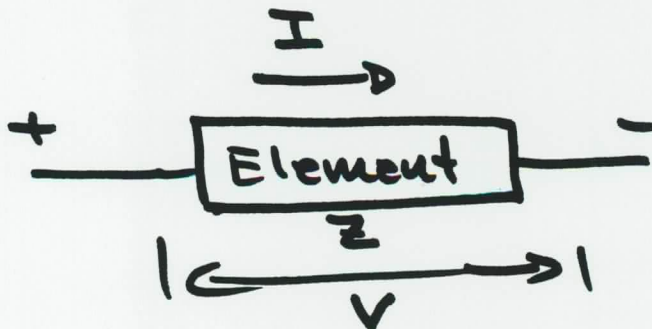

# Electrical

(2)

	Resistive Dissipative	Capacitive Across	Inductive Through
Equation	$V_R = R i_R$	$V_C = \frac{1}{C} \int i_C dt$	$V_L = L \frac{di_L}{dt}$
in s form	$V_R = R I_R$	$V_C = \frac{1}{C s} I_C$	$V_L = L s I_L$
Impedance	$Z_R = \frac{V_R}{I_R} = R$	$Z_C = \frac{V_C}{I_C} = \frac{1}{C s}$	$Z_L = \frac{V_L}{I_L} = L s$

# Mechanical

Equation	$V_B = \frac{1}{B} \cdot f_B$	$V_M = \frac{1}{M} \int F_M dt$	$V_K = \frac{1}{K} \frac{df_K}{dt}$
in s form	$V_B = \frac{1}{B} \cdot F_B$	$V_M = \frac{1}{M s} \cdot F_M$	$V_K = \frac{s}{K} F_K$
Impedance	$Z_B = \frac{V_B}{F_B} = \frac{1}{B}$	$Z_M = \frac{V_M}{F_M} = \frac{1}{M s}$	$Z_K = \frac{V_K}{F_K} = \frac{s}{K}$

# Fluid

Equation	$P_R = R_f \cdot Q_R$	$P_C = \frac{1}{C_f} \int Q_C dt$	$P_I = I_f \frac{dQ_I}{dt}$
in s form	$P_R = R_f \cdot Q_R$	$P_C = \frac{1}{C_f s} Q_C$	$P_I = I_f \cdot s Q_I$
Impedance	$Z_R = \frac{P_R}{Q_R} = R_f$	$Z_C = \frac{P_C}{Q_C} = \frac{1}{C_f s}$	$Z_I = \frac{P_I}{Q_I} = I_f \cdot s$


Summary :

Impedance

	D Type	A Type	T Type
Electrical	R	$\frac{1}{C s}$	L s
Mechanical	$\frac{1}{B}$	$\frac{1}{M \cdot s}$	$\frac{s}{K}$
Fluid	$R_f$	$\frac{1}{C_f s}$	$I_f s$

3 Simple Circuit Analysis

a) Series

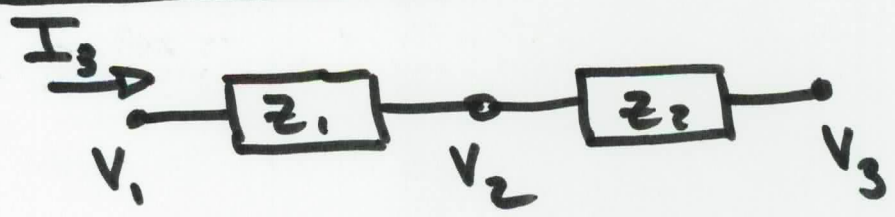

what is  $z_3$ ?

Loop:  $V_{12} + V_{23} = V_{13} (= V_1 - V_3)$

$\Rightarrow z_1 \cdot I_1 + z_2 \cdot I_2 = V_{13}$

Node:  $I_1 = I_2 = I_3$  so:

$$z_1 \cdot I_3 + z_2 \cdot I_3 = V_{13} \Rightarrow V_{13} = (z_1 + z_2) \cdot I_3$$


Want to write this as  $V_{13} = z_3 \cdot I_3$

so the total impedance is


$$\boxed{z_3 = z_1 + z_2} \leftarrow \text{for series.}$$

In general: 
$$z_T = \sum_{i=1}^n z_i$$

## b) Parallel

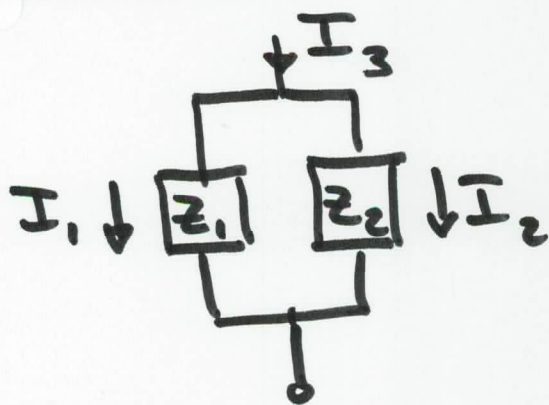

want to replace with

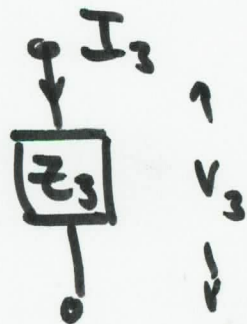

Loop: 
$$V_{z_1} = V_{z_2} = V_3$$

Node: 
$$I_1 + I_2 = I_3$$

$$\frac{V_{z_1}}{z_1} + \frac{V_{z_2}}{z_2} = I_3 \Rightarrow \left( \frac{1}{z_1} + \frac{1}{z_2} \right) V_3 = I_3$$


$$\Rightarrow z_3 = \left( \frac{1}{z_1} + \frac{1}{z_2} \right)^{-1} \Rightarrow \boxed{z_3 = \frac{z_1 \cdot z_2}{z_1 + z_2}} \leftarrow \text{parallel}$$

In general for parallel

$$\frac{1}{Z_T} = \sum_{i=1}^n \frac{1}{Z_i}$$

or  $Y_T = \sum_{i=1}^n Y_i$

c) "Voltage" Divider Rule  
(Across)

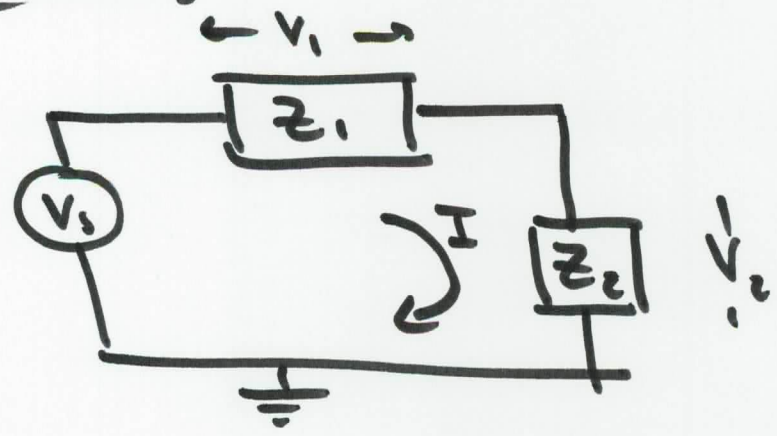

What are  $V_1$  and  $V_2$  ?

$$V_s = Z_{TOTAL} \cdot I = (Z_1 + Z_2) I$$

or 
$$I = \frac{V_s}{Z_1 + Z_2}$$

so


$$V_1 = Z_1 \cdot I = \frac{Z_1}{Z_1 + Z_2} \cdot V_s$$

and

$$V_2 = Z_2 \cdot I = \frac{Z_2}{Z_1 + Z_2} \cdot V_s$$

# d) Current Divider Rule

(6)

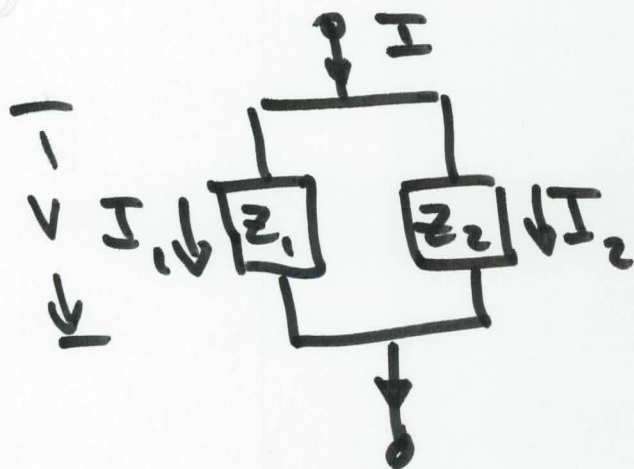

How much current (force) goes through  $z_1$  (or  $z_2$ )?

$$V_1 = V_2 = V \quad (\text{loop})$$

$$z_1 \cdot I_1 = z_2 \cdot I_2$$

← from node equ.

$$z_1 \cdot I_1 = z_2 (I - I_1)$$

$$(z_1 + z_2) \cdot I_1 = z_2 \cdot I$$

$$I_1 = \frac{z_2}{z_1 + z_2}$$

also:

$$I_2 = \frac{z_1}{z_1 + z_2}$$