
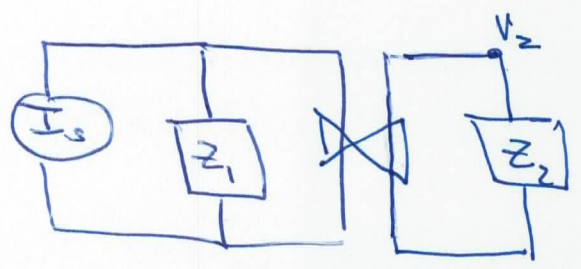


13-20

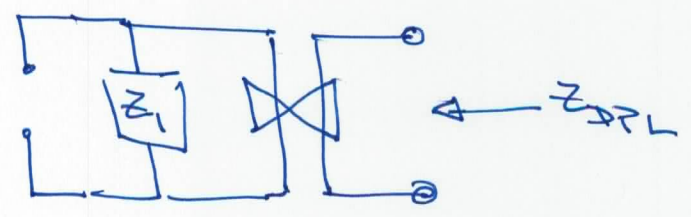


Let's use a Norton Equiv Circuit :

$Z_{DPL}$  :



$$Z_{DPL} = G^2 \frac{1}{Z_1}$$

$I_{sc}$  :

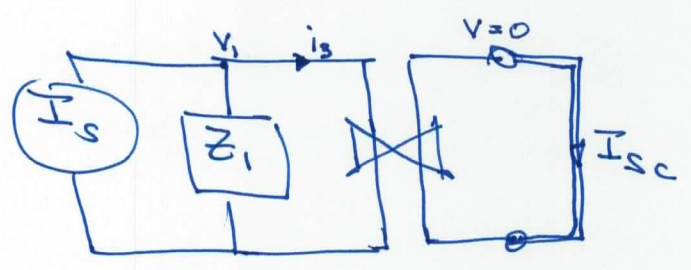


From gyrator eqn :  $i_3 = 0$  (since  $V=0$ )  
 so all current goes through  $Z_1$ , hence :

$$V_1 = Z_1 \cdot I_s$$

~~the~~ since  $V_1 = G \cdot I_{sc}$  we get  $I_{sc} = \frac{Z_1 \cdot I_s}{G}$

So we have: (Norton eq circ)

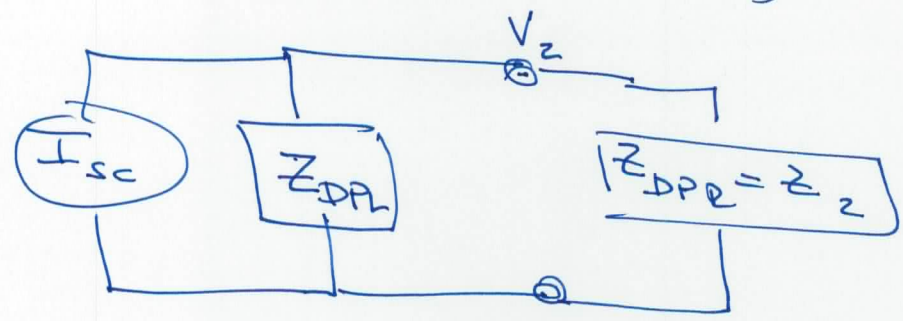


$$V_2 = Z_{DPL} \parallel Z_{DPR} \cdot I_{sc}$$

$$= \frac{Z_{DPL} \cdot Z_{DPR}}{Z_{DPL} + Z_{DPR}} \cdot \left( \frac{Z_1 \cdot I_s}{G} \right)$$

but:

$$z_1 = \frac{z_{R_1} \cdot z_{C_1}}{z_{R_1} + z_{C_1}}$$
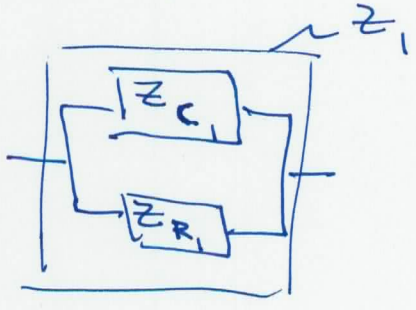
$$= \frac{R_1 \cdot \frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} =$$



$$z_1 = \frac{R_1}{R_1 C_1 s + 1}$$

and  $z_2 = \frac{R_2}{R_2 C_2 s + 1}$

so

$$Z_{DPL} = G^2 \cdot \frac{R_1 C_1 s + 1}{R_1}$$

$$Z_{DPR} = z_2 = \frac{R_2}{R_2 C_2 s + 1}$$

$$\Rightarrow V_2 = \frac{G^2 \cdot \left( \frac{R_1 C_1 s + 1}{R_1} \right) \cdot \frac{R_2}{R_2 C_2 s + 1}}{\left( \frac{R_2}{R_2 C_2 s + 1} \right) + G^2 \left( \frac{R_1 C_1 s + 1}{R_1} \right)} \cdot \frac{R_1}{(R_1 C_1 s + 1) G} I_s$$

$$V_2 = \frac{G \frac{R_2}{R_2 C_2 s + 1} \cdot R_1}{R_2 R_1 + G^2 (R_1 C_1 s + 1)(R_2 C_2 s + 1)} H_s \quad (5)$$

$$= \frac{G R_2 R_1}{R_2 R_1 + G^2 R_1 R_2 C_1 C_2 s^2 + G^2 (R_1 C_1 + R_2 C_2) s + G^2} H_s$$

$\Rightarrow$

$$\frac{V_2}{H_s} = \frac{\frac{1}{C_1 C_2 G}}{s^2 + \left( \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \right) s + \frac{1}{C_1 C_2 G^2} + \frac{1}{R_1 R_2 C_1 C_2}}$$