

BEE 332 Final project demonstration

1. Introduce your design
2. Explain your design (with circuit scheme in hand)
3. Demonstrate your design with 0.5 VAC sinusoidal signal first, then switch to music player

Name					
specifications	Input 0.5 VAC				
Output power					
Load					
Idling power					
Distortion					
Design					
Justification					
Result	With music				
distortion					
bandwidth					
Maximum power					