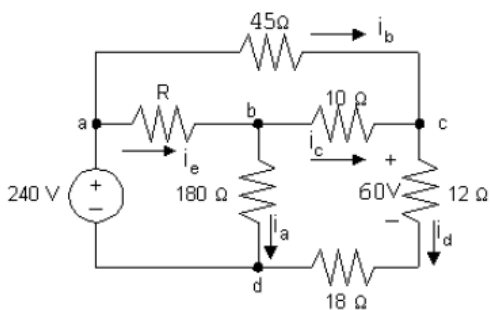


P 2.24



$$\begin{aligned}
 i_d &= 60/12 = 5 \text{ A}; \quad \text{therefore, } v_{cd} = 60 + 18(5) = 150 \text{ V} \\
 -240 + v_{ac} + v_{cd} &= 0; \quad \text{therefore, } v_{ac} = 240 - 150 = 90 \text{ V} \\
 i_b &= v_{ac}/45 = 90/45 = 2 \text{ A}; \quad \text{therefore, } i_c = i_d - i_b = 5 - 2 = 3 \text{ A} \\
 v_{bd} &= 10i_c + v_{cd} = 10(3) + 150 = 180 \text{ V}; \\
 \text{therefore, } i_a &= v_{bd}/180 = 180/180 = 1 \text{ A} \\
 i_e &= i_a + i_c = 1 + 3 = 4 \text{ A} \\
 -240 + v_{ab} + v_{bd} &= 0 \quad \text{therefore, } v_{ab} = 240 - 180 = 60 \text{ V} \\
 R &= v_{ab}/i_e = 60/4 = 15 \Omega
 \end{aligned}$$


$$\text{CHECK: } i_g = i_b + i_e = 2 + 4 = 6 \text{ A}$$

$$p_{\text{dev}} = (240)(6) = 1440 \text{ W}$$

$$\begin{aligned}
 \sum P_{\text{dis}} &= 1^2(180) + 4^2(15) + 3^2(10) + 5^2(12) + 5^2(18) + 2^2(45) \\
 &= 1440 \text{ W (CHECKS)}
 \end{aligned}$$

P 2.27 [a] $i_o = 0$ because no current can exist in a single conductor connecting two parts of a circuit.

[b]

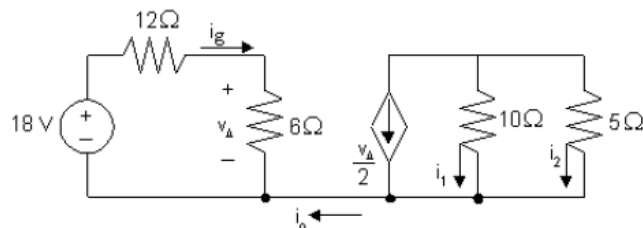

$$18 = (12 + 6)i_g \quad i_g = 1 \text{ A}$$

$$v_{\Delta} = 6i_g = 6\text{V} \quad v_{\Delta}/2 = 3 \text{ A}$$

$$10i_1 = 5i_2, \text{ so } i_1 + 2i_1 = -3 \text{ A; therefore, } i_1 = -1 \text{ A}$$

$$[c] \quad i_2 = 2i_1 = -2 \text{ A.}$$

P 3.5 [a] $R_{ab} = 10 + (5 \parallel 20) + 6 = 10 + 4 + 6 = 20 \Omega$

[b] $R_{ab} = 30 \text{ k} \parallel 60 \text{ k} \parallel [20 \text{ k} + (200 \text{ k} \parallel 50 \text{ k})] = 30 \text{ k} \parallel 60 \text{ k} \parallel (20 \text{ k} + 40 \text{ k})$
 $= 30 \text{ k} \parallel 60 \text{ k} \parallel 60 \text{ k} = 15 \text{ k}\Omega$

P 3.13 [a] $R_{eq} = R \parallel R = \frac{R^2}{2R} = \frac{R}{2}$

[b] $R_{eq} = R \parallel R \parallel R \parallel \cdots \parallel R \quad (n \text{ } R\text{'s})$
 $= R \parallel \frac{R}{n-1}$
 $= \frac{R^2/(n-1)}{R + R/(n-1)} = \frac{R^2}{nR} = \frac{R}{n}$

[c] $\frac{R}{2} = 5000 \quad \text{so} \quad R = 10 \text{ k}\Omega$
This is a resistor from Appendix H.

[d] $\frac{R}{n} = 4000 \quad \text{so} \quad R = 4000n$
If $n = 3 \quad r = 4000(3) = 12 \text{ k}\Omega$
This is a resistor from Appendix H. So put three 12k resistors in parallel to get 4k Ω .

P 3.20 $\frac{(24)^2}{R_1 + R_2 + R_3} = 80, \quad \text{Therefore, } R_1 + R_2 + R_3 = 7.2 \Omega$

$$\frac{(R_1 + R_2)24}{(R_1 + R_2 + R_3)} = 12$$

Therefore, $2(R_1 + R_2) = R_1 + R_2 + R_3$

Thus, $R_1 + R_2 = R_3; \quad 2R_3 = 7.2; \quad R_3 = 3.6 \Omega$

$$\frac{R_2(24)}{R_1 + R_2 + R_3} = 5$$

$$4.8R_2 = R_1 + R_2 + 3.6 = 7.2$$

Thus, $R_2 = 1.5 \Omega; \quad R_1 = 7.2 - R_2 - R_3 = 2.1 \Omega$

$$\text{P 3.28} \quad 5\,\Omega \parallel 20\,\Omega = 4\,\Omega; \quad 4\,\Omega + 6\,\Omega = 10\,\Omega; \quad 10 \parallel (15 + 12 + 13) = 8\,\Omega;$$

$$\text{Therefore, } i_g = \frac{125}{2 + 8} = 12.5 \text{ A}$$

$$i_{6\Omega} = \frac{8}{6 + 4}(12.5) = 10 \text{ A}; \quad i_o = \frac{5 \parallel 20}{20}(10) = 2 \text{ A}$$

$$\text{P 3.30} \quad [\text{a}] \quad \text{The voltage across the } 9\,\Omega \text{ resistor is } 1(12 + 6) = 18 \text{ V.}$$

The current in the $9\,\Omega$ resistor is $18/9 = 2 \text{ A}$. The current in the $2\,\Omega$ resistor is $1 + 2 = 3 \text{ A}$. Therefore, the voltage across the $24\,\Omega$ resistor is $(2)(3) + 18 = 24 \text{ V}$.

The current in the $24\,\Omega$ resistor is 1 A . The current in the $3\,\Omega$ resistor is $1 + 2 + 1 = 4 \text{ A}$. Therefore, the voltage across the $72\,\Omega$ resistor is $24 + 3(4) = 36 \text{ V}$.

The current in the $72\,\Omega$ resistor is $36/72 = 0.5 \text{ A}$.

The $20\,\Omega \parallel 5\,\Omega$ resistors are equivalent to a $4\,\Omega$ resistor. The current in this equivalent resistor is $0.5 + 1 + 3 = 4.5 \text{ A}$. Therefore the voltage across the $108\,\Omega$ resistor is $36 + 4.5(4) = 54 \text{ V}$.

The current in the $108\,\Omega$ resistor is $54/108 = 0.5 \text{ A}$. The current in the $1.2\,\Omega$ resistor is $4.5 + 0.5 = 5 \text{ A}$. Therefore,

$$v_g = (1.2)(5) + 54 = 60 \text{ V}$$

$$[\text{b}] \quad \text{The current in the } 20\,\Omega \text{ resistor is}$$

$$i_{20} = \frac{(4.5)(4)}{20} = \frac{18}{20} = 0.9 \text{ A}$$

Thus, the power dissipated by the $20\,\Omega$ resistor is

$$p_{20} = (0.9)^2(20) = 16.2 \text{ W}$$

$$\text{P 3.43} \quad [\text{a}] \quad v_{\text{meter}} = 180 \text{ V}$$

$$[\text{b}] \quad R_{\text{meter}} = (100)(200) = 20 \text{ k}\Omega$$

$$20 \parallel 70 = 15.555556 \text{ k}\Omega$$

$$v_{\text{meter}} = \frac{180}{35.555556} \times 15.555556 = 78.75 \text{ V}$$

$$[\text{c}] \quad 20 \parallel 20 = 10 \text{ k}\Omega$$

$$v_{\text{meter}} = \frac{180}{80}(10) = 22.5 \text{ V}$$

[d] $v_{\text{meter a}} = 180 \text{ V}$

$$v_{\text{meter b}} + v_{\text{meter c}} = 101.26 \text{ V}$$

No, because of the loading effect.

P 3.45 [a] $R_1 = (100/2)10^3 = 50 \text{ k}\Omega$

$$R_2 = (10/2)10^3 = 5 \text{ k}\Omega$$

$$R_3 = (1/2)10^3 = 500 \Omega$$

[b] Let i_a = actual current in the movement

i_d = design current in the movement

$$\text{Then \% error} = \left(\frac{i_a}{i_d} - 1 \right) 100$$

For the 100 V scale:

$$i_a = \frac{100}{50,000 + 25} = \frac{100}{50,025}, \quad i_d = \frac{100}{50,000}$$

$$\frac{i_a}{i_d} = \frac{50,000}{50,025} = 0.9995 \quad \% \text{ error} = (0.9995 - 1)100 = -0.05\%$$

For the 10 V scale:

$$\frac{i_a}{i_d} = \frac{5000}{5025} = 0.995 \quad \% \text{ error} = (0.995 - 1.0)100 = -0.4975\%$$

For the 1 V scale:

$$\frac{i_a}{i_d} = \frac{500}{525} = 0.9524 \quad \% \text{ error} = (0.9524 - 1.0)100 = -4.76\%$$