

P 5.12 [a] This circuit is an example of an inverting summing amplifier.

$$[b] \quad v_o = -\frac{220}{44}v_a - \frac{220}{27.5}v_b - \frac{220}{80}v_c = -5 - 12 + 11 = -6 \text{ V}$$

$$[c] \quad v_o = -6 - 8v_b = \pm 10$$

$$\therefore v_b = -0.5 \text{ V} \quad \text{when} \quad v_o = 10 \text{ V};$$

$$v_b = 2 \text{ V} \quad \text{when} \quad v_o = -10 \text{ V}$$

$$\therefore -0.5 \text{ V} \leq v_b \leq 2 \text{ V}$$

$$P \ 5.18 \quad [a] \quad v_p = v_n = \frac{68}{80}v_g = 0.85v_g$$

$$\therefore \frac{0.85v_g}{30,000} + \frac{0.85v_g - v_o}{63,000} = 0;$$

$$\therefore v_o = 2.635v_g = 2.635(4), \quad v_o = 10.54 \text{ V}$$

$$[b] \quad v_o = 2.635v_g = \pm 12$$

$$v_g = \pm 4.55 \text{ V}, \quad -4.55 \leq v_g \leq 4.55 \text{ V}$$

$$[c] \quad \frac{0.85v_g}{30,000} + \frac{0.85v_g - v_o}{R_f} = 0$$

$$\left( \frac{0.85R_f}{30,000} + 0.85 \right) v_g = v_o = \pm 12$$

$$\therefore 1.7R_f + 51 = \pm 360; \quad 1.7R_f = 360 - 51; \quad R_f = 181.76 \text{ k}\Omega$$

P 5.26 Use voltage division to find  $v_p$ :

$$v_p = \frac{2000}{2000 + 8000}(5) = 1 \text{ V}$$

Write a KCL equation at  $v_n$  and solve it for  $v_o$ :

$$\frac{v_n - v_a}{5000} + \frac{v_n - v_o}{R_f} = 0 \quad \text{so} \quad \left( \frac{R_f}{5000} + 1 \right) v_n - \frac{R_f}{5000} v_a = v_o$$

Since the op amp is ideal,  $v_n = v_p = 1\text{V}$ , so

$$v_o = \left( \frac{R_f}{5000} + 1 \right) - \frac{R_f}{5000} v_a$$

To satisfy the equation,

$$\left( \frac{R_f}{5000} + 1 \right) = 5 \quad \text{and} \quad \frac{R_f}{5000} = 4$$

Thus,  $R_f = 20\text{ k}\Omega$ .

P 5.31  $v_p = \frac{1500}{9000}(-18) = -3\text{ V} = v_n$

$$\frac{-3 + 18}{1600} + \frac{-3 - v_o}{R_f} = 0$$

$$\therefore v_o = 0.009375 R_f - 3$$

$$v_o = 9\text{ V}; \quad R_f = 1280\text{ }\Omega$$

$$v_o = -9\text{ V}; \quad R_f = -640\text{ }\Omega$$

$$\text{But } R_f \geq 0, \quad \therefore R_f = 1.28\text{ k}\Omega$$

P 6.1  $0 \leq t \leq 2\text{ s} :$

$$i_L = \frac{10^3}{2.5} \int_0^t 3 \times 10^{-3} e^{-4x} dx + 1 = 1.2 \frac{e^{-4x}}{-4} \bigg|_0^t + 1$$


$$= -0.3e^{-4t} + 1.3\text{ A}, \quad 0 \leq t \leq 2\text{ s}$$

$$i_L(2) = -0.3e^{-8} + 1.3 = 1.3\text{ A}$$

$t \geq 2 \text{ s} :$

$$i_L = \frac{10^3}{2.5} \int_2^t -3 \times 10^{-3} e^{-4(x-2)} dx + 1.3 = -1.2 \frac{e^{-4(x-2)}}{-4} \Big|_2^t + 1.3$$
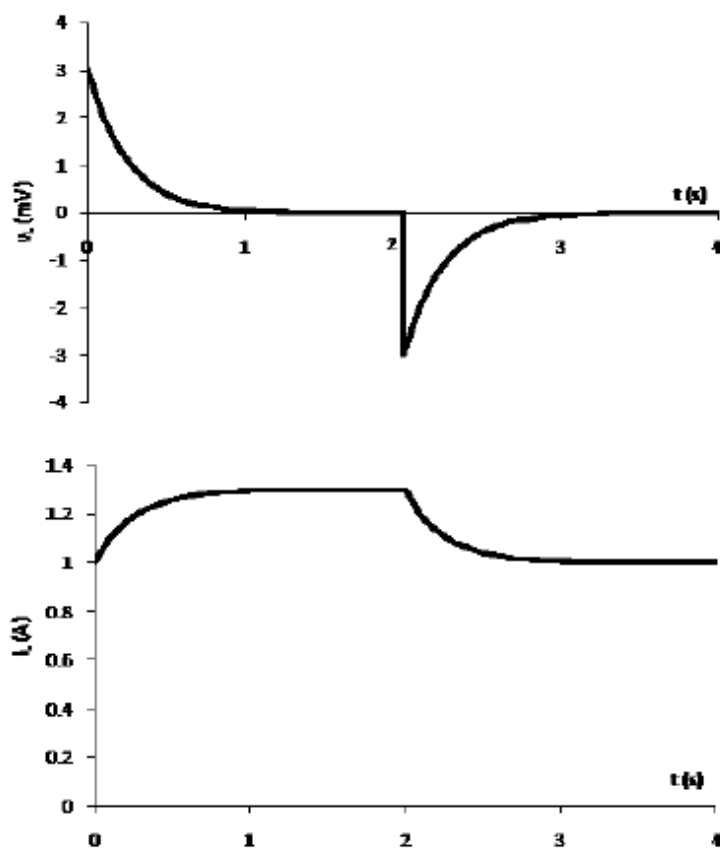
$$= 0.3e^{-4(t-2)} + 1 \text{ A}, \quad t \geq 2 \text{ s}$$



P 6.6 [a]  $i(0) = A_1 + A_2 = 0.04$

$$\frac{di}{dt} = -10,000A_1e^{-10,000t} - 40,000A_2e^{-40,000t}$$

$$v = -200A_1e^{-10,000t} - 800A_2e^{-40,000t} \text{ V}$$

$$v(0) = -200A_1 - 800A_2 = 28$$

Solving,  $A_1 = 0.1$  and  $A_2 = -0.06$

Thus,

$$i_1 = (100e^{-10,000t} - 60e^{-40,000t}) \text{ mA} \quad t \geq 0$$

$$v = -20e^{-10,000t} + 48e^{-40,000t} \text{ V}, \quad t \geq 0$$

$$[\text{b}] \quad i = 0 \quad \text{when} \quad 100e^{-10,000t} = 60e^{-40,000t}$$

Therefore

$$e^{30,000t} = 0.6 \quad \text{so} \quad t = -17.03 \mu\text{s} \quad \text{which is not possible!}$$

$$v = 0 \quad \text{when} \quad 20e^{-10,000t} = 48e^{-40,000t}$$

Therefore

$$e^{30,000t} = 2.4 \quad \text{so} \quad t = 29.18 \mu\text{s}$$

Thus the power is zero at  $t = 29.18 \mu\text{s}$ .

$$\text{P 6.21} \quad 5 \parallel (12 + 8) = 4 \text{ H}$$


$$4 \parallel 4 = 2 \text{ H}$$

$$15 \parallel (8 + 2) = 6 \text{ H}$$

$$3 \parallel 6 = 2 \text{ H}$$

$$6 + 2 = 8 \text{ H}$$

P 6.25 [a]

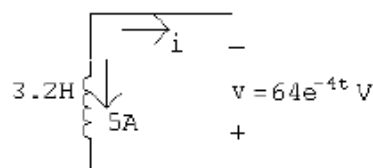

$$3.2 \frac{di}{dt} = 64e^{-4t} \quad \text{so} \quad \frac{di}{dt} = 20e^{-4t}$$

$$i(t) = 20 \int_0^t e^{-4x} dx - 5$$

$$= 20 \left. \frac{e^{-4x}}{-4} \right|_0^t - 5$$

$$i(t) = -5e^{-4t} \text{ A}$$

[b]  $4 \frac{di_1}{dt} = 64e^{-4t}$

$$i_1(t) = 16 \int_0^t e^{-4x} dx - 10$$

$$= 16 \left. \frac{e^{-4x}}{-4} \right|_0^t - 10$$

$$i_1(t) = -4e^{-4t} - 6 \text{ A}$$

[c]  $16 \frac{di_2}{dt} = 64e^{-4t} \quad \text{so} \quad \frac{di_2}{dt} = 4e^{-4t}$

$$i_2(t) = 4 \int_0^t e^{-4x} dx + 5$$

$$= 4 \left. \frac{e^{-4x}}{-4} \right|_0^t + 5$$

$$i_2(t) = -e^{-4t} + 6 \text{ A}$$

[d]  $p = -vi = (-64e^{-4t})(-5e^{-4t}) = 320e^{-8t} \text{ W}$

$$w = \int_0^\infty p dt = \int_0^\infty 320e^{-8t} dt$$

$$= 320 \left. \frac{e^{-8t}}{-8} \right|_0^\infty$$

$$= 40 \text{ J}$$


[e]  $w = \frac{1}{2}(4)(-10)^2 + \frac{1}{2}(16)(5)^2 = 400 \text{ J}$

[f]  $w_{\text{trapped}} = w_{\text{initial}} - w_{\text{delivered}} = 400 - 40 = 360 \text{ J}$

$$[\text{g}] \quad w_{\text{trapped}} = \frac{1}{2}(4)(-6)^2 + \frac{1}{2}(16)(6)^2 = 360 \text{ J} \quad \text{checks}$$


$$\text{P 6.26} \quad \frac{1}{C_1} = \frac{1}{48} + \frac{1}{16} = \frac{1}{12}; \quad C_1 = 12 \mu\text{F}$$

$$C_2 = 3 + 12 = 15 \mu\text{F}$$

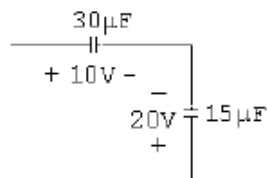


$$\frac{1}{C_3} = \frac{1}{30} + \frac{1}{15} = \frac{1}{10}; \quad C_3 = 10 \mu\text{F}$$

$$C_4 = 10 + 10 = 20 \mu\text{F}$$

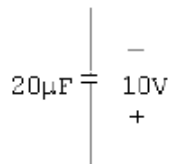
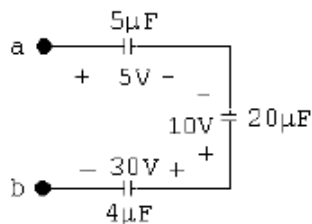
$$\frac{1}{C_5} = \frac{1}{5} + \frac{1}{20} + \frac{1}{4} = \frac{1}{2}; \quad C_5 = 2 \mu\text{F}$$




Equivalent capacitance is  $2 \mu\text{F}$  with an initial voltage drop of  $+25 \text{ V}$ .

$$\text{P 6.29} \quad \frac{1}{C_e} = \frac{1}{1} + \frac{1}{5} + \frac{1}{1.25} = \frac{10}{5} = 2$$

$$\therefore C_2 = 0.5 \mu\text{F}$$

$$v_b = 20 - 250 + 30 = -200 \text{ V}$$

[a]

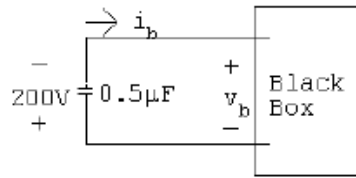

$$\begin{aligned}
 v_b &= -\frac{10^6}{0.5} \int_0^t -5 \times 10^{-3} e^{-50x} dx - 200 \\
 &= 10,000 \frac{e^{-50x}}{-50} \Big|_0^t - 200 \\
 &= -200e^{-50t} \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[b]} \quad v_a &= \frac{10^6}{5} \left[ \int_0^t -5 \times 10^{-3} e^{-50x} dx - 20 \right] \\
 &= 20(e^{-50t} - 1) - 20 \\
 &= 20e^{-50t} - 40 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[c]} \quad v_c &= \frac{10^6}{1.25} \int_0^t -5 \times 10^{-3} e^{-50x} dx - 30 \\
 &= 80(e^{-50t} - 1) - 30 \\
 &= 80e^{-50t} - 110 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad v_d &= 10^6 \int_0^t -5 \times 10^{-3} e^{-50x} dx + 250 \\
 &= 100(e^{-50t} - 1) + 250 \\
 &= 100e^{-50t} + 150 \text{ V}
 \end{aligned}$$

$$\begin{aligned}
 \text{CHECK: } v_b &= -v_c - v_d - v_a \\
 &= -200e^{-50t} \text{ V} \quad (\text{checks})
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad i_1 &= 0.2 \times 10^{-6} \frac{d}{dt} [100e^{-50t} + 150] \\
 &= 0.2 \times 10^{-6} (-5000e^{-50t}) \\
 &= -e^{-50t} \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 \text{[f]} \quad i_2 &= 0.8 \times 10^{-6} \frac{d}{dt} [100e^{-50t} + 150] \\
 &= -4e^{-50t} \text{ mA}
 \end{aligned}$$