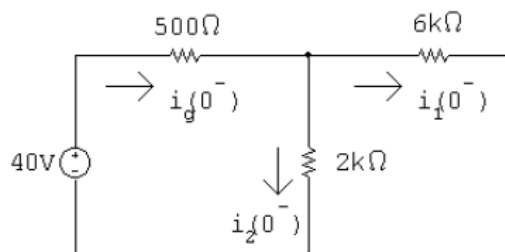


P 7.4 [a] $t < 0$



$$2\text{ k}\Omega \parallel 6\text{ k}\Omega = 1.5\text{ k}\Omega$$

Find the current from the voltage source by combining the resistors in series and parallel and using Ohm's law:

$$i_g(0^-) = \frac{40}{(1500 + 500)} = 20\text{ mA}$$

Find the branch currents using current division:

$$i_1(0^-) = \frac{2000}{8000}(0.02) = 5\text{ mA}$$

$$i_2(0^-) = \frac{6000}{8000}(0.02) = 15\text{ mA}$$

[b] The current in an inductor is continuous. Therefore,

$$i_1(0^+) = i_1(0^-) = 5\text{ mA}$$

$$i_2(0^+) = -i_1(0^+) = -5\text{ mA} \quad (\text{when switch is open})$$

$$[c] \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3}}{8 \times 10^3} = 5 \times 10^{-5}\text{ s}; \quad \frac{1}{\tau} = 20,000$$


$$i_1(t) = i_1(0^+)e^{-t/\tau} = 5e^{-20,000t}\text{ mA}, \quad t \geq 0$$

$$[d] \quad i_2(t) = -i_1(t) \quad \text{when } t \geq 0^+$$

$$\therefore i_2(t) = -5e^{-20,000t}\text{ mA}, \quad t \geq 0^+$$

[e] The current in a resistor can change instantaneously. The switching operation forces $i_2(0^-)$ to equal 15 mA and $i_2(0^+) = -5\text{ mA}$.


P 7.6 For $t < 0$

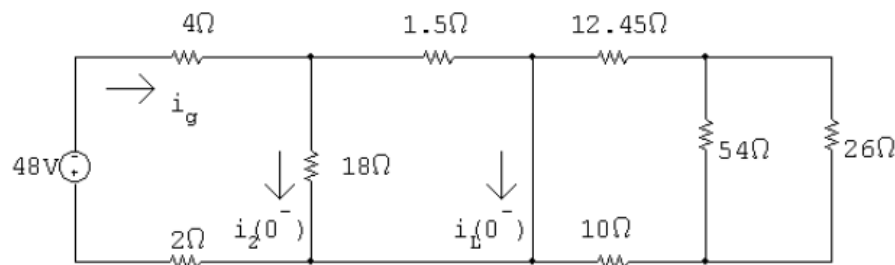

$$i_g = \frac{-48}{6 + (18 \parallel 1.5)} = -6.5 \text{ A}$$

$$i_L(0^-) = \frac{18}{18 + 1.5}(-6.5) = -6 \text{ A} = i_L(0^+)$$

For $t > 0$

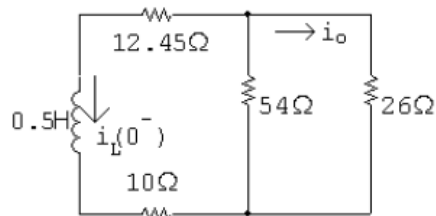


$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.5}{10 + 12.45 + (54 \parallel 26)} = 0.0125 \text{ s}; \quad \frac{1}{\tau} = 80$$

$$i_L(t) = -6e^{-80t} \text{ A}, \quad t \geq 0$$

$$i_o(t) = \frac{54}{80}(-i_L(t)) = \frac{54}{80}(6e^{-80t}) = 4.05e^{-80t} \text{ V}, \quad t \geq 0^+$$


P 7.25 [a] $t < 0$:

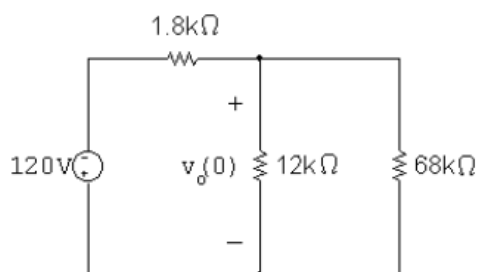

$$R_{\text{eq}} = 12 \text{ k} \parallel 68 \text{ k} = 10.2 \text{ k}\Omega$$

$$v_o(0) = \frac{10,200}{10,200 + 1800}(-120) = -102 \text{ V}$$

$t > 0$:

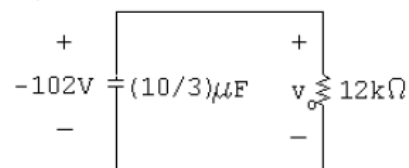

$$\tau = [(10/3) \times 10^{-6}](12,000) = 40 \text{ ms}; \quad \frac{1}{\tau} = 25$$

$$v_o = -102e^{-25t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12,000} = 867 \times 10^{-3} e^{-50t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{12 \times 10^{-3}} 867 \times 10^{-3} e^{-50t} dt \\ &= 17.34 \times 10^{-3} (1 - e^{-50(12 \times 10^{-3})}) = 7824 \mu\text{J} \end{aligned}$$


$$[\text{b}] \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{10}{3}\right) (102)^2 \times 10^{-6} = 17.34 \text{ mJ}$$

$$0.75w(0) = 13 \text{ mJ}$$

$$\int_0^{t_o} 867 \times 10^{-3} e^{-50x} dx = 13 \times 10^{-3}$$

$$\therefore 1 - e^{-50t_o} = 0.75; \quad e^{50t_o} = 4; \quad \text{so } t_o = 27.73 \text{ ms}$$

P 7.26 [a] $t < 0$:

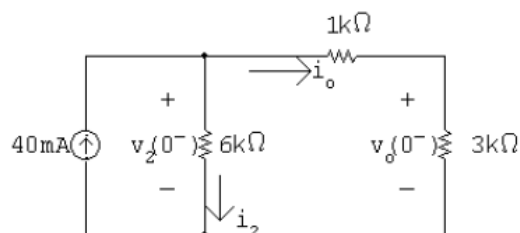


$$i_o(0^-) = \frac{6000}{6000 + 4000}(40 \text{ m}) = 24 \text{ mA}$$

$$v_o(0^-) = (3000)(24 \text{ m}) = 72 \text{ V}$$


$$i_2(0^-) = 40 - 24 = 16 \text{ mA}$$

$$v_2(0^-) = (6000)(16 \text{ m}) = 96 \text{ V}$$

$$t > 0$$

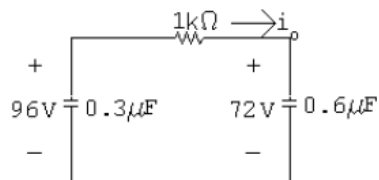

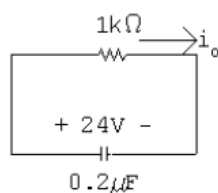
$$\tau = RC = (1000)(0.2 \times 10^{-6}) = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{24}{1 \times 10^3} e^{-t/\tau} = 24e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

[b]

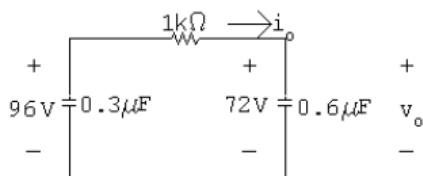

$$\begin{aligned} v_o &= \frac{1}{0.6 \times 10^{-6}} \int_0^t 24 \times 10^{-3} e^{-5000x} dx + 72 \\ &= (40,000) \frac{e^{-5000x}}{-5000} \bigg|_0^t + 72 \\ &= -8e^{-5000t} + 8 + 72 \\ v_o &= [-8e^{-5000t} + 80] \text{ V}, \quad t \geq 0 \end{aligned}$$

[c] $w_{\text{trapped}} = (1/2)(0.3 \times 10^{-6})(80)^2 + (1/2)(0.6 \times 10^{-6})(80)^2$

$$w_{\text{trapped}} = 2880 \mu\text{J}.$$

Check:


$$w_{\text{diss}} = \frac{1}{2}(0.2 \times 10^{-6})(24)^2 = 57.6 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.3 \times 10^{-6})(96)^2 + \frac{1}{2}(0.6 \times 10^{-6})(72)^2 = 2937.6 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$


$$2880 + 57.6 = 2937.6 \quad \text{OK.}$$

P 7.35 [a] $t < 0$

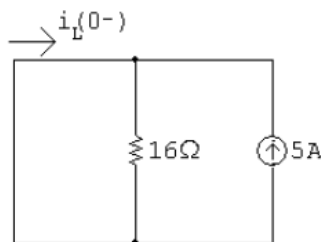

$$i_L(0^-) = -5 \text{ A}$$

$t > 0$

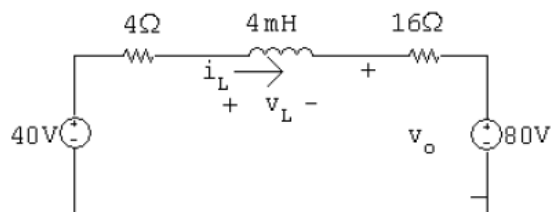

$$i_L(\infty) = \frac{40 - 80}{4 + 16} = -2 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{4 \times 10^{-3}}{4 + 16} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$

$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -2 + (-5 + 2)e^{-5000t} = -2 - 3e^{-5000t} \text{ A}, \quad t \geq 0$$


$$v_o = 16i_L + 80 = 16(-2 - 3e^{-5000t}) + 80 = 48 - 48e^{-5000t} \text{ V}, \quad t \geq 0$$

[b] $v_L = L \frac{di_L}{dt} = 4 \times 10^{-3}(-5000)[-3e^{-5000t}] = 60e^{-5000t} \text{ V}, \quad t \geq 0^+$

$$v_L(0^+) = 60 \text{ V}$$

From part (a) $v_o(0^+) = 0 \text{ V}$

Check: at $t = 0^+$ the circuit is:

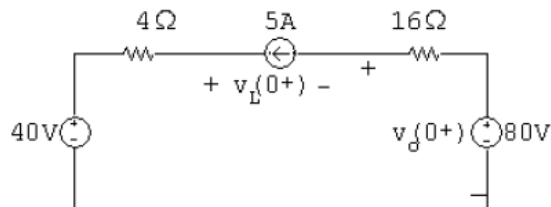

$$v_L(0^+) = 40 + (5 \text{ A})(4 \Omega) = 60 \text{ V}, \quad v_o(0^+) = 80 - (16 \Omega)(5 \text{ A}) = 0 \text{ V}$$

P 7.56 [a] Use voltage division to find the initial value of the voltage:

$$v_c(0^+) = v_{9k} = \frac{9k}{9k + 3k}(120) = 90 \text{ V}$$

[b] Use Ohm's law to find the final value of voltage:

$$v_c(\infty) = v_{40k} = -(1.5 \times 10^{-3})(40 \times 10^3) = -60 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{\text{Th}} = -60 \text{ V}, \quad R_{\text{Th}} = 10k + 40k = 50k\Omega$$

$$\tau = R_{\text{Th}}C = 1 \text{ ms} = 1000 \mu\text{s}$$

$$[d] \quad v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau}$$

$$= -60 + (90 + 60)e^{-1000t} = -60 + 150e^{-1000t} \text{ V}, \quad t \geq 0$$

$$\text{We want } v_c = -60 + 150e^{-1000t} = 0:$$

$$\text{Therefore } t = \frac{\ln(150/60)}{1000} = 916.3 \mu\text{s}$$


$$v_o(0^-) = v_o(0^+) = 40 \text{ V}$$

$$v_o(\infty) = 80 \text{ V}$$

$$\tau = (0.16 \times 10^{-6})(6.25 \times 10^3) = 1 \text{ ms}; \quad 1/\tau = 1000$$


$$v_o = 80 - 40e^{-1000t} \text{ V}, \quad t \geq 0$$

P 7.70 $t < 0$:

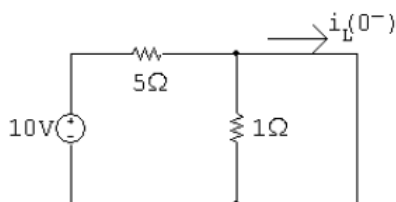

$$i_L(0^-) = 10 \text{ V} / 5 \Omega = 2 \text{ A} = i_L(0^+)$$

$0 \leq t \leq 5$:

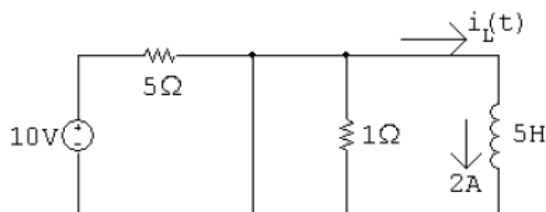


$$\tau = 5/0 = \infty$$

$$i_L(t) = 2e^{-t/\infty} = 2e^{-0} = 2$$

$$i_L(t) = 2 \text{ A} \quad 0 \leq t \leq 5 \text{ s}$$

$$5 \leq t < \infty:$$

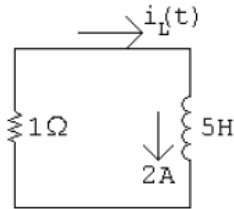

$$\tau = \frac{5}{1} = 5 \text{ s}; \quad 1/\tau = 0.2$$

$$i_L(t) = 2e^{-0.2(t-5)} \text{ A}, \quad t \geq 5 \text{ s}$$

P 8.2 [a] $i_R(0) = \frac{15}{200} = 75 \text{ mA}$

$$i_L(0) = -45 \text{ mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 45 - 75 = -30 \text{ mA}$$

[b] $\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 12,500$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{1.5625 \times 10^8 - 10^8} = -12,500 \pm 7500$$

$$s_1 = -5000 \text{ rad/s}; \quad s_2 = -20,000 \text{ rad/s}$$

$$v = A_1 e^{-5000t} + A_2 e^{-20,000t}$$

$$v(0) = A_1 + A_2 = 15$$


$$\frac{dv}{dt}(0) = -5000A_1 - 20,000A_2 = \frac{-30 \times 10^{-3}}{0.2 \times 10^{-6}} = -15 \times 10^4 \text{ V/s}$$

$$\text{Solving, } A_1 = 10; \quad A_2 = 5$$

$$v = 10e^{-5000t} + 5e^{-20,000t} \text{ V}, \quad t \geq 0$$

$$\begin{aligned}
[\text{c}] \quad i_C &= C \frac{dv}{dt} \\
&= 0.2 \times 10^{-6} [-50,000e^{-5000t} - 100,000e^{-20,000t}] \\
&= -10e^{-5000t} - 20e^{-20,000t} \text{ mA} \\
i_R &= 50e^{-5000t} + 25e^{-20,000t} \text{ mA} \\
i_L &= -i_C - i_R = -40e^{-5000t} - 5e^{-20,000t} \text{ mA}, \quad t \geq 0
\end{aligned}$$

P 8.21

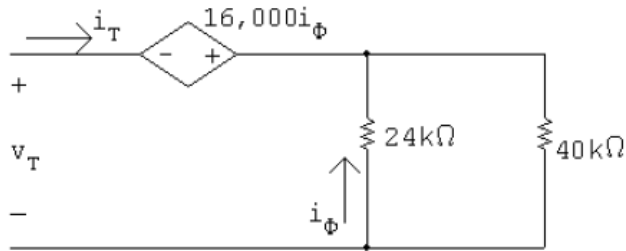

$$v_T = -16,000i_\phi + i_T(15,000) = -16,000 \frac{-i_T(40)}{64} + i_T(15,000)$$

$$\frac{v_T}{i_T} = 10,000 + 15,000 = 25 \text{ k}\Omega$$

$$V_o = \frac{4000}{5000}(7.5) = 6 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{6}{25,000} = -240 \mu\text{A}$$

$$\frac{i_C(0)}{C} = \frac{-240 \times 10^{-6}}{4 \times 10^{-9}} = -60,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(4)(15.625)} = 16 \times 10^6; \quad \omega_o = 4000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(4)(25 \times 10^3)} = 5000 \text{ rad/s}$$

$$\alpha^2 > \omega_0^2 \quad \text{so the response is overdamped}$$

$$s_{1,2} = -5000 \pm \sqrt{5000^2 - 4000^2} = -5000 \pm 3000 \text{ rad/s}$$

$$v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$v_o(0) = A_1 + A_2 = 6 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = -60,000$$

$$\therefore A_1 = -2 \text{ V}; \quad A_2 = 8 \text{ V}$$

$$v_o = 8e^{-8000t} - 2e^{-2000t} \text{ V}, \quad t \geq 0$$