

EE215 – FUNDAMENTALS OF ELECTRICAL ENGINEERING

Tai-Chang Chen
University of Washington, Bothell
Spring 2010

EE215

1

EE215 - FUNDAMENTALS OF EE

- **Electrical Engineering** deals with systems that produce, transmit, and measure electrical signals
- Five major categories:
 - E & M: Communications systems
 - Electronics: device, semiconductors, & transducers
 - Controls & Robotics systems
 - Energy: Power electronics
 - Signal & Image Processing systems
- They all have one thing in common:
Electric Circuits!

EE215

© TC Chen UWB 2010 2

EE215 – GOALS AND OBJECTIVES

- Goals:
 - Develop the tools to design and analyze (linear) circuits
 - Learn the “alphabet” of circuits including
 - Wires and switches
 - Resistors
 - Capacitors
 - Inductors
 - Independent and dependent voltage and current sources
 - Operational amplifiers

EE215 – GOALS AND OBJECTIVES

- Objectives:
 - Identify linear systems and represent them in schematic form
 - Apply Kirchhoff’s and Ohm’s Law
 - Simplify circuits
 - Perform node and loop analysis
(→ systems of linear equations)
 - Identify and model first and second order electric systems involving capacitors and inductors
(→ differential equations)
 - Predict their transient behavior

COURSE ADMINISTRATION (1)

- Instructor: Tai-Chang Chen (tcchen@u)
- Textbook: Nilsson & Riedel, Electric Circuits 9th ed.
 - class will follow textbook closely
 - beware of typo's
- Recitation sessions:
 - Review of class material, work out more elaborate examples, build and present lab circuits, discuss material with other students

EE215

© TC Chen UWB 2010 5

COURSE ADMINISTRATION (2)

- Grades:
 - Homeworks (20%): top 6 of 7
 - Homeworks are individual work
 - Not all problems may be graded
 - Homeworks are due at the beginning of class Fridays
 - Labs (20%): 5 demos + reports
 - Exams (60%)
 - One midterm @ 30%, one final @ 30%
 - Tentative midterm date: 05/07
 - Final Exam: 06/11

EE215

© TC Chen UWB 2010 6

ANNOUNCEMENTS

- NO recitation sessions this week.
- 1st homework posted today.
- 1st Lab posted today, due on the 3rd week.
- Materials covered this week: chapter 1; 2.1-2.3

WEEK 1 CIRCUIT BASICS

March 31, 2010

QUESTIONS TO ANSWER


- Electric Circuits
 - What is an electric circuit?
 - How to build an electric circuit?
- Current, Voltage, and Power
 - What are those parameters?
 - What is Ohm's law?
- Power calculation (passive sign convention)
 - What is the developed or dissipated power?

EE215

© TC Chen UWB 2010 9

ELECTRIC CIRCUITS

- Example: car battery

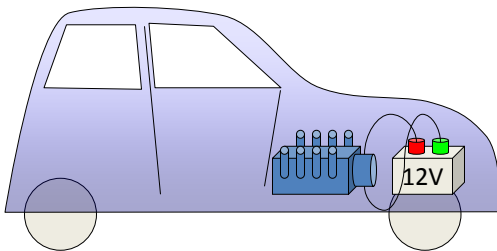

"actual electrical system"


EE215

© TC Chen UWB 2010 10

BASIC CIRCUIT ELEMENTS

- Ideal basic circuit elements:

- General representation:

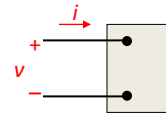

EE215

© TC Chen UWB 2010 11

IDEAL BASIC CIRCUIT ELEMENTS

- Ideal voltage source
- Ideal current source
- Resistor
- List of circuit elements to be continued...

EE215

© TC Chen UWB 2010 12

CURRENT AND VOLTAGE SOURCES

- Example: which circuits are permissible, and which violate the constraints imposed by ideal sources?
 - (a)
 - (b)
 - (c)
 - (d)

EE215

© TC Chen UWB 2010 13


CURRENT (1)

- Electrical current

EE215

© TC Chen UWB 2010 14

CURRENT (2)

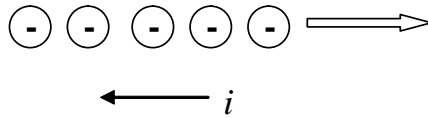

(The reason for this is that Ben Franklin had to pick a direction for current flow. He had no idea what actually moved. He guessed wrong.)

Don't worry too much about what physically moves until you are inside the guts of semiconductors in advanced EE courses. Just think of current as the flow of positive charge.

EE215

© TC Chen UWB 2010 15

CURRENT (3)

- Charge, q ,
- Current, i ,

EE215

© TC Chen UWB 2010 16

VOLTAGE (1)


- Like pressure making water flow, creating a current, voltage
-
- Voltage has symbol v and units of volts (V), named after an Italian physicist. (Volta of frog leg fame.)
- Pressure is measured between two points, a high pressure point and a low pressure point. (Even when you measure the pressure in a tire, you are measuring the pressure between the tire and the atmosphere.)

EE215

© TC Chen UWB 2010 17

VOLTAGE (2)

- Similarly, voltage is measured between two points,

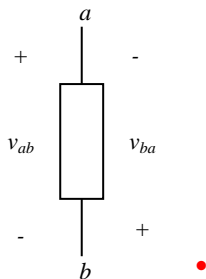

EE215

© TC Chen UWB 2010 18

POWER (1)

- Another definition of voltage,

EE215

© TC Chen UWB 2010 19

POWER (2)

- where W is work.

- A lot of the general public get power and energy mixed up. Power, p , is

EE215

© TC Chen UWB 2010 20

POWER (3)

- Let's do a trick and apply the Chain Rule.

Now note that we know what each of the derivatives in the chain is: voltage and current! So

CAR BATTERY EXAMPLE (AGAIN)

- What is **Ohm's Law** ?

RESISTORS AND OHM'S LAW


-

EE215

© TC Chen UWB 2010 23

CAR BATTERY EXAMPLE (AGAIN)


- What is the **developed** or **dissipated** power ?

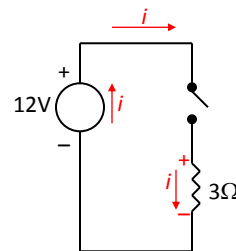

EE215

© TC Chen UWB 2010 24

CAR BATTERY EXAMPLE (AGAIN)

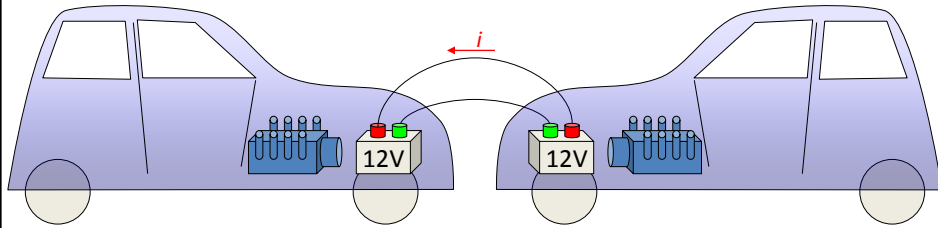

EE215

© TC Chen UWB 2010 25

MORE IDEAL BASIC CIRCUIT ELEMENTS

- Ideal dependent sources
- Ideal dependent voltage-controlled voltage source (VCVS)
- Ideal dependent voltage-controlled current source (VCCS)

EE215

© TC Chen UWB 2010 26

MORE IDEAL BASIC CIRCUIT ELEMENTS

- Ideal dependent current-controlled voltage source (CCVS)
- Ideal dependent current-controlled current source (CCCS)
- Capacitor (to be discussed later)
- Inductor (to be discussed later)

EE215

© TC Chen UWB 2010 27

MORE EXAMPLES: CURRENT AND VOLTAGE SOURCES

(a)

(b)

(c)

(d)

EE215

© TC Chen UWB 2010 28

POWER DISSIPATION IN RESISTORS

- Recall that power is
- Therefore
- Example (a):

EE215

© TC Chen UWB 2010 29

MORE EXAMPLES

(b)

(c)

(d)

EE215

© TC Chen UWB 2010 30

PASSIVE SIGN CONVENTION

- It is useful to establish an agreement about voltage drop, direction of current, and sign of voltage / current.

EXAMPLES

(a)

(b)

(c)

A MORE INTERESTING EXAMPLE

- What does this circuit do?

