

# EE215 – FUNDAMENTALS OF ELECTRICAL ENGINEERING

Tai-Chang Chen  
University of Washington, Bothell  
Spring 2010

EE215

1

## WEEK 3 CIRCUIT ANALYSIS (I)

April 16<sup>th</sup> , 2010

EE215

© TC Chen UWB 2010

2

## QUESTIONS TO ANSWER

- Terminology
  - What are those terminologies?
- Node Voltage method
  - What is a reference node?
  - How to establish node voltage equations for an electric circuit?
- Supernode
  - What is a supernode?
  - How to apply the technique to analyze an electric circuit?

EE215

© TC Chen UWB 2010 3

## SYSTEMATIC TECHNIQUES FOR CIRCUIT ANALYSIS

- Kirchhoff's Laws, Ohm's Law, (and  $\Delta$ -Y-transforms) gave us some basic tools to analyze resistive circuits.
- These tools will become cumbersome for more complex circuits.
- Need to develop more powerful, systematic methods for circuit analysis.
  - "Node-Voltage-Method"
  - "Mesh-Current-Method"

EE215

© TC Chen UWB 2010 4

# TERMINOLOGY


## Definitions

- Essential node:
- Branch:
- Essential branch:
- Mesh:
- Planar circuit:

EE215

© TC Chen UWB 2010 5

## EXAMPLE

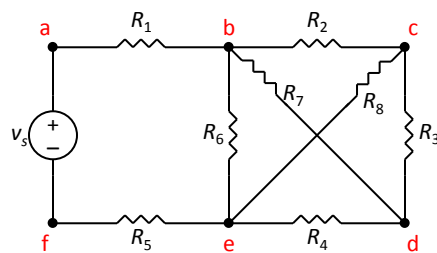

- Essential nodes:
- Essential branches:
- Meshes:
- Planar circuit:

EE215

© TC Chen UWB 2010 6

## EXAMPLE

- Essential nodes:  
b, c, d, e
- Essential branches:  
bc, bd, be, bafe, ce, cd, de
- Meshes:
- Planar circuit:


EE215

© TC Chen UWB 2010 7

## NODE VOLTAGE METHOD

Example

- Nodes:
- Essential nodes:
- Essential branches:
- Meshes:

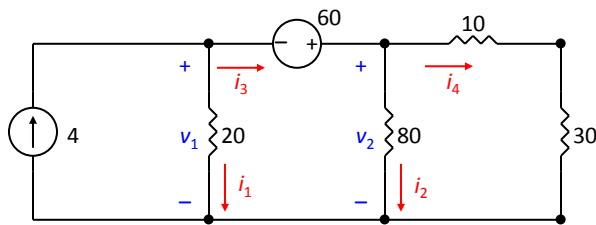

EE215

© TC Chen UWB 2010 8

## NODE VOLTAGE METHOD (2)


- How do we solve this system?
- Approach 1

EE215

© TC Chen UWB 2010 9

## NODE VOLTAGE METHOD (3)

- Approach 2

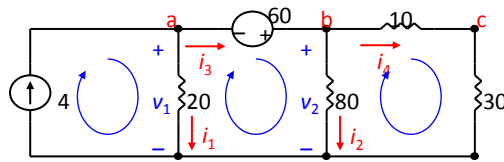

EE215


© TC Chen UWB 2010 10

## NODE VOLTAGE METHOD (4)

- Essential nodes:

a: (1)

b: (2)

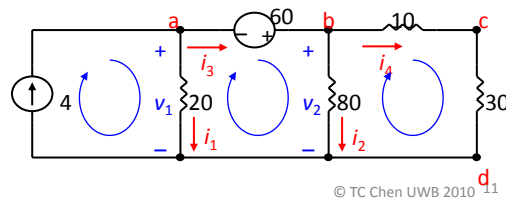

EE215

© TC Chen UWB 2010 11


## NODE VOLTAGE METHOD (5)

- $b_e = 5$  currents (1 is known)

Need to derive 2 more eq.s from meshes

abd: (3)

bcd: (4)

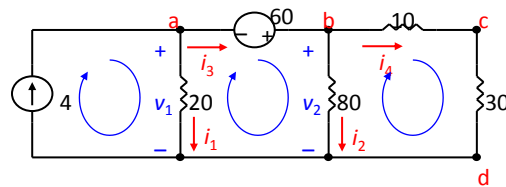

EE215

© TC Chen UWB 2010 12

## NODE VOLTAGE METHOD (6)

- Essential nodes:  
 a:  $-4 + i_1 + i_3 = 0$  (1)  
 b:  $-i_3 + i_2 + i_4 = 0$  (2)
- $b_e = 5$  currents (1 is known)  
 Need to derive 2 more eq.s from meshes  
 abd:  $-60 + 80i_2 - 20i_1 = 0$  (3)  
 bcd:  $10i_4 + 30i_4 - 80i_2 = 0$  (4)  
 From (1):  
 Plug into (3):  
 From (2)  
 Plug into (4):

EE215

© TC Chen UWB 2010 13

## NODE VOLTAGE METHOD (7)

- Now we have 2 eq.s with 2 unknowns:

EE215

© TC Chen UWB 2010 14

## NODE VOLTAGE METHOD (8)

- Is there a faster solution?
- **Definition:**
- Note: Node voltages appeared in eq.s (3) and (4).
- Approach 3:

EE215

© TC Chen UWB 2010 15

## NODE VOLTAGE METHOD (9)

- **Node Voltage:** Voltages are measured between two points.
- We have been using the ends of circuit elements as the points, and getting the voltage across the element.
- But what if we chose one node and measured all other voltages with respect to that node?
- We call the one node we choose the **reference node**.

EE215

© TC Chen UWB 2010 16


## NODE VOLTAGE METHOD (10)

- **reference node.** :
- We mark the reference node with a special symbol, also called the ground symbol.
- The voltage between any node and the reference node is then a **node voltage**.

EE215

© TC Chen UWB 2010 17

## NODE VOLTAGE METHOD (11)

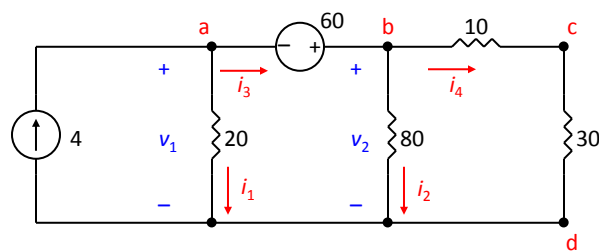

a:  
b:


(1)  
(2)  
(3)

- (1) + (2), plug in (3):

EE215

© TC Chen UWB 2010 18

## NODE VOLTAGE METHOD (12)

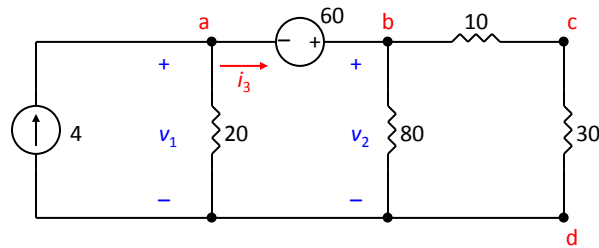

- Can we do even better?


•

•

EE215

© TC Chen UWB 2010 19

## NODE VOLTAGE METHOD (13)

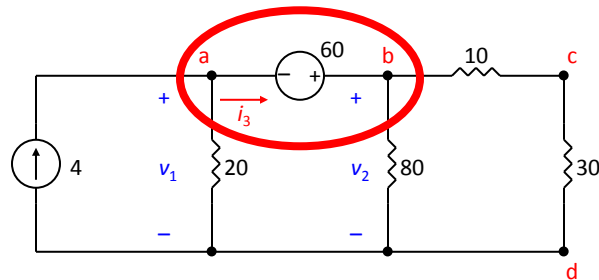

- KCL holds for this supernode:

(1')

(3')

EE215

© TC Chen UWB 2010 20


## DEPENDENT SOURCES IN THE NODE VOLTAGE METHOD (1)

- Modify our previous example:
  - Replace 60V source with current dependent voltage source (CDVS).

EE215

© TC Chen UWB 2010 21
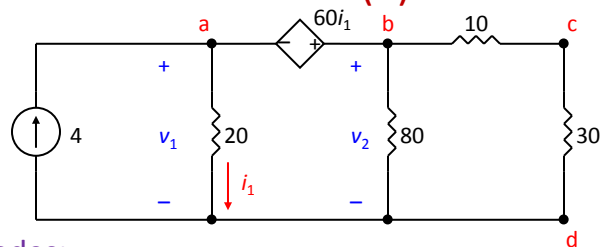
## DEPENDENT SOURCES IN THE NODE VOLTAGE METHOD (2)



- Solve circuit:
  - Find essential nodes:
  - Identify node voltages and reference node:
  - Identify supernode(s):
  - Set up equation(s) for each (super)node:


(1)

(2)

EE215

© TC Chen UWB 2010 22
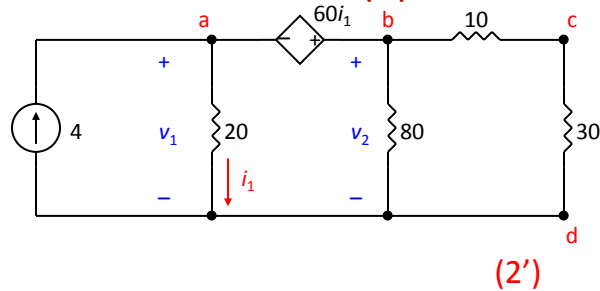
## DEPENDENT SOURCES IN THE NODE VOLTAGE METHOD (3)




- From (2):
- Plug (2') into (1):

EE215

© TC Chen UWB 2010

23
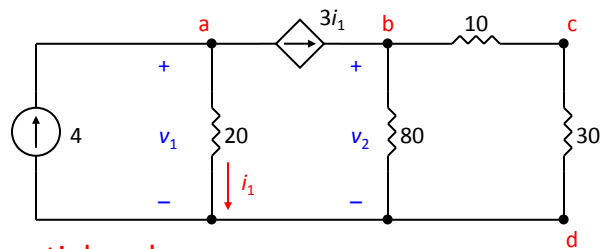
## MODIFIED EXAMPLE: REPLACE CDVS WITH CDCS



- No supernodes!
- Equations for essential nodes:
  - At a: (1)
  - At b: (2)
- From (1):
- Plug into (2):

EE215

© TC Chen UWB 2010 24