

# EE215 – FUNDAMENTALS OF ELECTRICAL ENGINEERING

Tai-Chang Chen  
University of Washington, Bothell  
Spring 2010

EE215

1

## WEEK 5 CIRCUIT ANALYSIS (III) & OPERATIONAL AMPLIFIERS

April 30<sup>th</sup> , 2010

EE215

© TC Chen UWB 2010

2

## QUESTIONS TO ANSWER

- Thévenin and Norton Equivalents
  - What are the Thevenin and Northon equivalents?
  - How to simplify electric circuits to those equivalents?
- Maximum Power Calculation
  - What is the condition of a resistive network to deliver maximum power?
  - How to calculate the maximum power delivered by the network?
- Operational Amplifier
  - What is an op amp and its circuit symbol?
  - What are the common configurations of op amps and their gains?

EE215

© TC Chen UWB 2010 3

## THÉVENIN AND NORTON EQUIVALENTS

April 30<sup>th</sup> , 2010

EE215

© TC Chen UWB 2010

4

## THÉVENIN AND NORTON EQUIVALENTS

- Every network consisting of independent and dependent sources and resistors with two terminals a and b can be replaced with equivalent circuits of the following form:

EE215

© TC Chen UWB 2010

5

## THÉVENIN AND NORTON EQUIVALENTS

- Thévenin and Norton equivalents are very useful if we are only interested in the effect on a load.
  - Example: home power outlet, car battery, ...
- How do we determine  $v_{Th}$  and  $R_{Th}$ ?
  - Open circuit
    - ➔
  - Short circuit
    - ➔
  - Dead network resistance
    - ➔

EE215

© TC Chen UWB 2010

6


## THÉVENIN AND NORTON EQUIVALENTS

- Therefore, we know the Thévenin equivalent if we know the open circuit voltage, the short circuit current, or dead network resistance.
  - Don't try this at home!

## EXAMPLE (1)

- Open circuit:

## EXAMPLE (1)

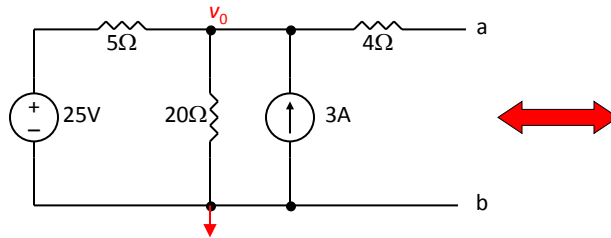


- Short circuit:

EE215

© TC Chen UWB 2010

9

## EXAMPLE (2A)

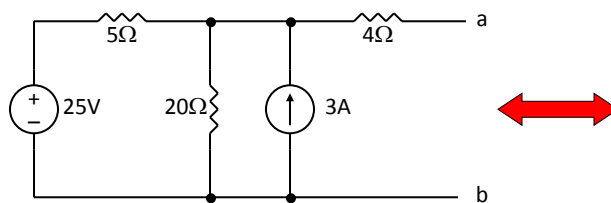


- We could have obtained the same result with source transformations

EE215

© TC Chen UWB 2010

10

## EXAMPLE (2B)

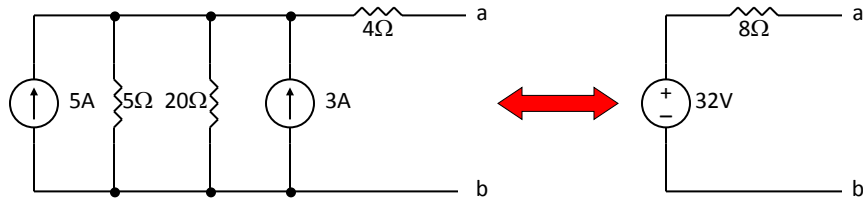

Replace combined current source with Thévenin equivalent:

## EXAMPLE (2C)

# MAXIMUM POWER TRANSFER

April 30<sup>th</sup> , 2010

EE215


© TC Chen UWB 2010

13


## MAXIMUM POWER TRANSFER (1)

- For what output load  $R_L$  is the power maximized?

- General resistive network:

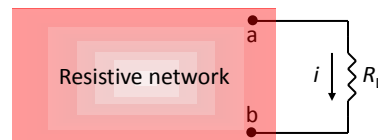

- Find Thévenin equivalent:

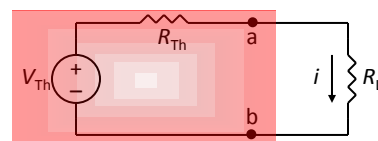

EE215

© TC Chen UWB 2010

14

## MAXIMUM POWER TRANSFER (2)

- Calculate output power  $p$ :
- Find load  $R_L$  such that  $p$  is maximized:
- Max. power if load is equal to Thévenin resistance

## OPERATIONAL AMPLIFIER

April 30<sup>th</sup> , 2010



## OPERATIONAL AMPLIFIER (1)


- The operational amplifier, or op amp for short, is a fundamental building block in circuit design. Stuffed inside a chip are a bunch of transistors and other elements that make up a near-ideal voltage controlled voltage source (VCVS) with near-infinite gain. Of course, we'll start by assuming it is ideal...

## OPERATIONAL AMPLIFIER (2)

- **Circuit Symbol:**
  - The op amp has a special circuit symbol, a triangle with two inputs and one output

## OPERATIONAL AMPLIFIER (3)

- Voltage transfer characteristic:

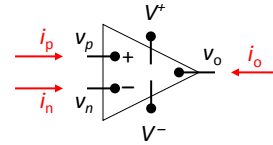

## OPERATIONAL AMPLIFIER (4)

- **Slew Rate:**
  - At this point we should probably note that another departure from ideality in the op amp is that the slew rate, is also limited. This affects how fast the op amp responds to a step change in input, and how high a frequency it can operate at.

## OPERATIONAL AMPLIFIER (5)

- Operation in the linear region:
  - 
  - 
  - 
  - 
  -
- Op amps have very high input resistance.
  - 
  - 
  -

EE215

© TC Chen UWB 2010

21

## OPERATIONAL AMPLIFIER (6)

- **Ideal Op Amps Relationships:**
  - An ideal op amp is an ideal voltage controlled voltage source. We can think of the op amp symbol being replaced as follows:

EE215

© TC Chen UWB 2010

22

## OPERATIONAL AMPLIFIER (7)

- Negative feedback can be used to ensure operation in the linear region.

—

—

EE215

© TC Chen UWB 2010

23

## OPERATIONAL AMPLIFIER (8)

- Inverting Amplifier:

EE215

© TC Chen UWB 2010

24

## OPERATIONAL AMPLIFIER (9)

- Summing Amplifier:

## OPERATIONAL AMPLIFIER (10)

- Non-inverting Amplifier:

## OPERATIONAL AMPLIFIER (11)

- Differential Amplifier:

EE215

© TC Chen UWB 2010

27

## OPERATIONAL AMPLIFIER (12)

### Remember:

- Input current:  $i_p = i_n = 0$
- Virtual short condition (in linear region):  $v_p = v_n$
- First assume op amp operates in linear region.
  - If this leads to a contradiction, then op amp is in saturation.

EE215

© TC Chen UWB 2010

28