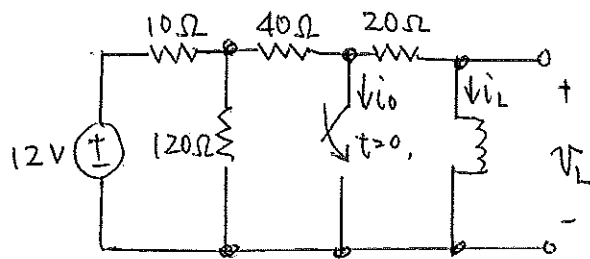


Example: 7.5



Switch has been open for a long time.

- (a) Find  $i_o(0^-)$ ;  $i_L(0^-)$ ;  
 $i_o(0^+)$ ;  $i_L(0^+)$ ;  
 $i_o(\infty)$ ;  $i_L(\infty)$ ;

(b)  $i_L(t)$  for  $t \geq 0$ .


(c) Find  $v_L(0^-)$ ,  $v_L(0^+)$ ,  $v_L(\infty)$ .

(d)  $v_L(t)$  for  $t \geq 0$ .

(e)  $i_o(t)$  for  $t \geq 0$ .

(a)  $0^- = t$ , open circuit for  $i_o \Rightarrow i_o(0^-) = 0$ .

Inductor  $\rightarrow$  short circuit.

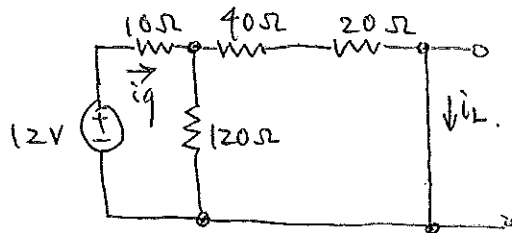


$$120 \parallel 60 = 40 \Omega$$

$$i_g = \frac{12}{10+40} = 0.24 \text{ A}$$

$$i_L(0^-) = i_g \times \frac{120}{120+60} = 160 \text{ mA}$$

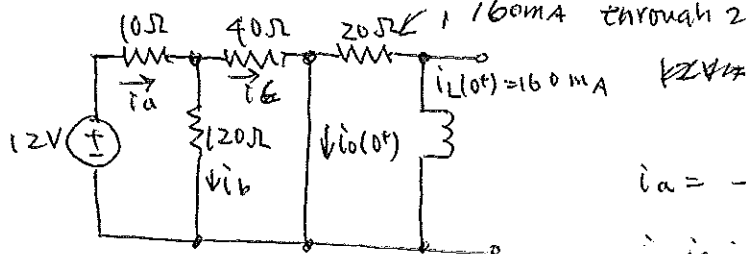$t = 0^+$ ,  $i_L(0^+) = 160 \text{ mA}$ . (Current cannot change instantaneously).



$$120 \parallel 40 = 30 \Omega$$

$$i_a = \frac{12}{10+30} = 0.30 \text{ A} = 300 \text{ mA}$$

$$i_c = 300 \text{ mA} \times \frac{120}{120+40} = 225 \text{ mA}$$

$$i_o(0^+) = i_c - 160 \text{ mA} = 65 \text{ mA}$$

$t = \infty$ ,  $i_o(\infty) = 225 \text{ mA}$  (all current through short circuit).

$$i_L(\infty) = 0 \text{ A}$$

(b)  $i_L(t)$  for  $t \geq 0$ , use the formula:  $i_L(t) = i_L(\infty) + (i_L(0) - i_L(\infty)) e^{-\frac{R}{L}t}$

$$-\frac{R}{L} = \frac{20}{100 \times 10^{-3}} = 200; i_L(t) = 160 \cdot e^{-200t} \text{ mA}$$

(c)  $v(0^-) = 0 \text{ V}$ . (inductor  $v = L \frac{di}{dt}$ ,  $i = \text{const}$ ).


$$v(0^+) \stackrel{\text{KVL}}{=} 20 \Omega + \text{inductor}: 20 \times (0 - 160) + v_L(0^+) = 0. v_L(0^+) = -3.2 \text{ V}$$

$$V_L(\infty) = 0, \text{ (short circuit).}$$

(d)  $V_L(t)$  for  $t \geq 0$ .

$$\begin{aligned} V_L(t) &= V_L(\infty) + (V_L(0) - V_L(\infty)) e^{-200t} \\ &= 0 + (-3.2 - 0) e^{-200t} = -3.2 e^{-200t} \text{ V.} \end{aligned}$$

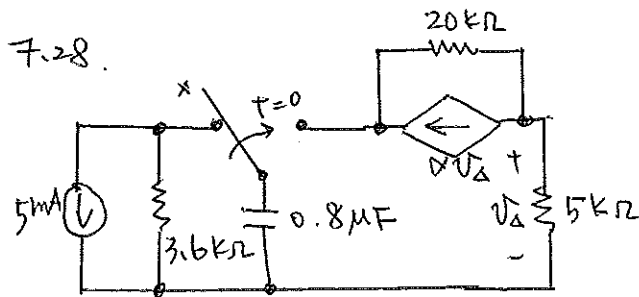
(e)  $i_o(t) = i_C - i_L(t) = 225 - 160 e^{-200t} \text{ mA } t \geq 0$ .



Find:  $\alpha$  so  $\tau = 40 \text{ ms}$

(b)  $V_{\Delta} \quad t \geq 0$ .

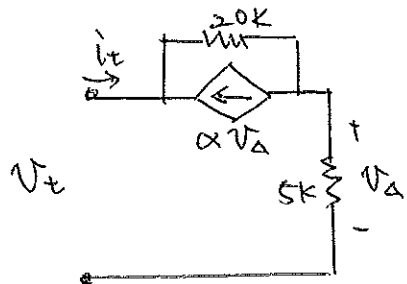(a) The circuit is not the standard form of RC circuit we familiar with. Apply Thevenin ~~to~~ respect to the terminals of capacitor to simplify circuit:



Apply test voltage to solve for  $R_{th}$ ...  
Need  $R_{th}$  to solve  $R_{th}C = \tau$ .

Applying KVL:

$$V_t = (i_t + \alpha V_{\Delta}) 20k + V_{\Delta}$$

$$\therefore V_{\Delta} = 5000 i_t.$$

$$\Rightarrow V_t = 25000 i_t + 20 \times 10^3 \alpha (5000 i_t)$$


$$R_{th} = \frac{V_t}{i_t} = 25000 + 100 \times 10^6 \alpha$$

$$\tau = 40 \times 10^{-3} = R_{th} C = (25000 + 100 \times 10^6 \alpha) \times C$$

$$R_{th} = 50 k\Omega = 25000 + 100 \times 10^6 \alpha$$

$$\alpha = 2.5 \times 10^{-4} \text{ A/V.}$$

(b) therefore:  $t \geq 0^+$

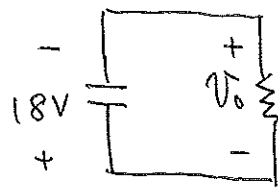


$$V_c(0^+) = 18V$$

$$V_0(0^+) = -18V$$

$$V_0(t) = -18e^{-\frac{t}{\tau}} \quad V(t \geq 0) \text{ simple RC.}$$

Apply to original circuit:

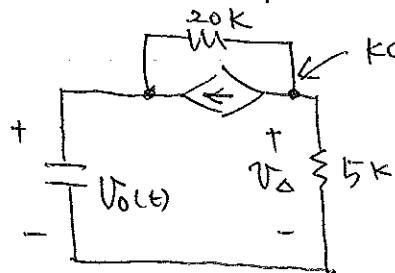

$$KCL: \frac{V_\Delta}{5000} + \frac{V_\Delta - V_0}{20000} + 2.5 \times 10^{-4} V_\Delta = 0$$

$$4V_\Delta + V_\Delta - V_0 + 5V_\Delta = 0$$

$$\therefore V_\Delta = \frac{V_0}{10} = -1.8 \times 10^{-2} e^{-\frac{t}{\tau}} \quad V(t \geq 0)$$