
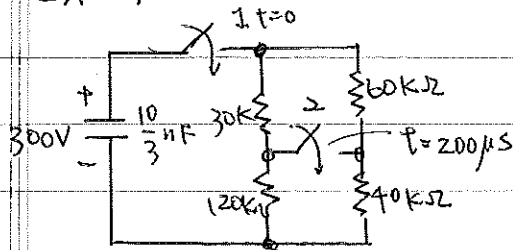


Example: 7.75.

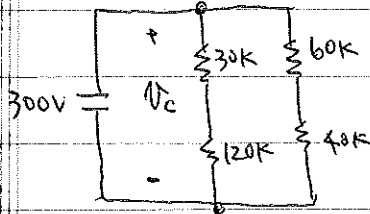

Find the magnitude and direction of the current in the 2nd switch 300 μ s after switch 1 closes.

① $t \geq 0$ and $t \leq 200 \mu$ s. Switch 1 closes. Switch 2 opens.



$\Rightarrow$ Find the current at $t = 200 \mu$ s.
as the initial condition of $t > 200 \mu$ s. $\therefore$
capacitor starts to discharge $\therefore$

Find: $V_C(t)$

$$R_{eq} = 150k \parallel 100k = 60k\Omega \quad (\text{Simple RC natural decay})$$


$$\tau = RC = \left(\frac{10}{3} \times 10^{-9}\right) \times (60 \times 10^3) = 200 \mu s.$$

$$V_C(t) = 300 \cdot e^{-\frac{t}{\tau}} \quad V. \quad (V_C(t) = A + B e^{-\frac{t}{\tau}}) \quad \begin{cases} A = 0. \\ B = 300. \end{cases}$$

At $t = 200 \mu$ s:

$$V_C(200 \mu s) = 300 e^{-1} = 110.36 V.$$

② when $t \geq 200 \mu$ s.

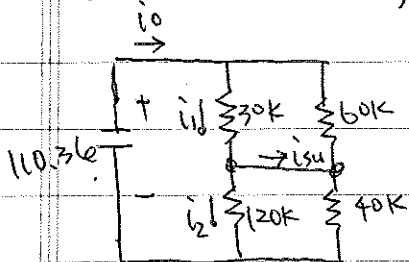

Simplify the circuit to a standard RC circuit...

$$R_{eq} = 30k \parallel 60k + 120k \parallel 40k = 50k\Omega,$$

$$\tau = \left(\frac{10}{3} \times 10^{-9}\right) (50 \times 10^3) = 166.67 \mu s.$$

$$\frac{1}{\tau} = 6000.$$

$$V_C(t) = 110.36 \times e^{-6000(t-200 \mu s)} \quad V.$$


$$\text{at } t = 300 \mu s; \quad V_C(300 \mu s) = 110.36 \cdot e^{-6000 \times 100 \mu s} = 60.57 V.$$

$$i_0(300 \mu s) = 60.57 / 50k = 1.21 \text{ mA}.$$

$$i_1(300 \mu s) = i_0(300 \mu s) \times \frac{60}{90} = 0.807 \text{ mA}.$$

$$i_2(300 \mu s) = i_0(300 \mu s) \times \frac{40}{160} = 0.303 \text{ mA}$$

Example: 8.21.

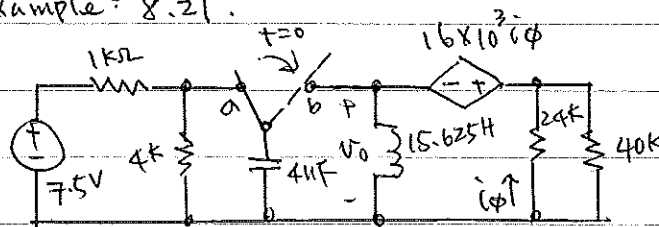


Find $V_0(t)$ for $t \geq 0$.

(RLC natural response).

When $t > 0$, we have non-standard RLC circuit...

First, simplify the circuit after $t > 0$, to standard RLC...

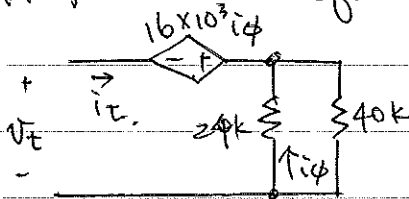⇒ apply Thevenin equivalent w.r.t. Inductor:



KVL:

$$V_t = -16000 i_\phi + i_\phi \times (24k\Omega + 40k\Omega)$$


$$= -16000 i_\phi + i_\phi \times 15000$$

$$\text{and } i_\phi = -i_t \times \frac{40}{64}$$

$$\Rightarrow V_t = -16000 \times (-i_t \times \frac{40}{64}) + 15000 i_t$$

$$\Rightarrow \frac{V_t}{i_t} = 10000 + 15000 = 25k\Omega$$

Therefore the circuit after $t > 0$:

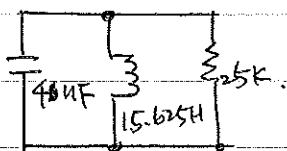

Find initial condition:

$$V_0 = 7.5 \times \frac{4k}{1k+4k} = 6V. \quad I_0 = 0 \text{ Amp.}$$

① Characteristic equation for RLC in parallel:

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0. \quad s_{1,2} = \frac{-\alpha \pm \sqrt{\alpha^2 - \omega_0^2}}{2}$$

$$\alpha = \frac{1}{2RC} = 5000 \text{ rad/s.} \quad \omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = 4000 \text{ rad/s}$$

$$\alpha^2 - \omega_0^2 > 0. \text{ Overdamped.} \quad s_{1,2} = -5000 \pm 3000 \text{ rad/s}$$

$$= -2000; -8000.$$

② Find $V_c(0^+)$ and $\frac{dV_c(0^+)}{dt}$:

$$V_c(0^+) = 6V. = A_1 + A_2$$

$$\frac{dV_c(0^+)}{dt} = \frac{i_c(0)}{C} = \frac{-i_R(0) - i_L(0)}{C} = \frac{-\frac{6}{25k} - 0}{4 \times 10^{-9}} = -60000$$

$$-60000 = A_1 s_1 + A_2 s_2$$

Therefore :

$$A_1 = -2 \text{ V.} \quad A_2 = 8 \text{ V.}$$

$$\text{Solution : } V_0(t) = 8e^{-8000t} - 2e^{-2000t} \text{ V.}$$