

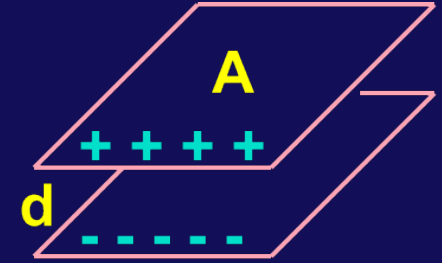


Capacitors: Part 1

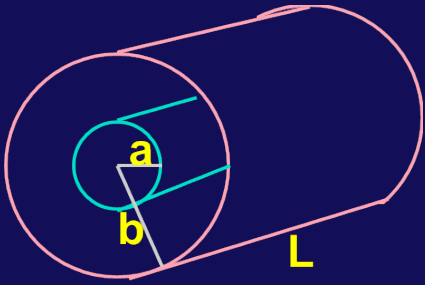

$$C \equiv \frac{Q}{V}$$

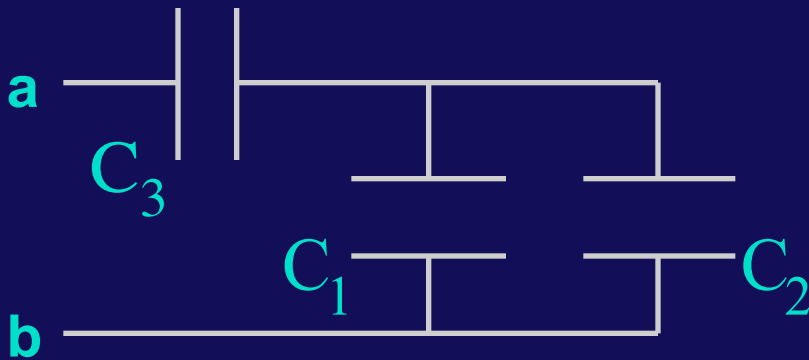


0



- Long-answer REGRADEs DUE today by 4 pm; turn in directly to Alexis Olsho; no special form required
- Dielectrics and more Capacitor stuff on **Monday**
 - no new Smart Physics due
- Go over tough significant figure problem on homework

Energy in Capacitors

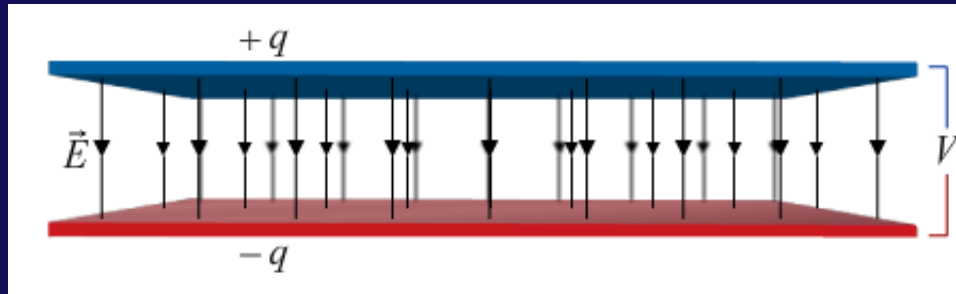

- The work done (usually by a battery) to separate the charges on a capacitor is stored (and can later be retrieved) as Electric Potential Energy

$$\Delta U = q\Delta V$$

- We charge a capacitor by moving dq through an existing $V(q)$, and integrate to get energy stored:

$$\Delta U = \int dU = \int V(q) dq \quad \text{where } V(q) = q/C$$


$$\Delta U = \int_0^{Q_{\max}} \frac{q}{C} dq = \frac{Q_{\max}^2}{2C} = \frac{Q_{\max} V_{\max}}{2} = \frac{1}{2} C V_{\max}^2$$

Equivalent Expressions: Energy in Capacitors

$$U = \frac{1}{2} CV^2$$

$$C = Q/V$$

$$U = \frac{1}{2} QV$$

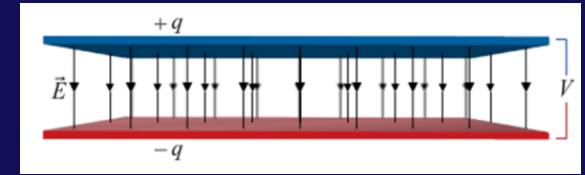

$$V = Q/C$$

$$U = \frac{1}{2} \frac{Q^2}{C}$$

• Energy Density:

– The energy stored (per volume) in ANY electric field


» Not just our parallel plate case

» Units: J / m^3

$$u \equiv \frac{U}{Vol} = \frac{\frac{1}{2} CV^2}{Ad} = \frac{\frac{1}{2} \epsilon_0 AV^2 / d}{Ad} = \frac{1}{2} \frac{\epsilon_0 V^2}{d^2} \rightarrow u = \frac{1}{2} \epsilon_0 E^2$$

Recall: $(V/d = E)$

Example: Cylindrical Capacitor

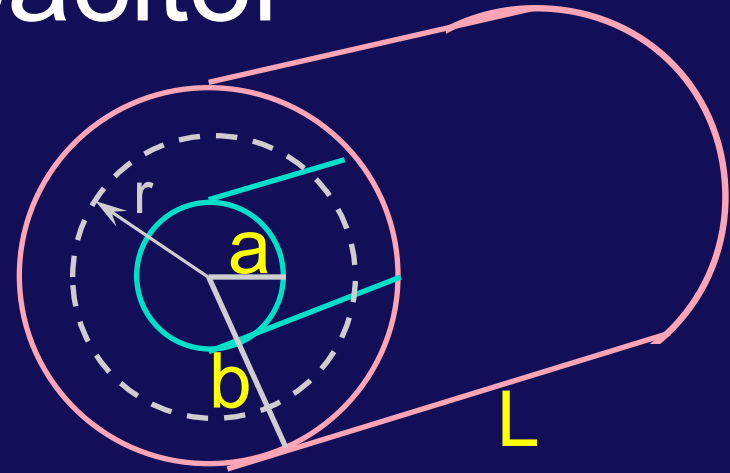


- Calculate the capacitance:
- Assume $+Q$, $-Q$ on surface of cylinders with potential difference V .

Recall: Cylindrical Symmetry

- Gaussian surface is cylinder of radius r and length L
- Cylinder has charge Q
- Apply Gauss' Law:
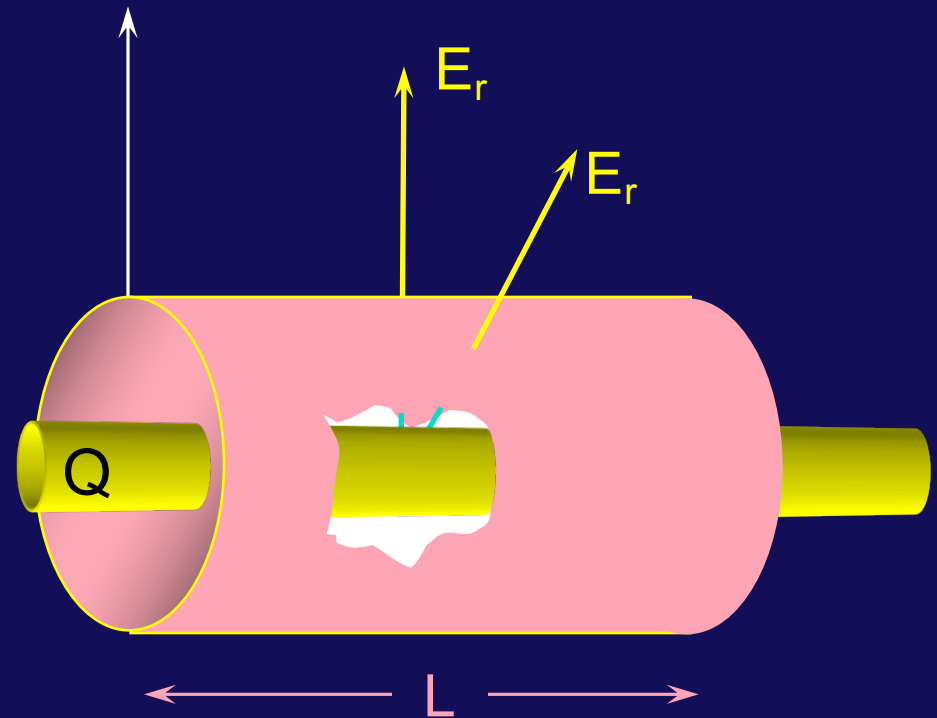
$$\oint \vec{E} \cdot d\vec{S} = 2\pi r L E = \frac{Q}{\epsilon_0}$$



Ⓟ


$$E = \frac{Q}{2\pi\epsilon_0 L r}$$

This is not new

Example: Cylindrical Capacitor

- Calculate the capacitance:
- Assume $+Q$, $-Q$ on surface of cylinders with potential difference V .
- From Gauss' Law:

$$E = \frac{Q}{2\pi\epsilon_0 rL}$$

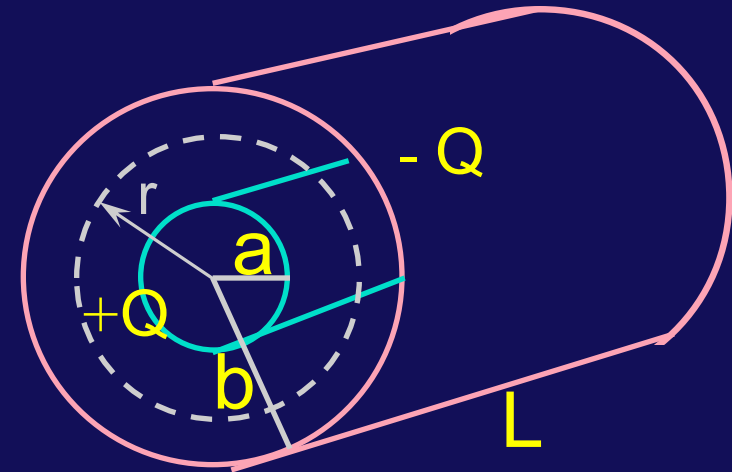

If inner cylinder has $+Q$, then the potential V is positive if we take the zero of potential to be defined at $r = b$:


$$V = -\int_b^a \vec{E} \cdot d\vec{l} = -\int_b^a E dr = \int_a^b \frac{Q}{2\pi\epsilon_0 rL} dr = \frac{Q}{2\pi\epsilon_0 L} \ln\left(\frac{b}{a}\right)$$

p


$$C \equiv \frac{Q}{V} = \frac{2\pi\epsilon_0 L}{\ln\left(\frac{b}{a}\right)}$$

Clicker

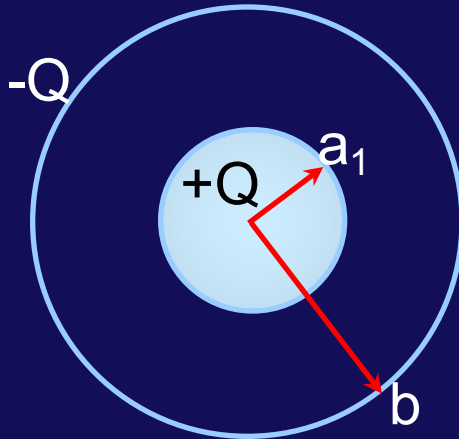- In each case below, a charge of $+Q$ is placed on a solid spherical conductor and a charge of $-Q$ is placed on a concentric conducting spherical shell.
 - Let V_1 be the potential difference between the spheres with (a_1, b) .
 - Let V_2 be the potential difference between the spheres with (a_2, b) .
 - What is the relationship between the absolute value of V_1 and V_2 ?



(a) $V_1 < V_2$

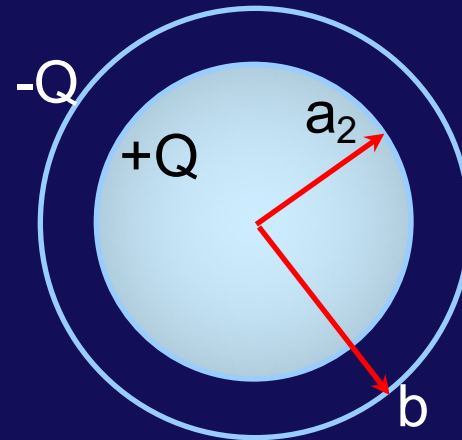

(b) $V_1 = V_2$



(c) $V_1 > V_2$

- Two spherical capacitors.
- Intuition: for parallel plate capacitors: $V = (Q/C) = (Qd)/(A\epsilon_0)$.
Therefore you might expect that $V_1 > V_2$ since $(b-a_1) > (b-a_2)$.
- In fact this is the case as we can show directly from the definition of V !

Follow up


Compute V_1 from E (let $V_b = 0$)
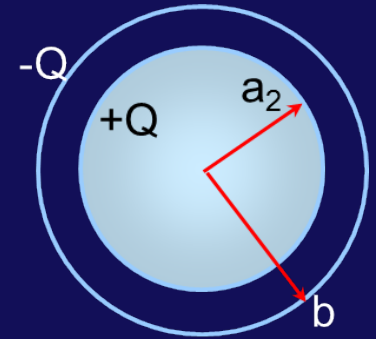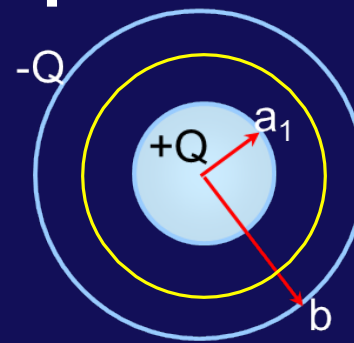
$$V_1 = -\int_b^{a_1} E(r) dr = \int_{a_1}^{a_2} E(r) dr + \int_{a_2}^b E(r) dr$$



Since $E(r)$ has the same form for $r > a_2$,

$$V_1 = \int_{a_1}^{a_2} E(r) dr + V_2$$

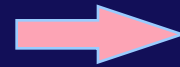

$$(c) V_1 > V_2$$


(Abs. value)

The actual functional form for the spherical capacitor:


$$V = -\int_b^a E(r) dr = -\frac{Q}{4\pi\epsilon_0} \int_b^a \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{r} \right]_b^a = \frac{Q}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{b} \right)$$

$$C \equiv \frac{Q}{V} = \frac{4\pi\epsilon_0}{\left(\frac{1}{a} - \frac{1}{b} \right)} = 4\pi\epsilon_0 \frac{ab}{b-a}$$

Capacitors in Parallel

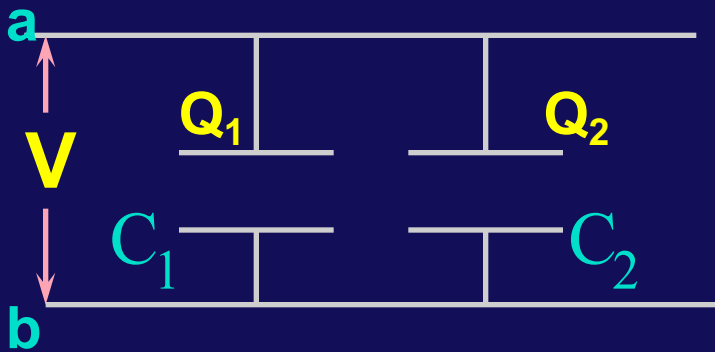

Q

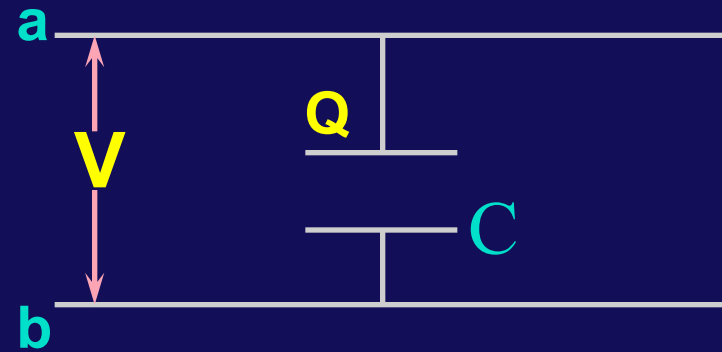

- Find “equivalent” capacitance C

Parallel Combination:

$$V = \frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

Equivalent Capacitor:


p

$$C \equiv \frac{Q}{V} = \frac{Q_1 + Q_2}{V} = \frac{C_1 V + C_2 V}{V}$$

p

$$C = C_1 + C_2$$

Parallel Capacitor Circuit

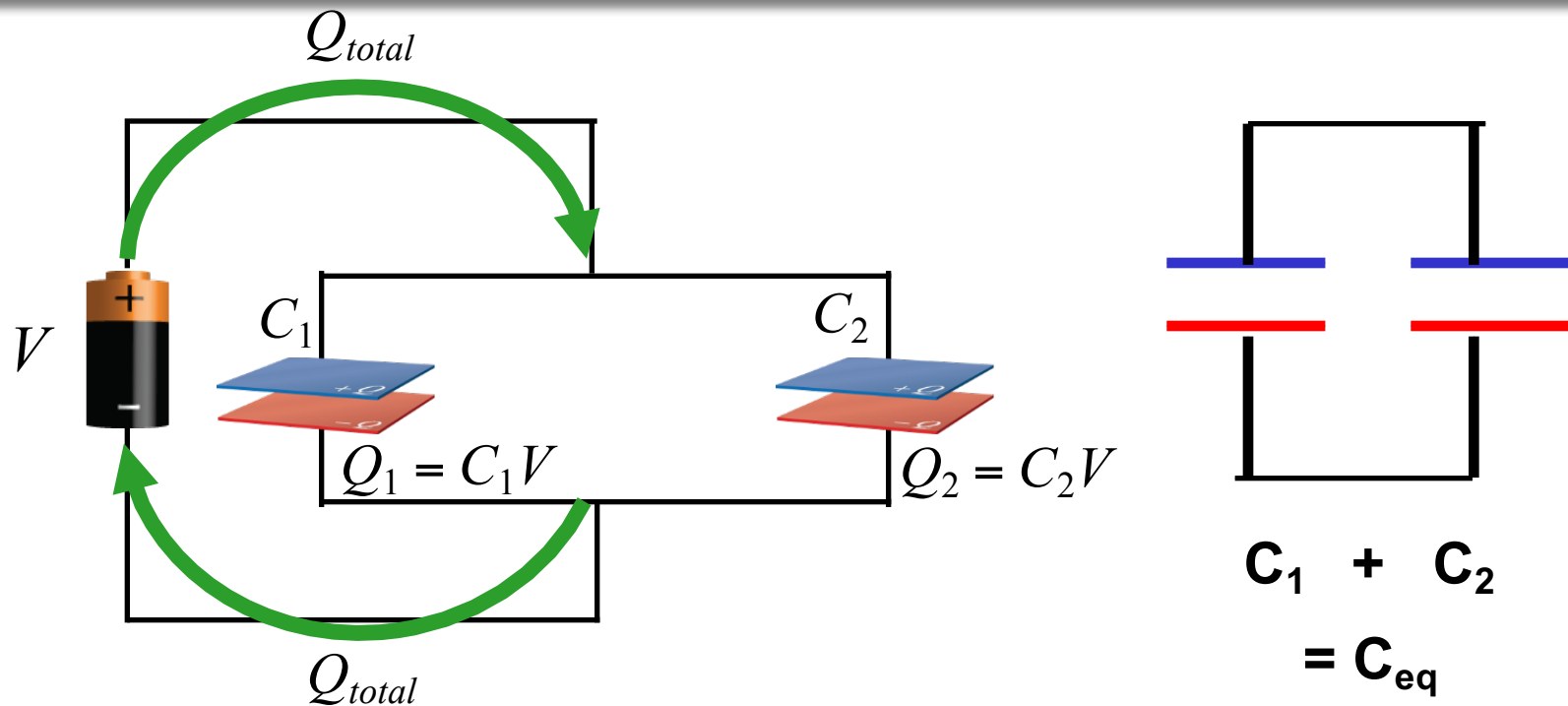


Key point: V is the same for both capacitors

Key Point: $Q_{total} = Q_1 + Q_2 = VC_1 + VC_2 = V(C_1 + C_2)$

$$C_{total} = C_1 + C_2$$

Capacitors in Series

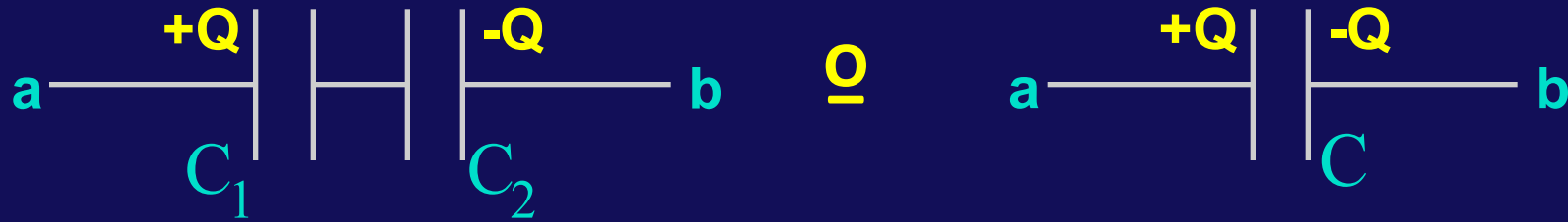

- Find “equivalent” capacitance C
- Charge on C_1 same as charge on C_2
 - since applying a potential difference across ab cannot produce a net charge on the inner plates of C_1 and C_2 .


RHS: $V_{ab} = \frac{Q}{C}$

LHS: $V_{ab} = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2}$

p

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

Examples: Combinations of Capacitors

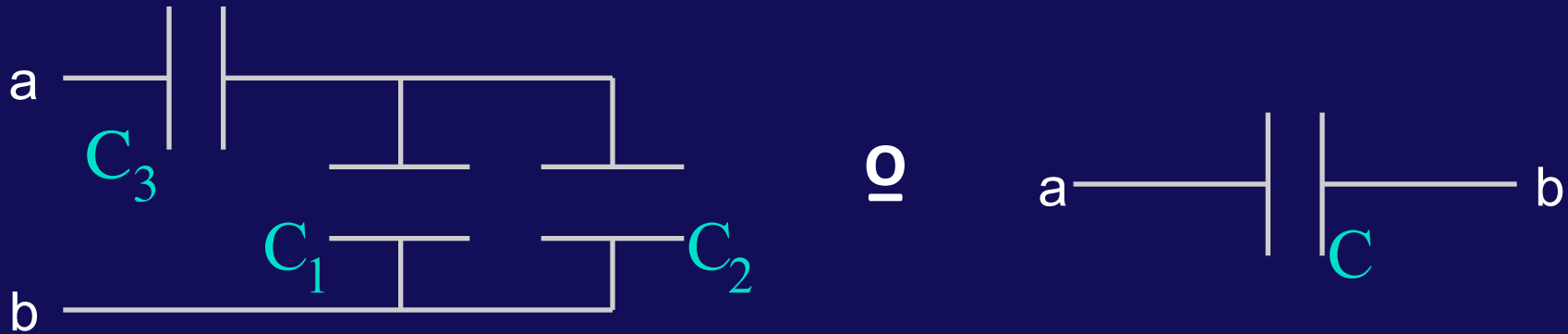

Note: C_3 is in series with the parallel combination on C_1 and C_2 . *i.e.*

$$\frac{1}{C} = \frac{1}{C_3} + \frac{1}{C_1 + C_2}$$

p

$$C = \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3}$$

PreLecture Trouble ... (click)


Suppose you have two identical capacitors, each having capacitance C . C_{\max} is the biggest possible equivalent capacitance that can be made by combining these two, and C_{\min} is the smallest.

How does C_{\max} compare to C_{\min} ?

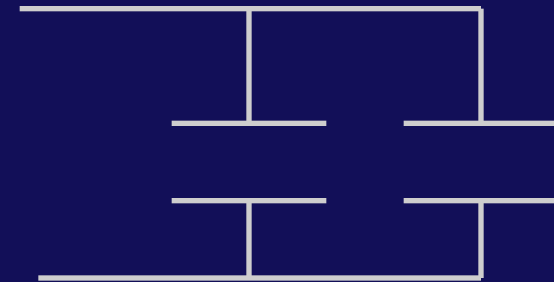- A. $C_{\max} = 4C_{\min}$
- B. $C_{\max} = 3C_{\min}$
- C. $C_{\max} = 2C_{\min}$
- D. $C_{\max} = (3/2)C_{\min}$
- E. $C_{\max} = C_{\min}$



$$\frac{1}{C_{\min}} = \frac{1}{C} + \frac{1}{C} \Rightarrow C/2$$




$$C_{\max} = C_1 + C_2 = 2C$$

$$C_{\max} / C_{\min} = 4$$

Checkpoint difficulty



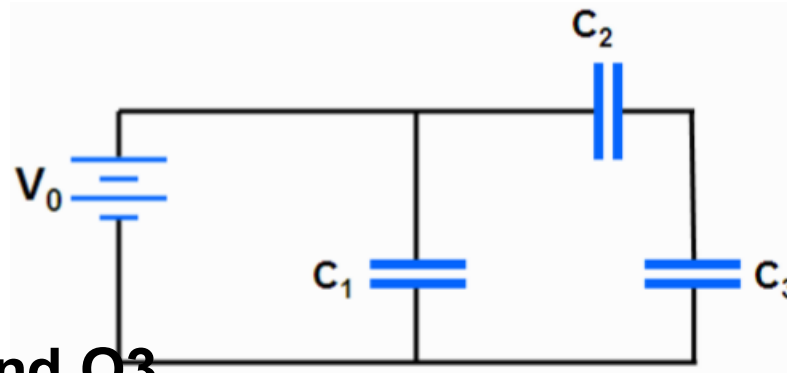A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .




Compare Q_1 , Q_2 , and Q_3 .

- $Q_1 > Q_3 > Q_2$
- $Q_1 > Q_2 > Q_3$
- $Q_1 > Q_2 = Q_3$
- $Q_1 = Q_2 = Q_3$
- $Q_1 < Q_2 = Q_3$

Great response

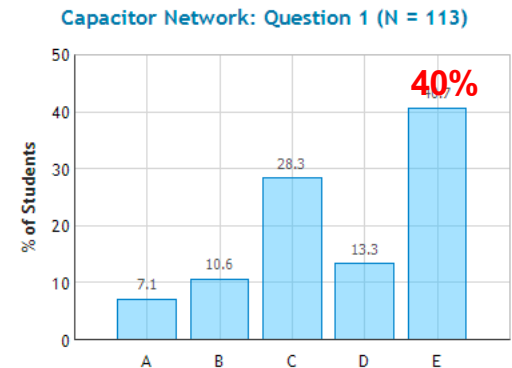
Q_2 and Q_3 will be the same since C_2 and C_3 are in series. The capacitance of the series C_2 and C_3 is 1.2 times the capacitance of C_1 . V_0 voltage will be running through the two parallel branches, so C_1 will have less charge than C_2 and C_3 because C_2 and C_3 have a combined capacitance of $1.2C$, where C is the capacitance of C_1 .



Checkpoint difficulty



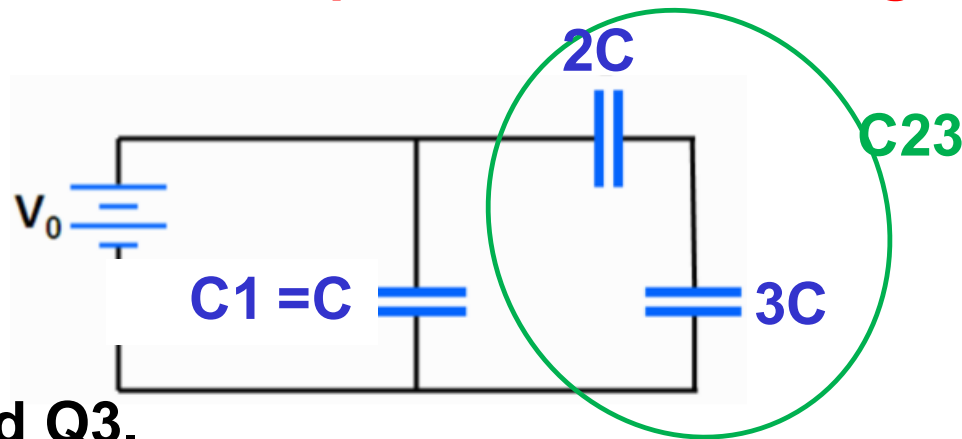A circuit consists of three unequal capacitors C_1 , C_2 , and C_3 which are connected to a battery of voltage V_0 . The capacitance of C_2 is twice that of C_1 . The capacitance of C_3 is three times that of C_1 . The capacitors obtain charges Q_1 , Q_2 , and Q_3 .




Compare Q_1 , Q_2 , and Q_3 .

- $Q_1 > Q_3 > Q_2$
- $Q_1 > Q_2 > Q_3$
- $Q_1 > Q_2 = Q_3$
- $Q_1 = Q_2 = Q_3$
- $Q_1 < Q_2 = Q_3$

- $V_0 = V_{C_1} = V_{C_{23}}$
- Which is larger? C_1 or C_{23} ?
- $C_{23} = \left(\frac{1}{2C} + \frac{1}{3C}\right)^{-1} = \frac{6}{5}C$ SO, $C_{23} > C_1$
- Recall $Q_2 = Q_3$ for series capacitors = Q_{23}
- $Q = CV$
- V 's the same, so $Q_{23} > Q_1$ since $C_{23} > C_1$

Clicker

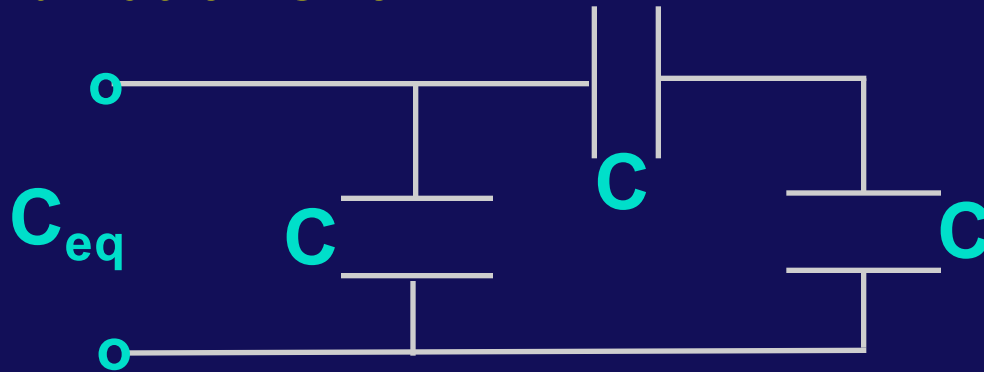What is the equivalent capacitance, C_{eq} , of the combination shown?




(a) $C_{eq} = (3/2)C$

(b) $C_{eq} = (2/3)C$

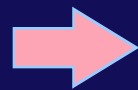
(c) $C_{eq} = 3C$



$$\frac{1}{C_1} = \frac{1}{C} + \frac{1}{C}$$




$$C_1 = \frac{C}{2}$$

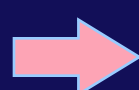

$$C_{eq} = C + \frac{C}{2} = \frac{3}{2}C$$

Similar to CheckPoint

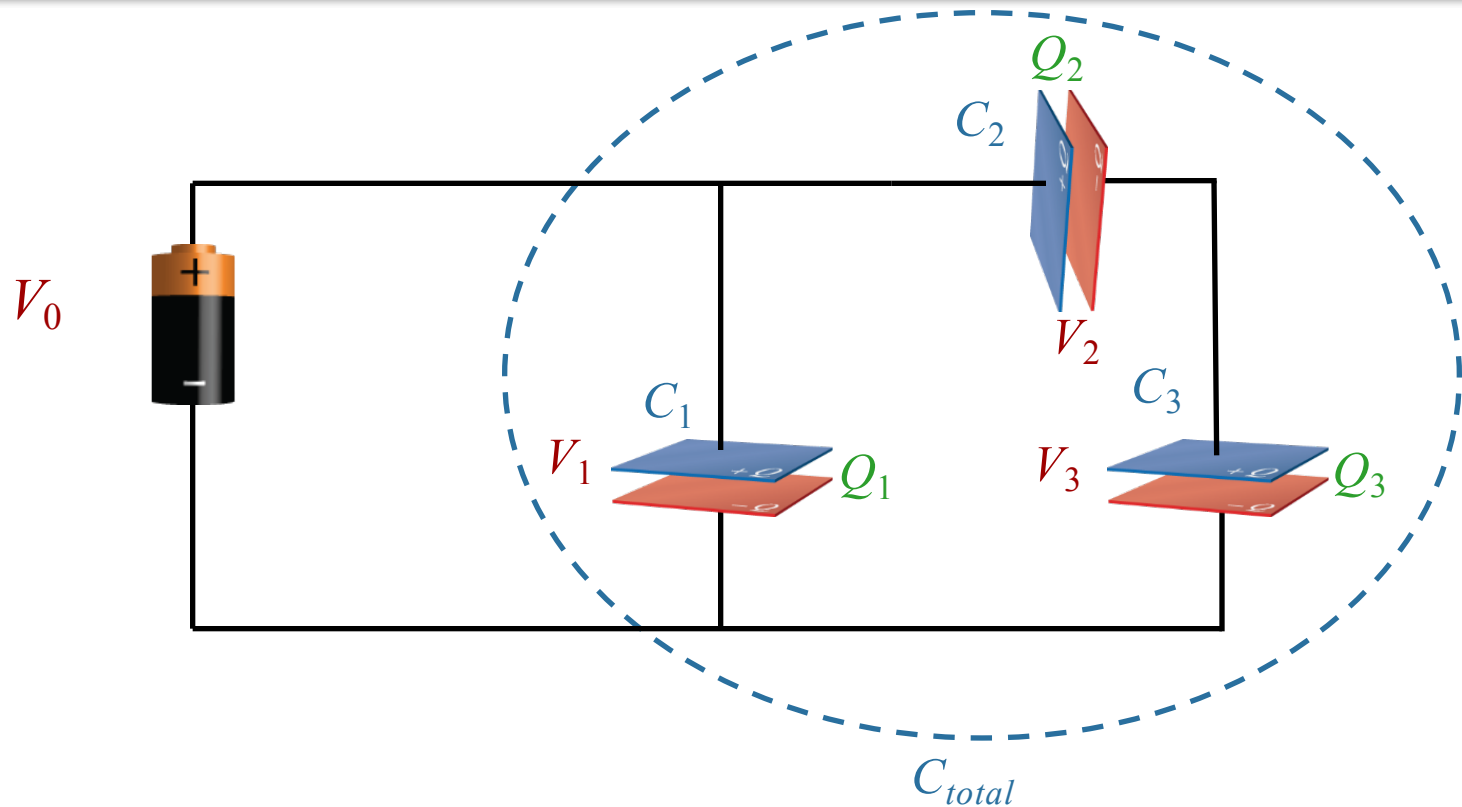

Which of the following is **NOT** necessarily true:

- A) $V_0 = V_1$
- B) $C_{total} > C_1$
- C) $V_2 = V_3$
- D) $Q_2 = Q_3$
- E) $V_1 = V_2 + V_3$