
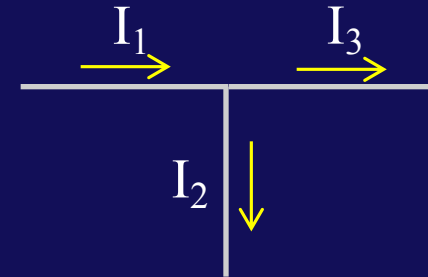


# Kirchoff Loop Laws ...

**Rule 1:** “What goes in, must go out “

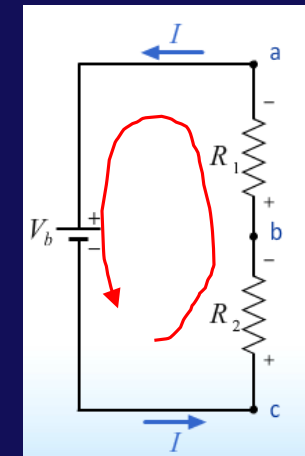

**Rule 2:** “What goes up, must come down”




# Business...

- Exam next Thursday !
- Material is everything through TODAY.
  - No RC circuits that we will cover Monday
- Practice exam and Eqn. posted on home page after lecture
- Try the SmartPhysics HOMEWORK this week on today's lessons. Very good practice for multi-loop problems and a very pedagogical example

Can we solve this from simple series and parallel combinations?


Answer: *no*

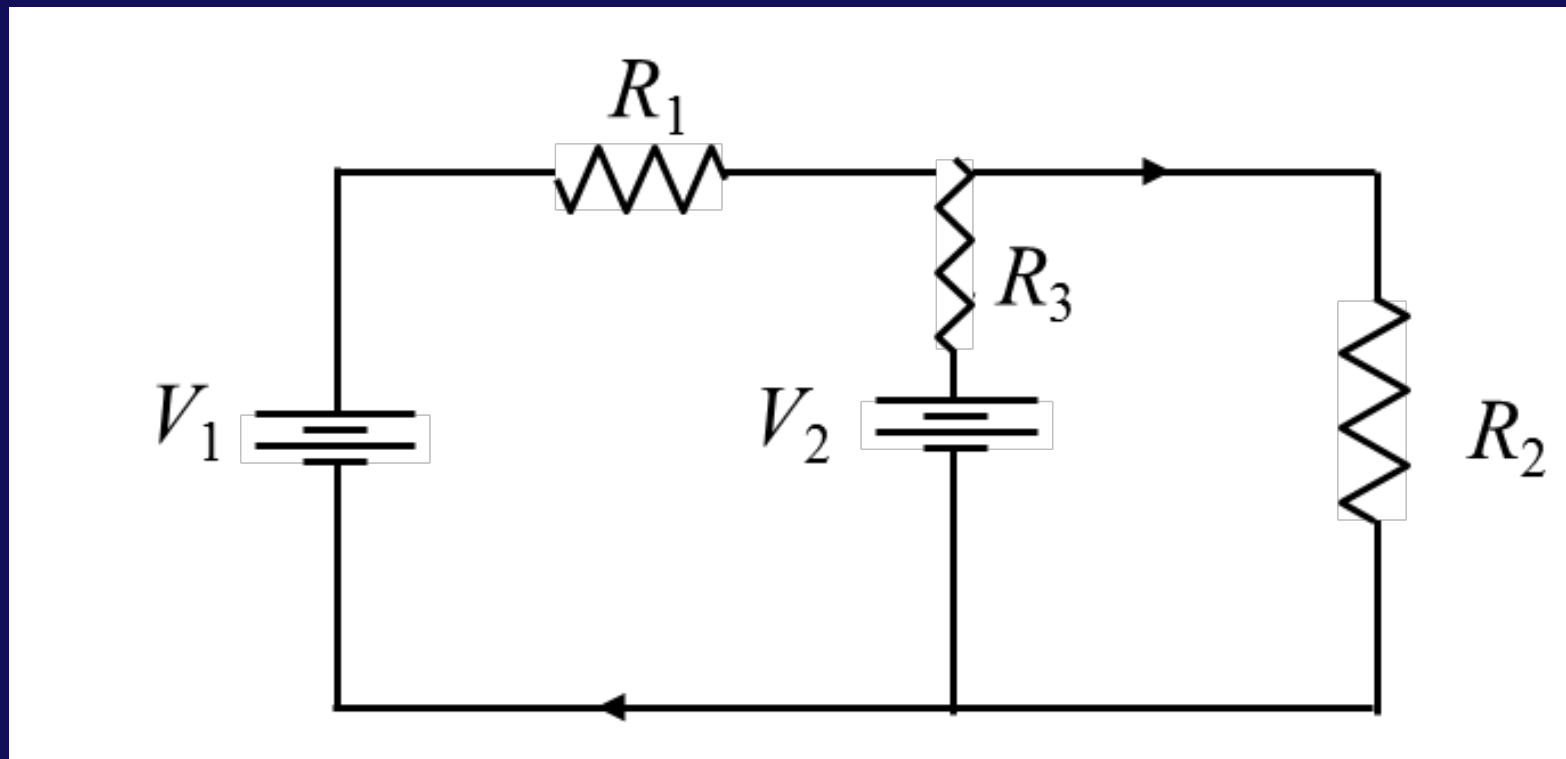

# Kirchoff Voltage Law: **KVL**

"When any closed circuit loop is traversed, the algebraic sum of the changes in potential must equal zero."

**KVL:** 
$$\sum_{loop} V_n = 0$$

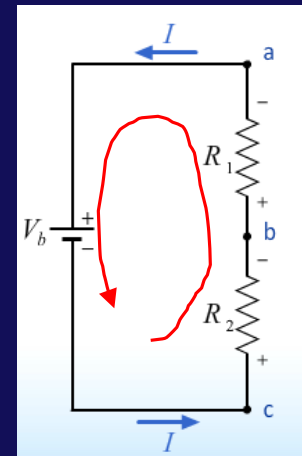

- This is just a restatement of what you already know: that the potential difference is independent of path!


We will follow the ECE conventions: (engineering)  
voltage drops enter with a **+ sign** and  
voltage gains enter with a **- sign** in this equation.

Let's go clockwise around circuit:



# This resistor labyrinth stuff is crazy! CheckPoint

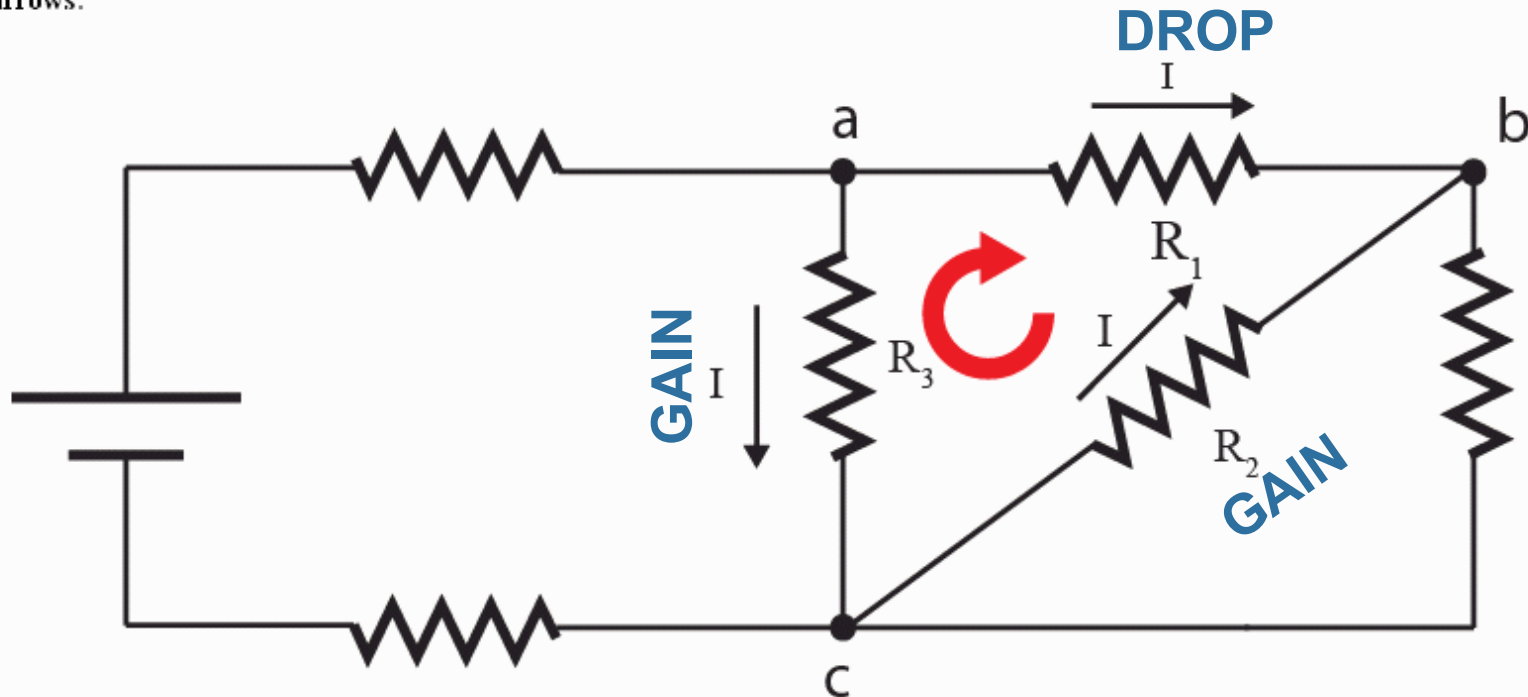5) In the following circuit, consider the loop abc. The direction of the current through each resistor is indicated by black arrows.




If we are to write Kirchoff's voltage equation for this loop in clockwise direction starting from point a, what is the correct order of voltage gains/drops that we'll encounter for resistors R1, R2 and R3?

- A drop, drop, drop
- B gain, gain, gain
- C drop, gain, gain
- D gain, drop, drop
- E drop, drop, gain
- other

With the current  VOLTAGE DROP  
Against the current  VOLTAGE GAIN

# Examine this loop

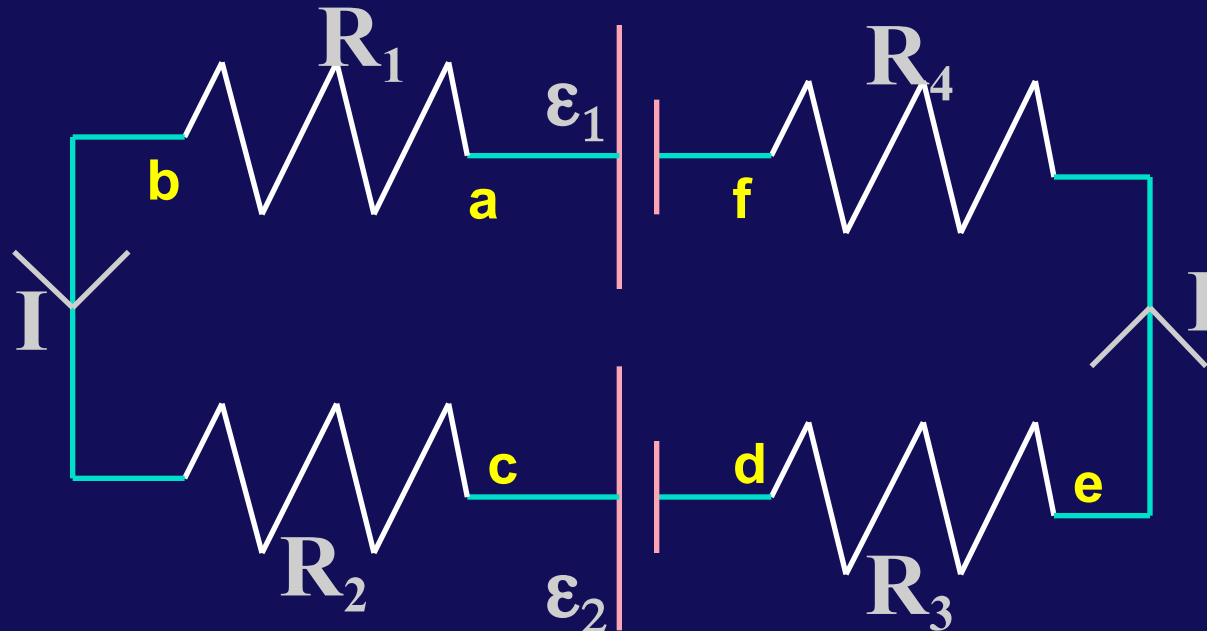

Let's go around the loop counterclockwise from a to f

**KVL:**  $\sum_{\text{loop}} V_n = 0$     $\Downarrow$     $IR_1 + IR_2 + \varepsilon_2 + IR_3 + IR_4 - \varepsilon_1 = 0$

$\Downarrow$

$$I = \frac{\varepsilon_1 - \varepsilon_2}{R_1 + R_2 + R_3 + R_4}$$


# Clicker

- Consider the circuit shown.
  - The switch is initially open and the current flowing through the bottom resistor is  $I_0$ .
  - After the switch is closed, the current flowing through the bottom resistor is  $I_1$ .
  - What is the relation between  $I_0$  and  $I_1$ ?

(a)  $I_1 < I_0$

(b)  $I_1 = I_0$

(c)  $I_1 > I_0$

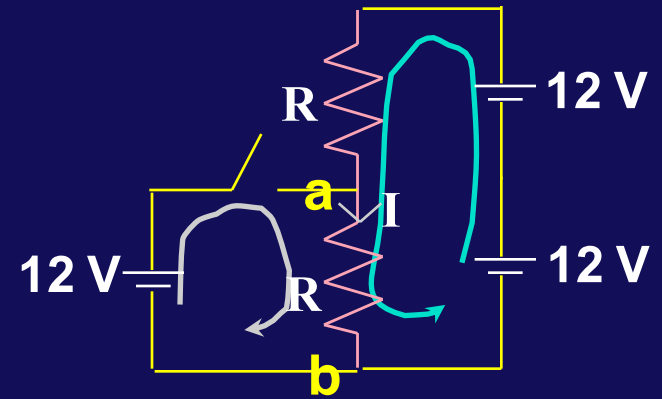

- Write a loop law for original loop:

$$-12V -12V + I_0R + I_0R = 0$$

$$I_0 = 12V/R$$

- Write a loop law for the new loop:


$$-12V + I_1R = 0$$

$$I_1 = 12V/R$$
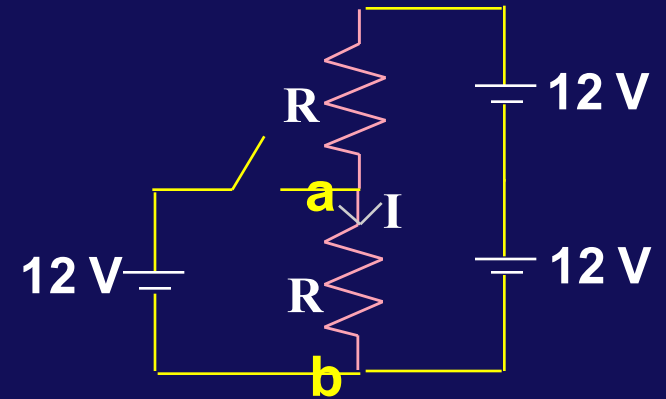
## ...or, alternative reasoning

- **Consider the circuit shown.**

- The switch is initially open and the current flowing through the bottom resistor is  $I_0$ .
- After the switch is closed, the current flowing through the bottom resistor is  $I_1$ .
- What is the relation between  $I_0$  and  $I_1$ ?



(a)  $I_1 < I_0$

(b)  $I_1 = I_0$

(c)  $I_1 > I_0$

- **The key here is to determine the potential ( $V_a - V_b$ ) before the switch is closed.**
- **From symmetry,  $(V_a - V_b) = +12V$ .**
- **Therefore, when the switch is closed, NO additional current will flow!**
- **Therefore, the current before the switch is closed is equal to the current after the switch is closed.**




# Kirchoff's Current Law: **KCL**

## Conservation of Charge (at a junction)



"At any junction point in a circuit where the current can divide (also called a node), the sum of the currents into the node must equal the sum of the currents out of the node."

$$I_{in} = \sum I_{out}$$

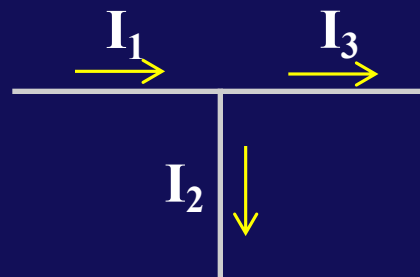

# CheckPoint

4) Consider the circuit shown below.

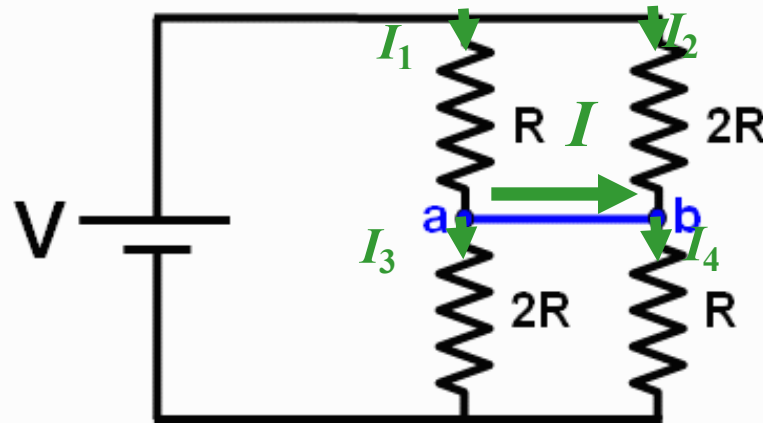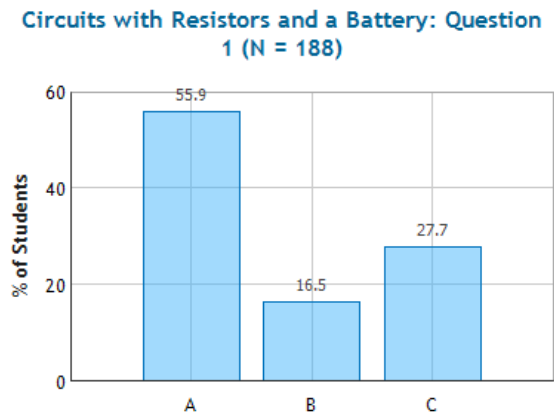

Which of the following statements best describes the current flowing in the blue wire connecting points a and b?


- Positive current flows from a to b
  Positive current flows from b to a
  No current flows between a and b

Wire connects **a** to **b**;  $\Delta V$  through R and 2R to **a/b** is  $V/2$ . (symmetry from below); Therefore:  $I_1 R = I_2 2R = V/2$ ;  $I_1 = V/2R$   
(twice as much current goes down the left)


From **a/b** to bottom of circuit,  $\Delta V/2$  as well;  $I_3 2R = I_4 R = V/2$ ;  $I_3 = V/4R$   
(twice as much current down right side)

Junction Rule at **a**:  $I_1 = I_{ab} + I_3 \rightarrow V/(2R) = I_{ab} + V/(4R) \rightarrow I_{ab}$  is positive

# Prelecture

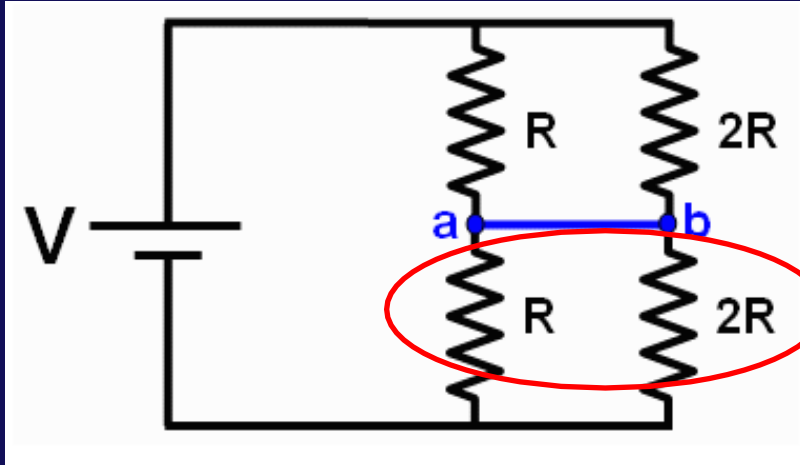


# CheckPoint

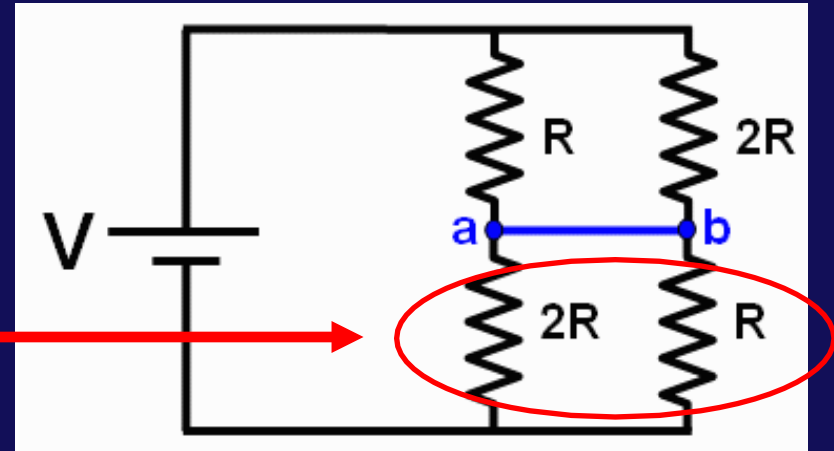

What is the same?


Equivalent resistance is the same.

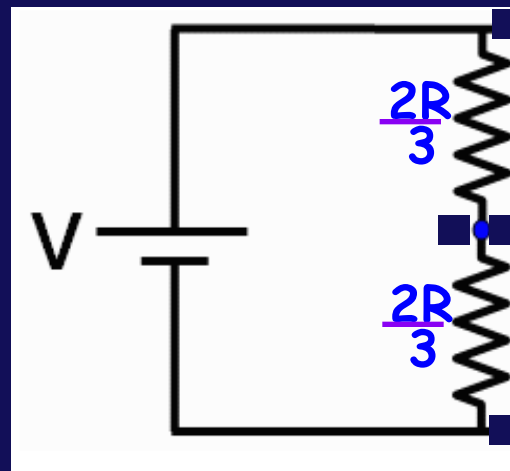Current flowing in and out of the battery.




What is different?

Current flowing from **a** to **b**.

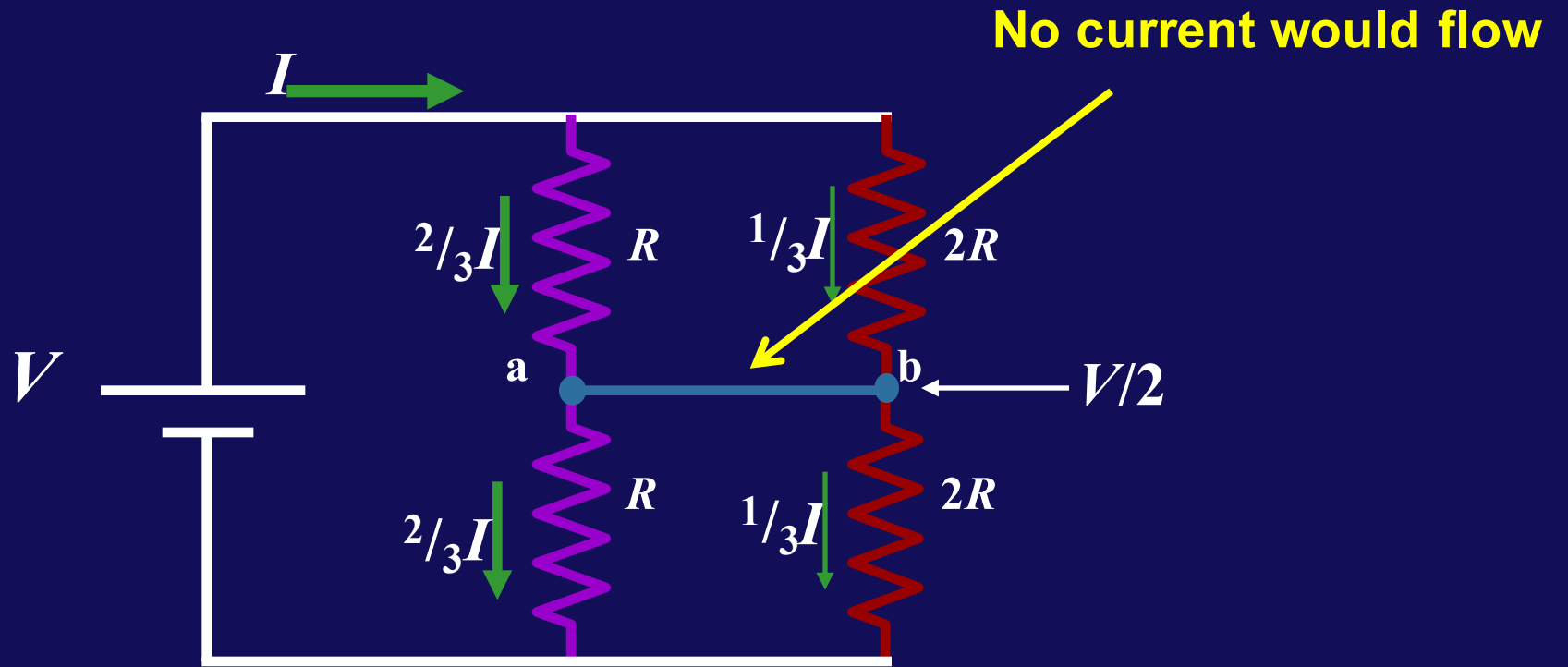


Current  $1/3 I$  will flow

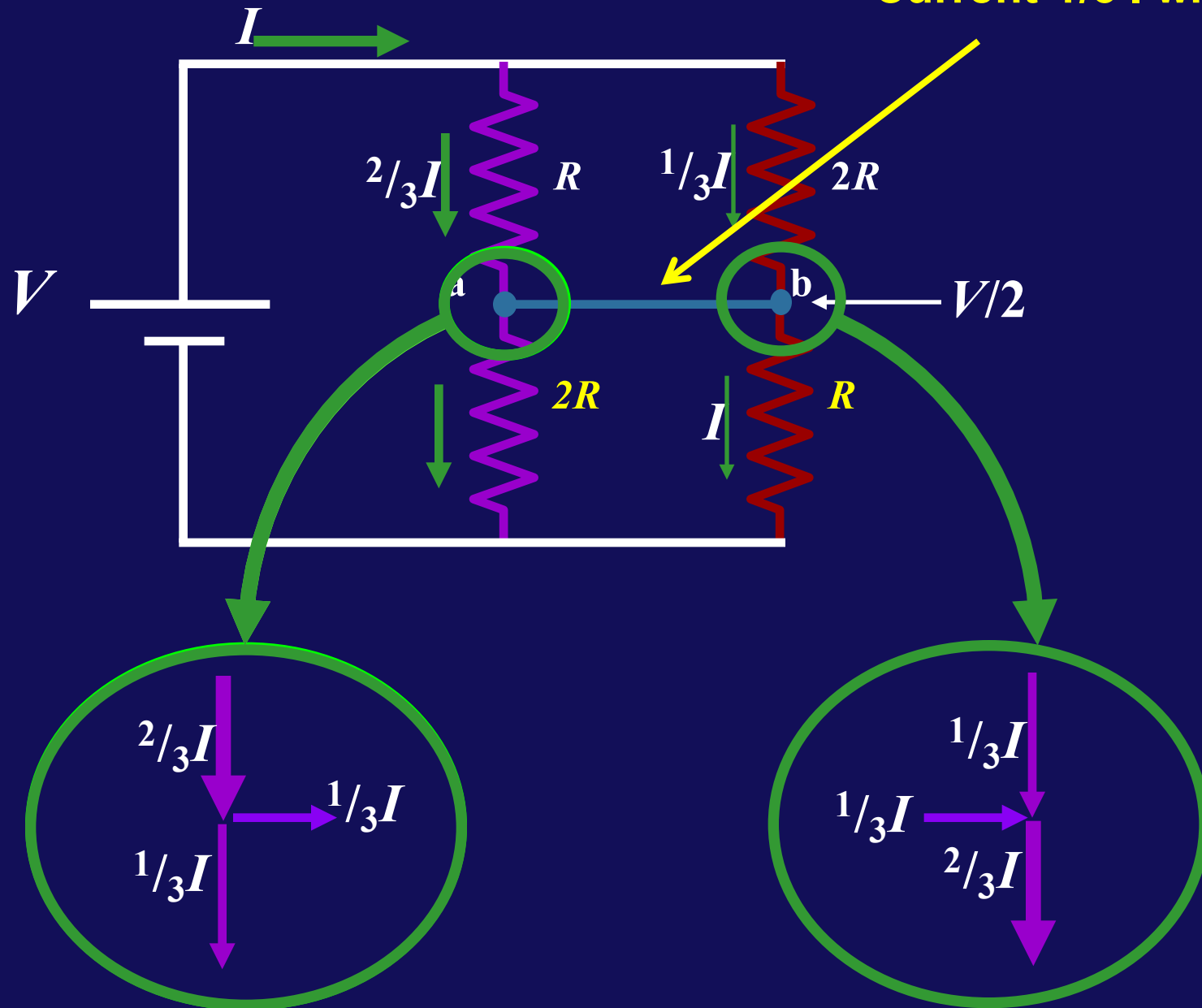

# Have a look at this if you missed it. Some reasoning below ...

7) Consider the circuit shown below.

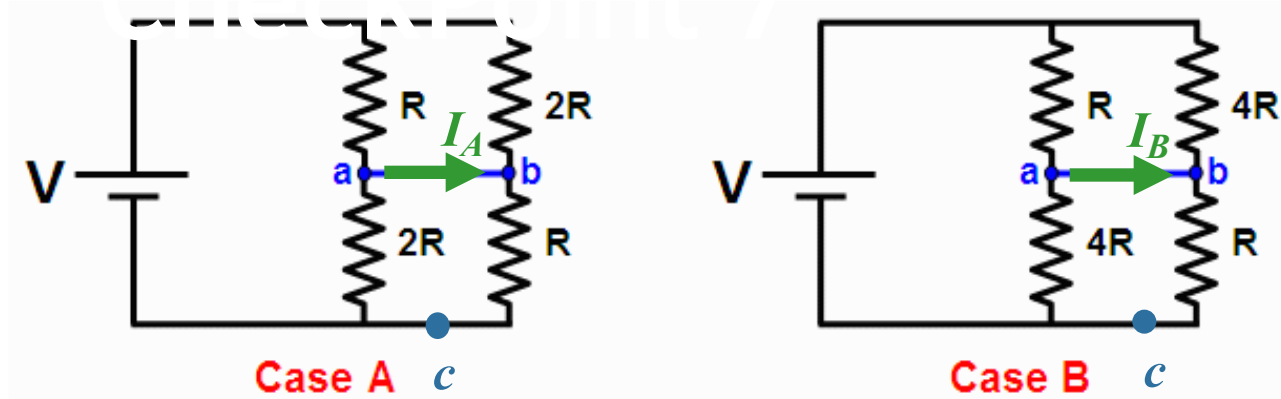

In which case is the current flowing in the blue wire connecting points a and b biggest

- Case A 
  Case B 
  They are the same

Current will flow from left to right in both cases.

In both cases,  $V_{ac} = V/2$




$$I_{2R} = 2I_{4R}$$

$$\begin{aligned}
 I_A &= I_R - I_{2R} \\
 &= I_R - 2I_{4R}
 \end{aligned}$$

$$I_B = I_R - I_{4R}$$

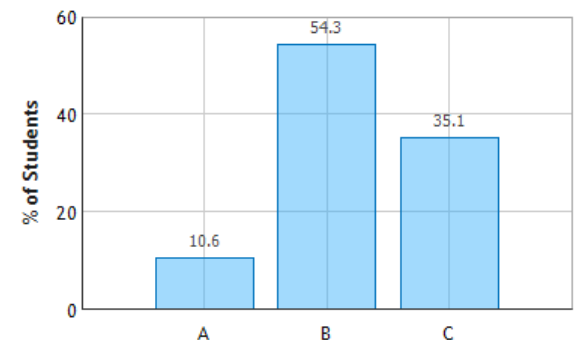Circuits with Resistors and a Battery: Question 3 (N = 188)



# Analysis of a circuit

Junction:


$$I_1 = I_2 + I_3$$

Outside loop:

$$I_1R + I_3R + \varepsilon_3 - \varepsilon_1 = 0$$

Top loop:
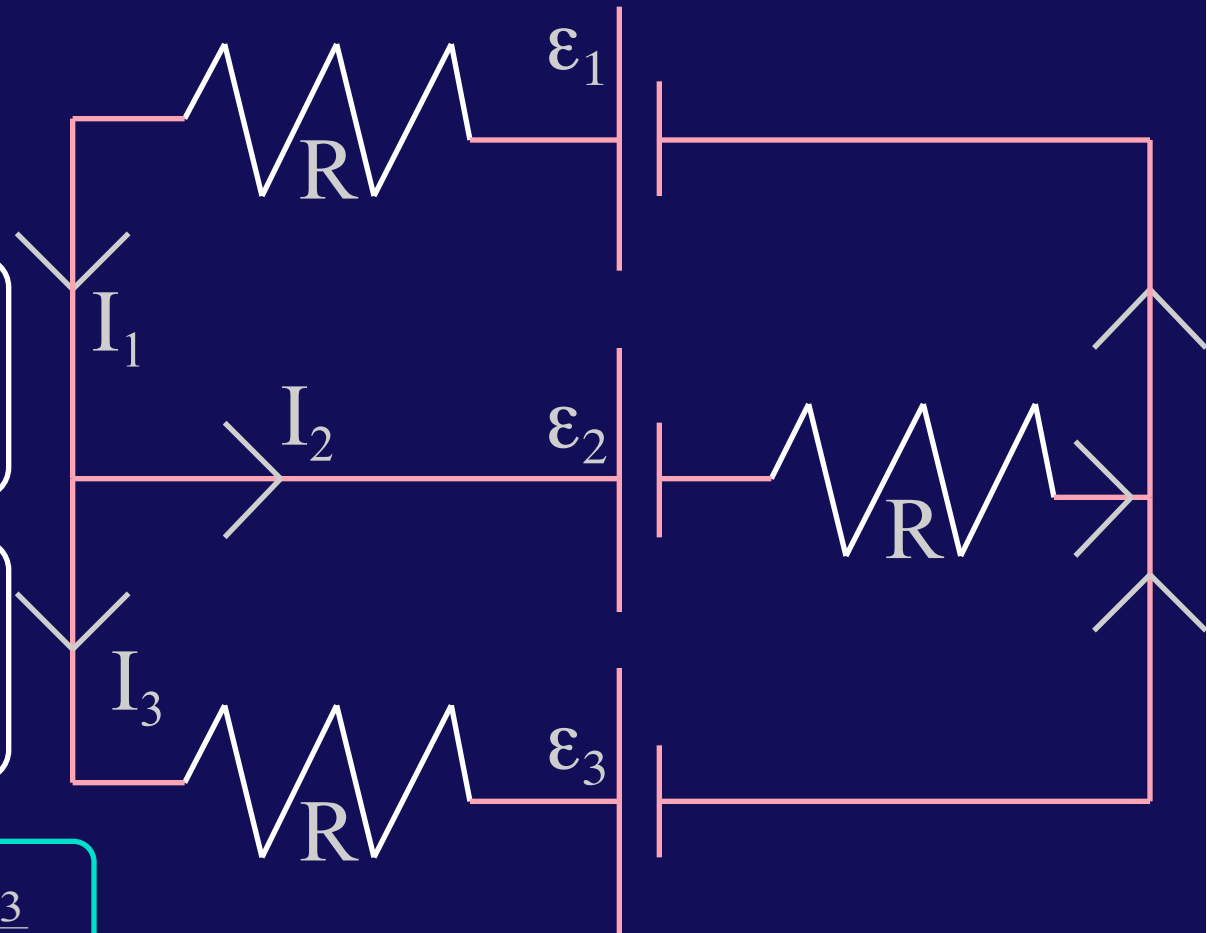
$$I_1R + \varepsilon_2 + I_2R - \varepsilon_1 = 0$$



$$I_1 = \frac{2\varepsilon_1 - \varepsilon_2 - \varepsilon_3}{3R}$$

$$I_3 = \frac{\varepsilon_1 + \varepsilon_2 - 2\varepsilon_3}{3R}$$

$$I_2 = \frac{\varepsilon_1 + \varepsilon_3 - 2\varepsilon_2}{3R}$$

**No getting around it  
3 equations/3 unknowns typically**

# Clicker


Consider the circuit shown:

– What is the relation between  $V_a - V_d$  and  $V_a - V_c$  ?

(a)  $(V_a - V_d) < (V_a - V_c)$

(b)  $(V_a - V_d) = (V_a - V_c)$

(c)  $(V_a - V_d) > (V_a - V_c)$

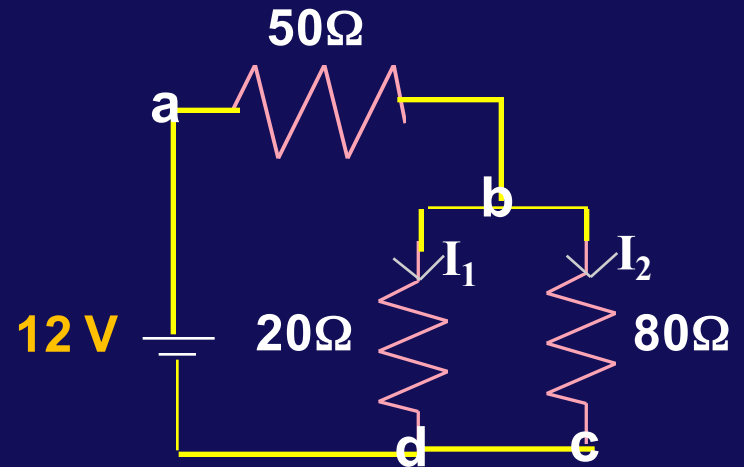

- Remember: potential is independent of path

Going from a to d or c is like going to the same place, electrically


→  $(V_a - V_d) = (V_a - V_c)$


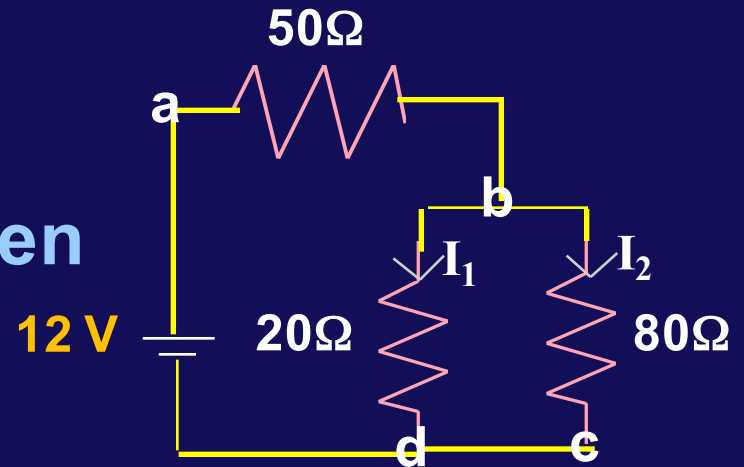
# Clicker

- Consider the circuit shown:

– What is the relation between  $I_1$  and  $I_2$ ?



(a)  $I_1 < I_2$

(b)  $I_1 = I_2$

(c)  $I_1 > I_2$

- Note that:  $V_b - V_d = V_b - V_c$

- Therefore,

$$I_1(20\Omega) = I_2(80\Omega) \quad \Rightarrow \quad I_1 = 4I_2$$