
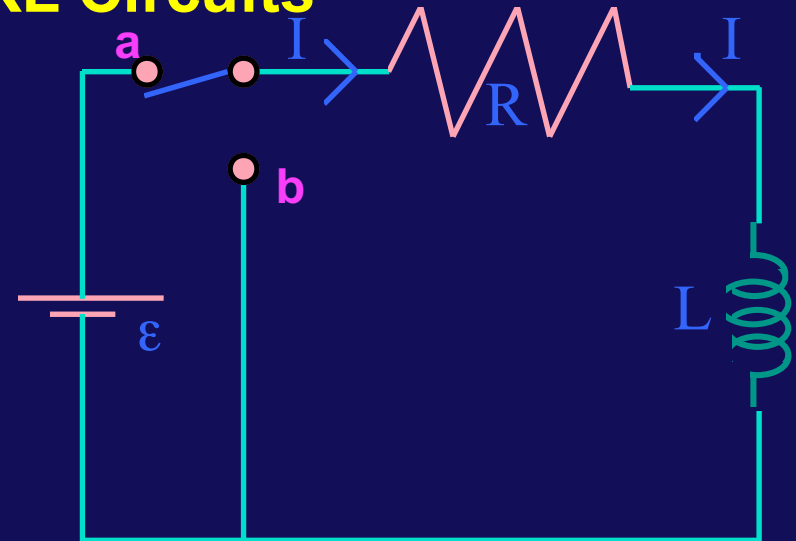



Finish Faraday Introduce: Induction

Self-Inductance, RL Circuits

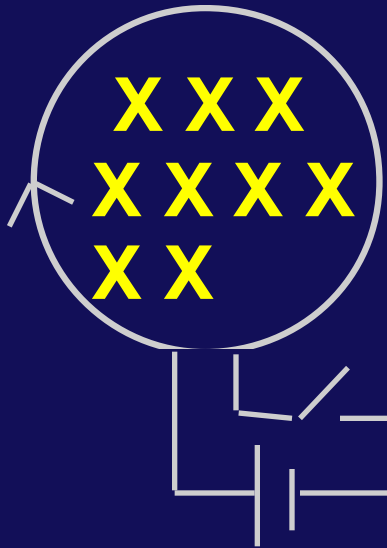

$$L \equiv \frac{\Phi_B}{I}$$

$$L \equiv -\frac{\epsilon}{(dI/dt)}$$

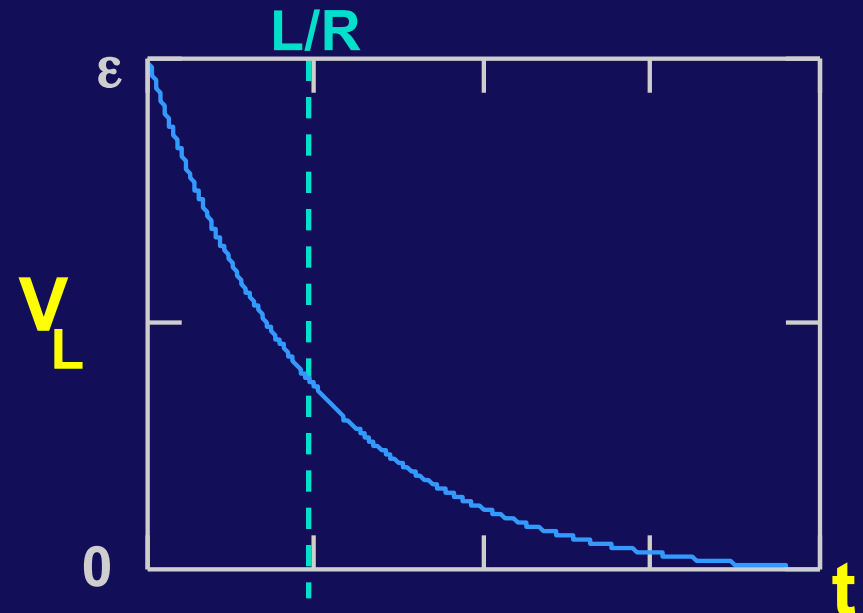


Business

- **Test Next Thursday – will cover through Faraday's & Lenz's law**
- **Practice Exam 3 to go up today, solutions next week**
- **Schedule Change: We'll do LRC Circuits on Monday and exam review on Wednesday (NOTE THIS MEANS FLIPITPHYSICS HAS BEEN MOVED TO MONDAY)**

Last time: Faraday's Law

- Define the flux of the magnetic field through a surface (closed or open) from:
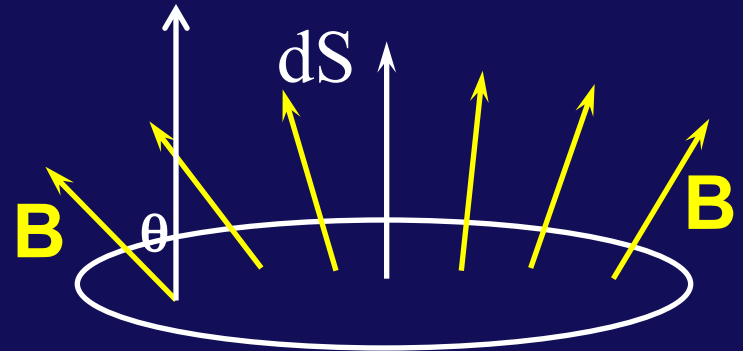
$$\Phi_B \equiv \int \vec{B} \cdot d\vec{S}$$



- Faraday's Law:

The emf induced in a circuit is determined by the time rate of change of the magnetic flux through that circuit.


$$emf = \oint \vec{E} \cdot d\vec{\ell} = - \frac{d\Phi_B}{dt}$$

The minus sign indicates direction of induced current (given by Lenz's Law).

Clicker Part 1

The magnetic field in a region of space of radius $2R$ is aligned with the z -direction and changes in time as shown in the plot.

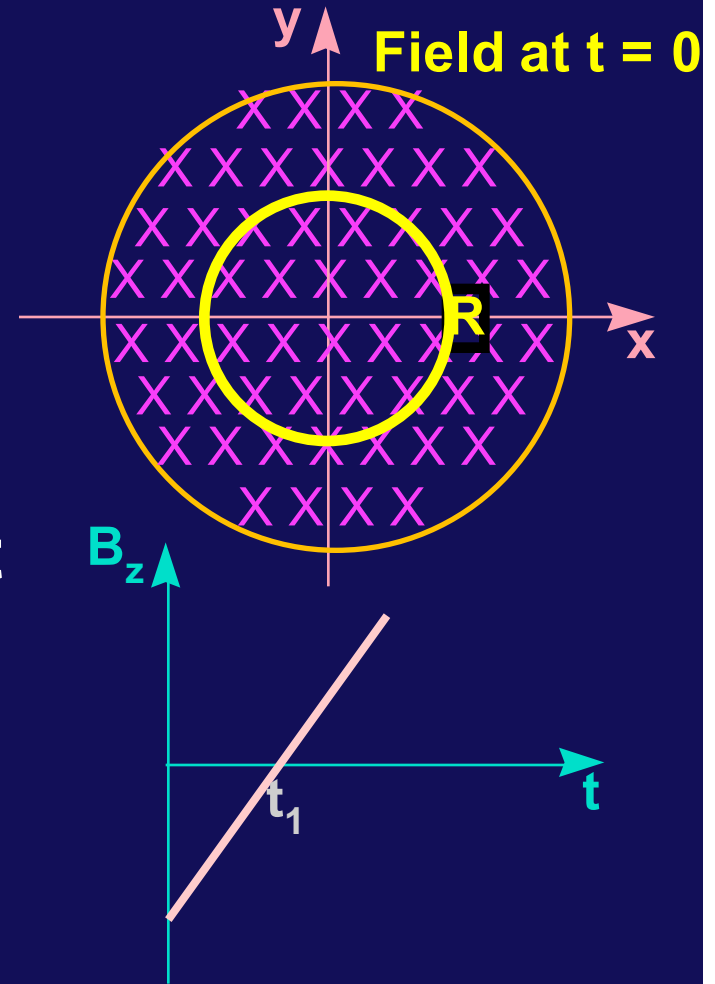Which way would the induced current flow in yellow loop at time $t=t_1$?




- (a) ccw (b) cw (c) No current

Clicker Part 1

The magnetic field in a region of space of radius $2R$ is aligned with the z -direction and changes in time as shown in the plot.

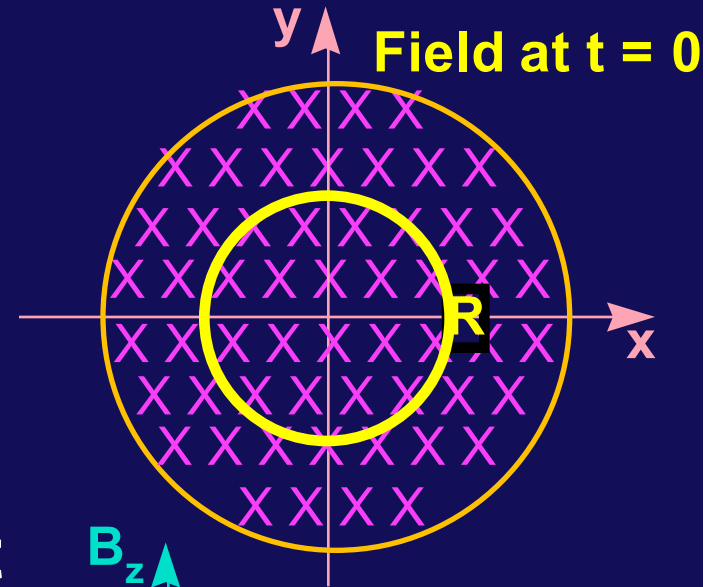Which way would the induced current flow in yellow loop at time $t=t_1$?




- (a) ccw (b) cw (c) No current

$d\Phi/dt > 0$ in $+z$ direction at all times, even at $t = t_1$.


Induced current in direction to create a induced B field in negative z direction

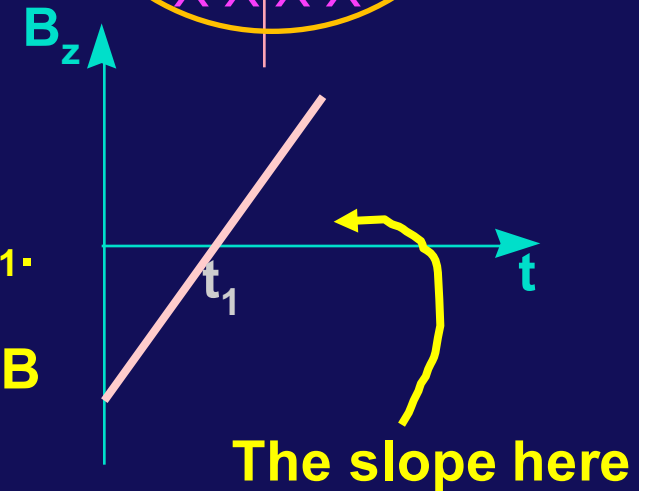Into the page: \rightarrow clockwise current



Clicker Part 2

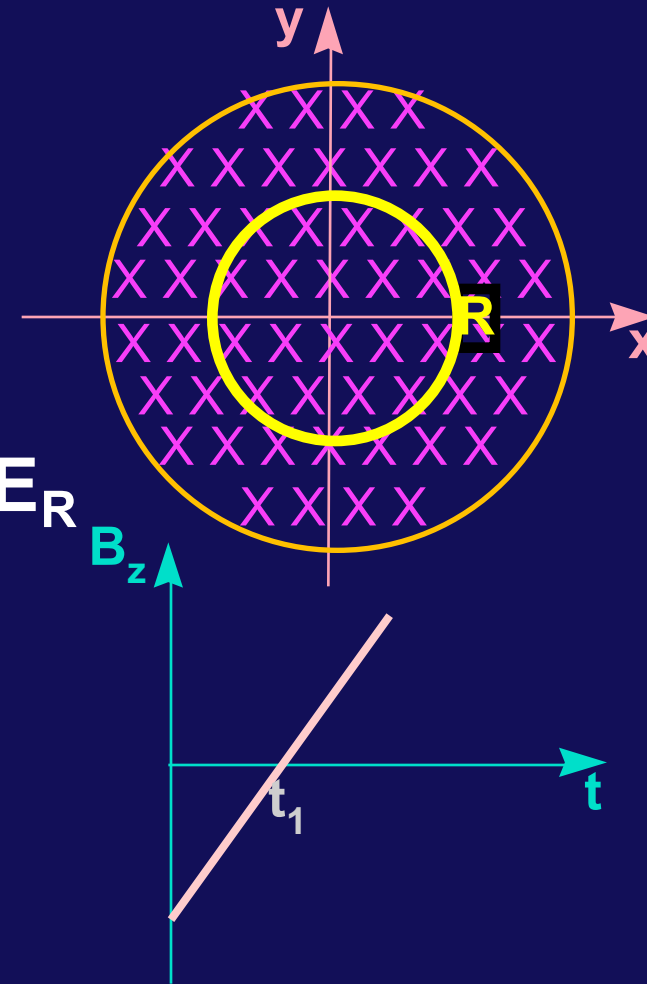What is the relation between the magnitudes of the induced electric fields E_R at radius R and E_{2R} at radius $2R$?



(a) $E_{2R} = E_R$

(b) $E_{2R} = 2E_R$

(c) $E_{2R} = 4E_R$

$$emf = \oint \vec{E} \cdot d\vec{\ell} = -\frac{d\Phi_B}{dt}$$

The rate of change of the flux is proportional to the area: $\frac{d\Phi_B}{dt} = -\pi R^2 \frac{dB}{dt}$


The path integral of the induced electric field is proportional to the radius. $\oint \vec{E} \cdot d\vec{\ell} = E(2\pi R)$

Therefore:

$$E \propto R$$

New: Mutual Inductance

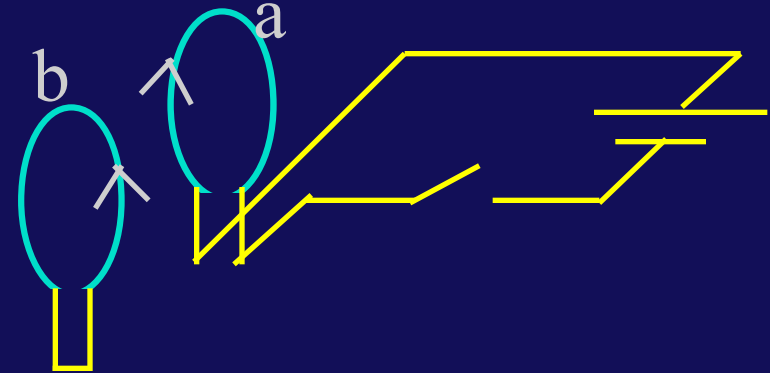- Demo: current is induced in coil b when the current is changed coil a
- Describe in terms of the mutual inductance: M
- Ratio of flux through the loop to current in opposite loop.




$$M \equiv \frac{\Phi_{ab}}{I_b} = \frac{\Phi_{ba}}{I_a}$$

- Note M has this symmetry (not obvious perhaps, but true)
- You can use M as you will use L , the self inductance, in the development which follows.

Meanwhile, what is L ?

Self*-Inductance

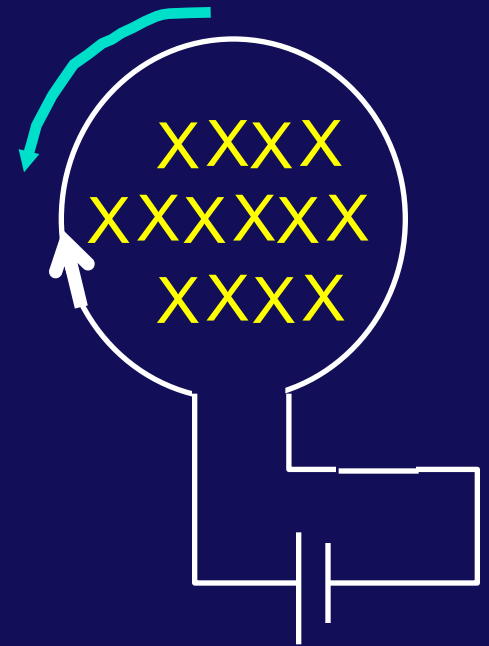- Consider the loop at the right.
 - Switch closed \Rightarrow current starts to flow in the loop.
 - Magnetic field produced in loop.
 - Flux through loop is changing
 - An emf is induced in loop in direction to oppose the initial emf from the battery
- **Self-Induction:** the act of a changing current through a loop inducing an opposing emf in that same loop.




**we will mostly drop the word 'self'*

Defining Self-Inductance

- The magnetic field produced by the current in the loop shown is proportional to that current.

$$B \propto I$$

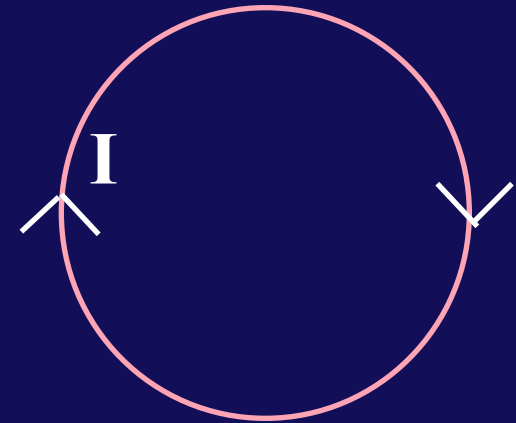

- Flux, is proportional to current.

$$\Phi_B \equiv \int \vec{B} \cdot d\vec{S} \propto I$$

- Define constant of proportionality between Φ and I to be the inductance L .

$$L \equiv \frac{\Phi_B}{I}$$

- Use Faraday's Law, in terms of the emf induced by a changing current,

$$\Phi_B = IL$$
$$\frac{d\Phi_B}{dt} = \frac{dI}{dt} L = -\varepsilon$$



$$\varepsilon = -L \frac{dI}{dt}$$

The inductance is a property of the device

(sound familiar? Recall resistors and capacitors)

- Long Solenoid:

N turns total, radius r, Length l

$$r \ll l \Rightarrow B = \mu_0 \frac{N}{l} I$$

For a single turn:

$$A = \pi r^2 \Rightarrow \phi = BA = \mu_0 \frac{N}{l} IA$$

The total flux through solenoid is given by:

$$\Phi_B = N\phi = \mu_0 \frac{N^2}{l} I\pi r^2 = \mu_0 n^2 lIA$$

Note: $n = N / l$



Inductance of solenoid can then be calculated as:


$$L \equiv \frac{\Phi_B}{I} = \mu_0 \frac{N^2}{l} A = \mu_0 n^2 Al$$

Note: if there are iron cores or other inserts, materials properties enter

What an inductor does ..

emf induced across L tries to keep I constant.

$$\mathcal{E}_L = -L \frac{dI}{dt}$$

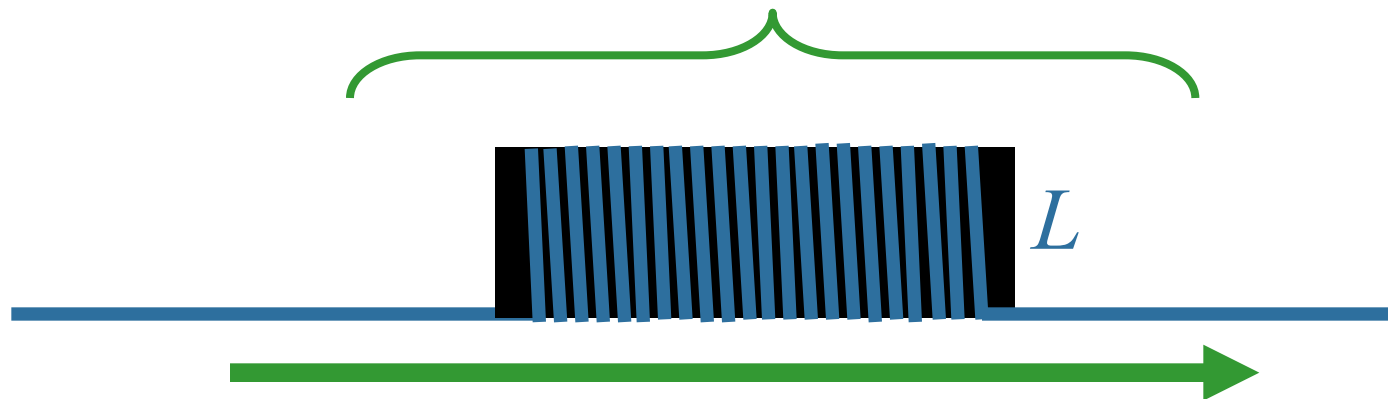

current I through an inductor in a circuit


Inductors prevent discontinuous current changes!

It's like **inertia** for the current

If **no current is flowing**, you can't instantaneously start it

If **current is flowing**, you can't instantaneously stop it

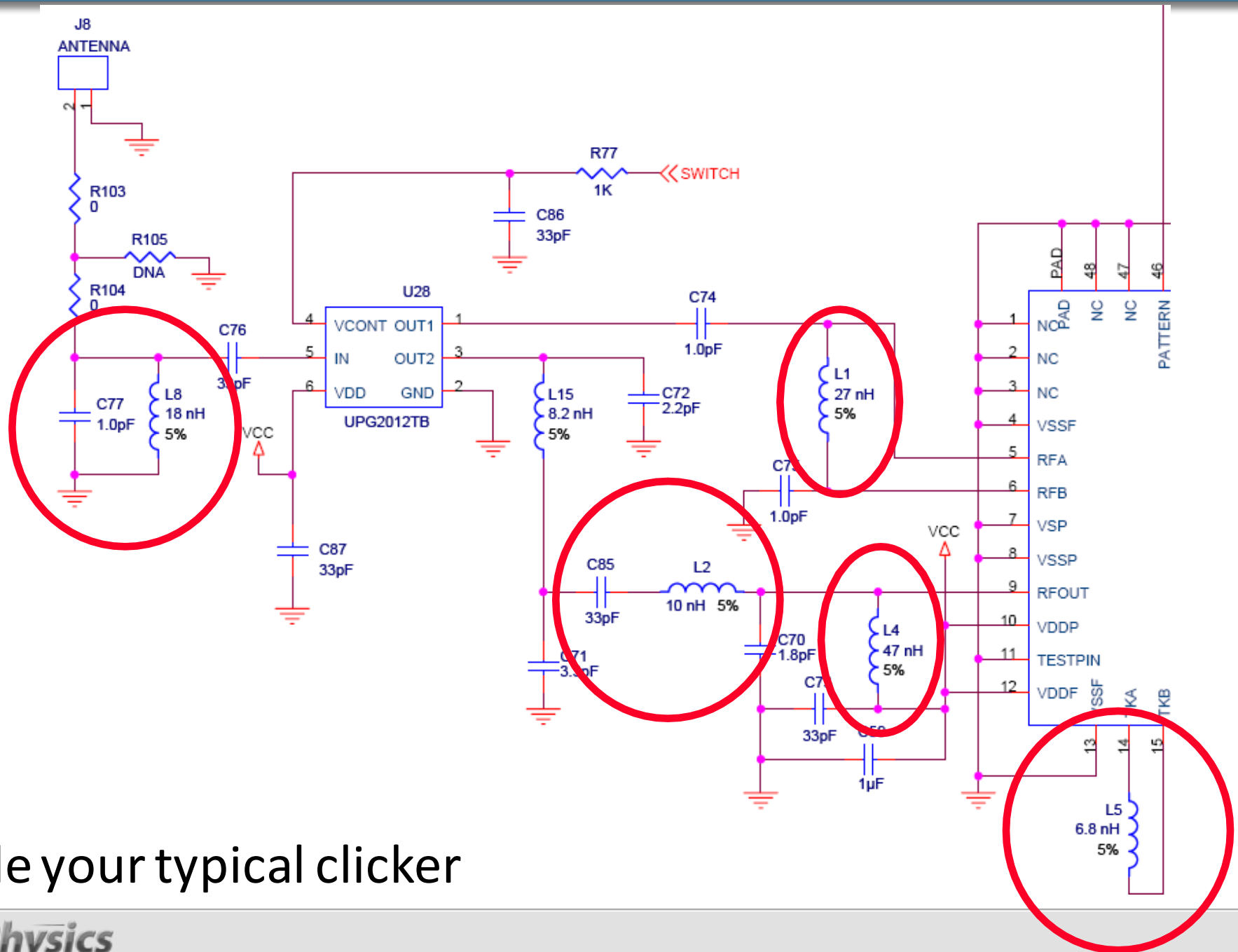What are Inductors and Capacitors Good For?



Inside your typical clicker


Checkpoint 4



In the circuit, the switch has been open for a long time, and the current is zero everywhere.

At time $t = 0$ the switch is closed.

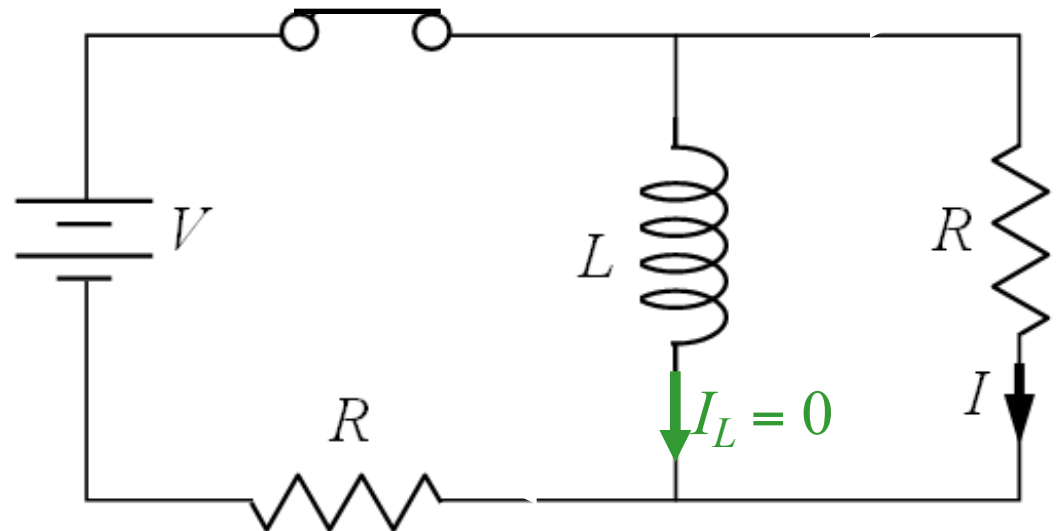What is the current I through the vertical resistor immediately after the switch is closed?



(+ is in the direction of the arrow)

A) $I = V/R$

B) $I = V/2R$

C) $I = 0$

D) $I = -V/2R$


E) $I = -V/R$

Before: $I_L = 0$

After: $I_L = 0$

→ $I = +V/2R$

RL Circuit: Question 1 (N = 194)

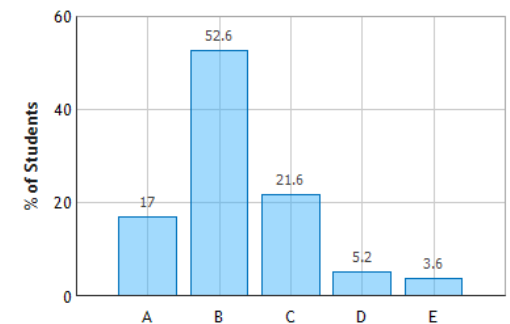

CheckPoint 6




After a long time, the switch is opened, abruptly disconnecting the battery from the circuit.

What is the current I through the vertical resistor immediately after the switch is opened?


(+ is in the direction of the arrow)

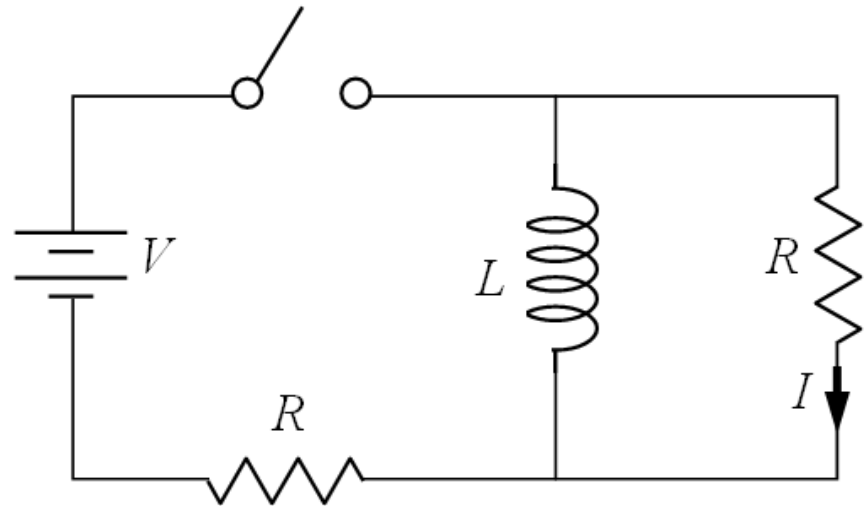- A) $I = V/R$
- B) $I = V/2R$
- C) $I = 0$
- D) $I = -V/2R$
- E) $I = -V/R$**


Current through inductor cannot change
DISCONTINUOUSLY



circuit when switch opened

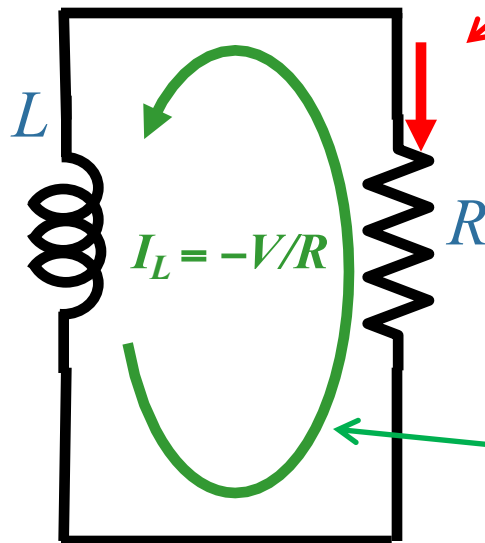


Note, their arrow for I

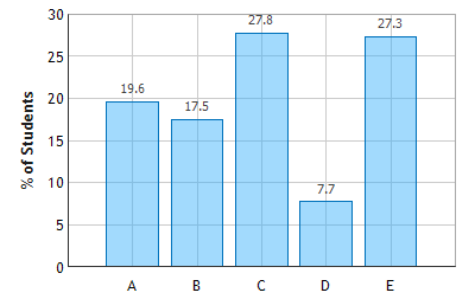

Actual current flow in same direction as before switch opened

RL Circuits

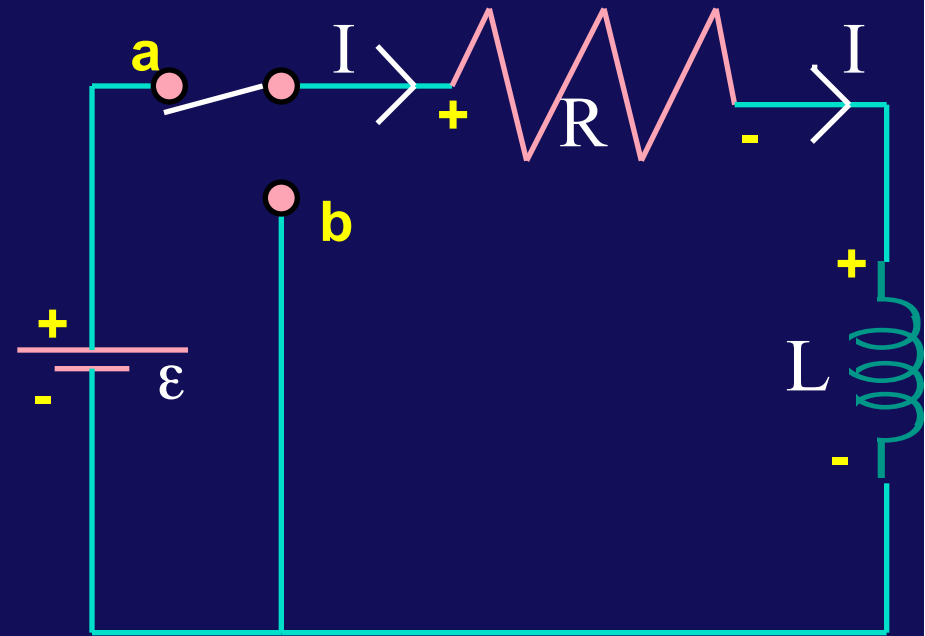- At $t=0$, the switch is closed and the current I starts to flow.



- Loop rule:

$$IR + L \frac{dI}{dt} - \varepsilon = 0$$

Equation is identical in form to that for the RC circuit with the following substitutions:

RC:

$$\frac{q}{C} + R \frac{dq}{dt} - \varepsilon = 0$$

$$\therefore \tau_{RC} = RC$$

\Rightarrow

RC \rightarrow RL:


$$\begin{array}{l} R \rightarrow L \\ \frac{1}{C} \rightarrow R \\ Q \rightarrow I \end{array}$$

\Rightarrow

$$\tau_{RL} = \frac{L}{R}$$

Clicker

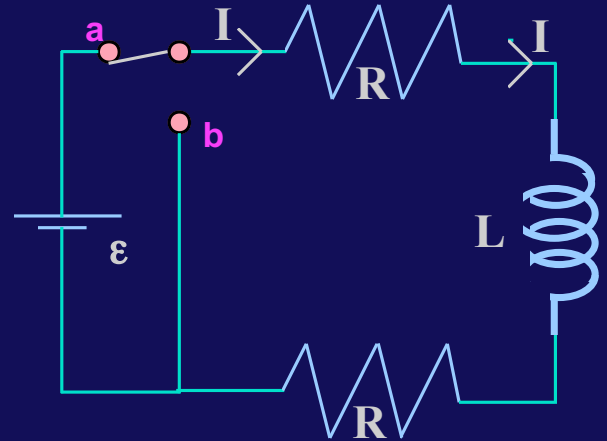- At $t = 0$ the switch is thrown from position **b** to position **a** in the circuit shown:
 - What is the value of the current I_{∞} a long time after the switch is thrown?



(a) $I_{\infty} = 0$


(b) $I_{\infty} = \varepsilon / 2R$

(c) $I_{\infty} = 2\varepsilon / R$

- A long time after the switch is thrown, the current approaches an asymptotic value. ie as $t \rightarrow \infty$, $dI/dt \rightarrow 0$.
- As $dI/dt \rightarrow 0$, the voltage across the inductor $\rightarrow 0$.
- $\therefore I_{\infty} = \varepsilon / 2R$.

Clicker

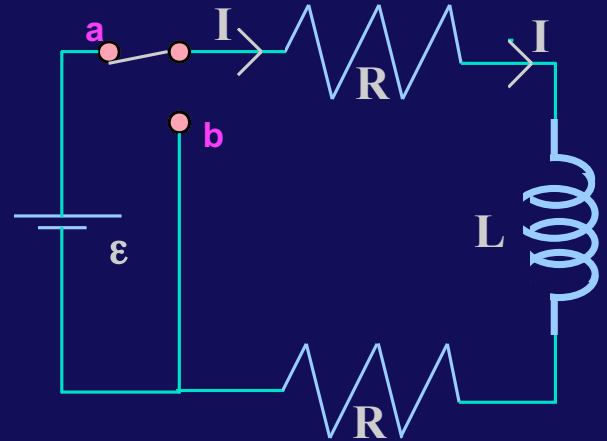What is the value of the current I_0 immediately after the switch is thrown?



(a) $I_0 = 0$

(b) $I_0 = \varepsilon / 2R$

(c) $I_0 = 2\varepsilon / R$


- Immediately after the switch is thrown, the rate of change of current is as large as it can be
 - *(before the inductor was introduced, we assumed the rate of change was ∞ !)*
- The inductor limits dI/dt to be initially equal to ε / L .
 - ie the voltage across the inductor = ε ;
 - the current then must be 0

RL Circuits

- For $I(t)$ choose exponential solution that satisfies the boundary conditions:

$$\frac{dI}{dt}(t = \infty) = 0 \Rightarrow$$
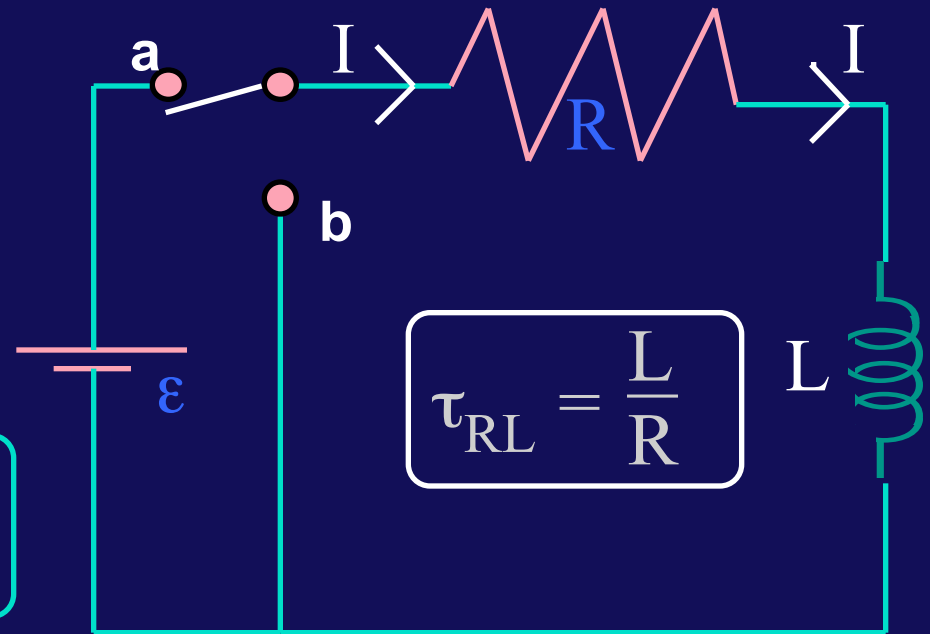
$$I(t = \infty) = \frac{\varepsilon}{R}$$



- We therefore write:

$$I = \frac{\varepsilon}{R} \left(1 - e^{-Rt/L} \right)$$

- The voltage drop across the inductor is given by:

$$V_L = L \frac{dI}{dt} = \varepsilon e^{-Rt/L}$$

RL Circuit (switch ε on)

Current

$$I = \frac{\varepsilon}{R} \left(1 - e^{-Rt/L} \right)$$

$$\text{Max} = \varepsilon/R$$


$$63\% \text{ Max at } t=L/R$$

Voltage on L

$$V_L = L \frac{dI}{dt} = \varepsilon e^{-Rt/L}$$

$$\text{Max} = \varepsilon$$

$$37\% \text{ Max at } t=L/R$$

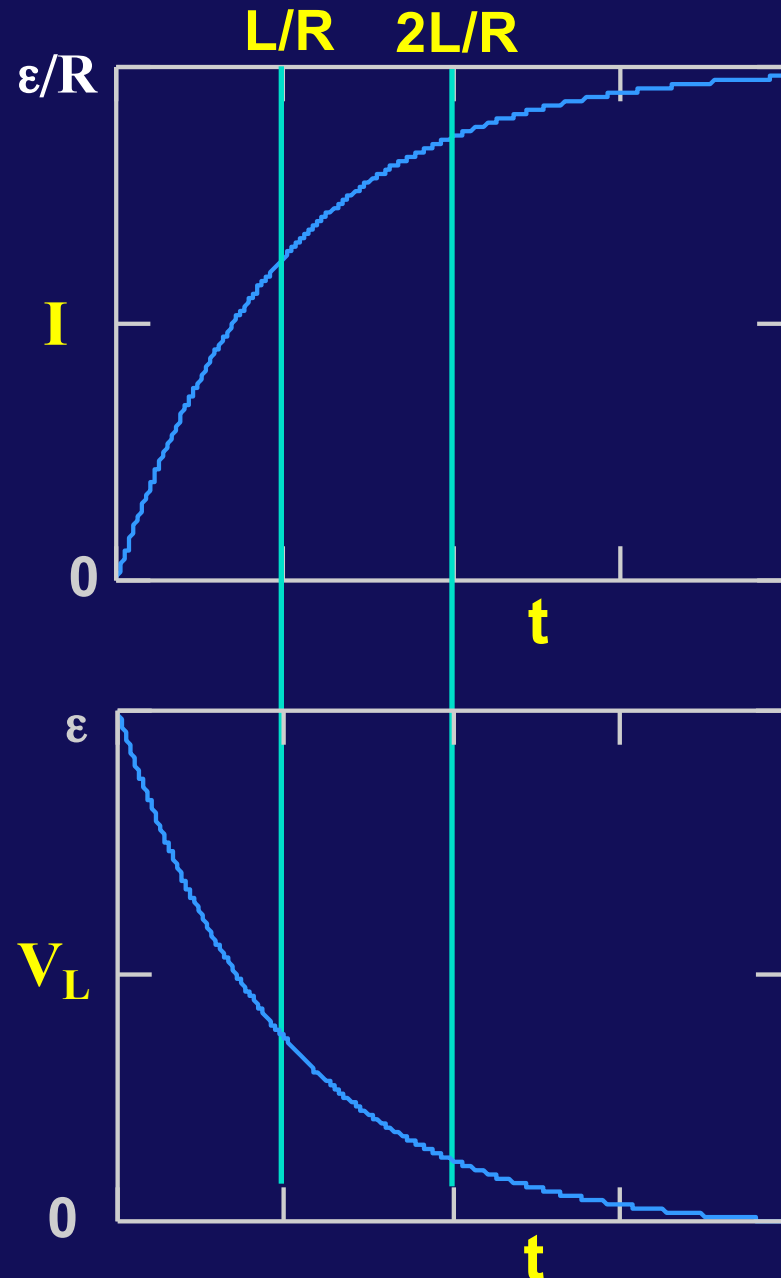


RL Circuits

- After the switch has been in position a for a long time, redefined to be $t=0$, it is moved to position b.

- Loop rule:

$$IR + L \frac{dI}{dt} = 0$$

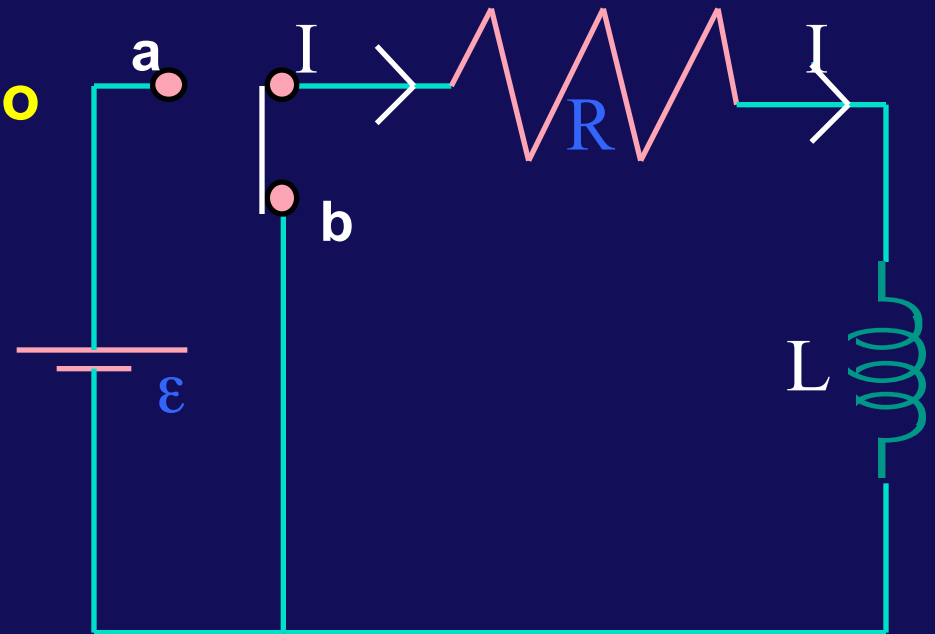

- The appropriate initial condition is:

$$I(t = 0) = \frac{\varepsilon}{R}$$

- The solution then must have the form:

$$I = \frac{\varepsilon}{R} e^{-Rt/L}$$

$$V_L = L \frac{dI}{dt} = -\varepsilon e^{-Rt/L}$$

Warning: this confuses people

RL Circuit (turn off ε)

Current

$$I = \frac{\varepsilon}{R} e^{-Rt/L}$$

Max = ε/R


37% Max at $t=L/R$

Voltage on L

$$V_L = L \frac{dI}{dt} = -\varepsilon e^{-Rt/L}$$





Max = $-\varepsilon$

37% Max at $t=L/R$

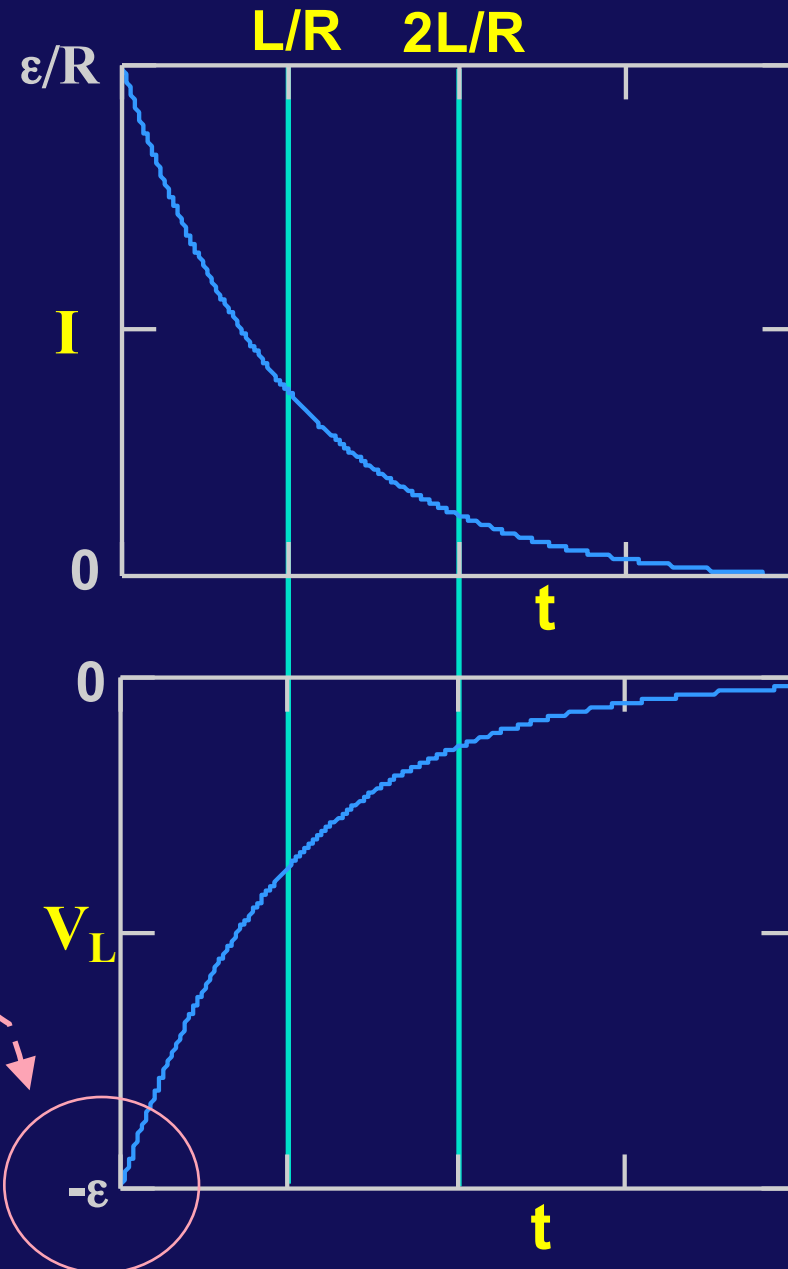

ε on


ε off

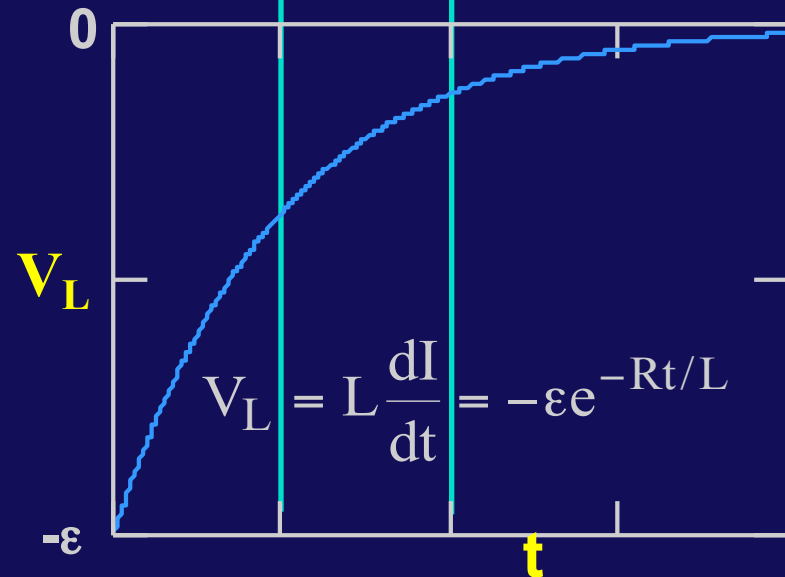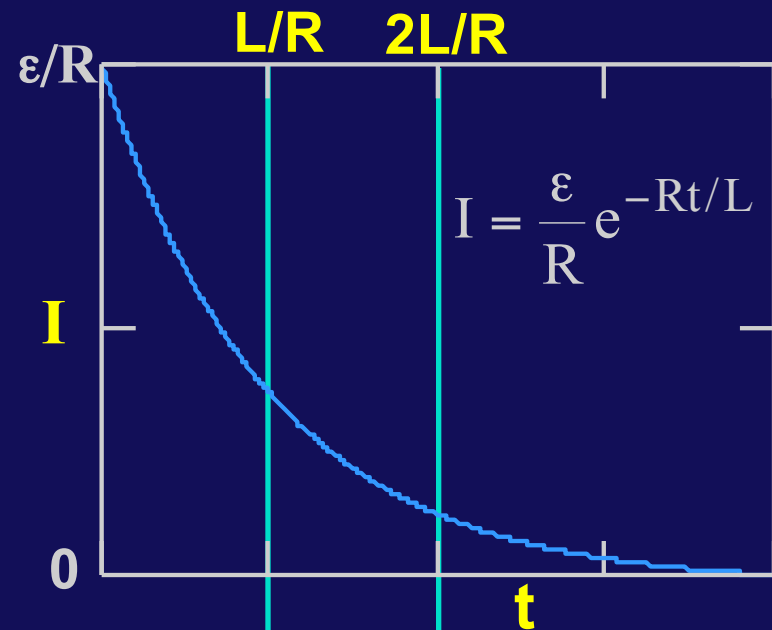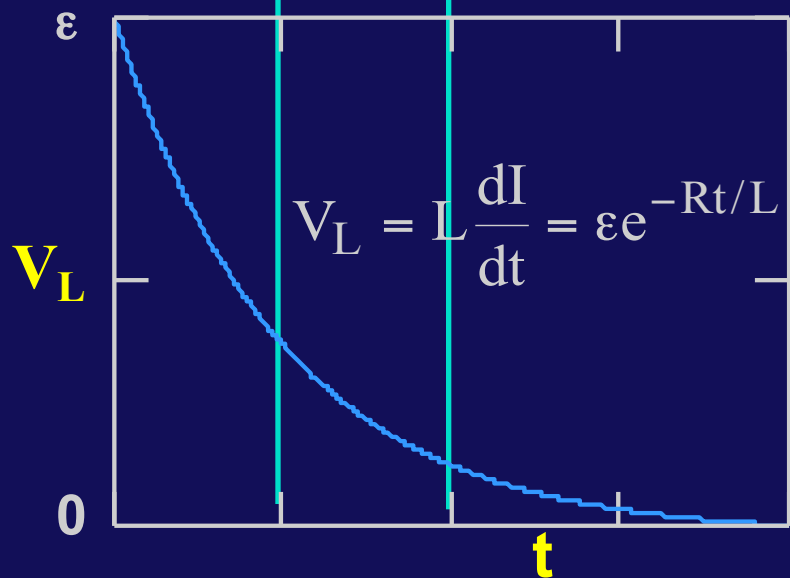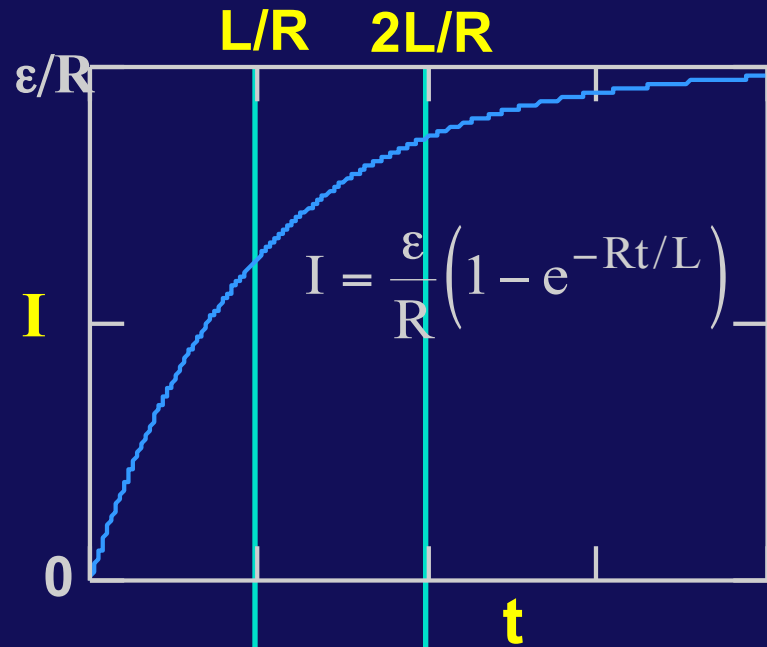

Checkpoint 8




After long time at 0, moved to 1

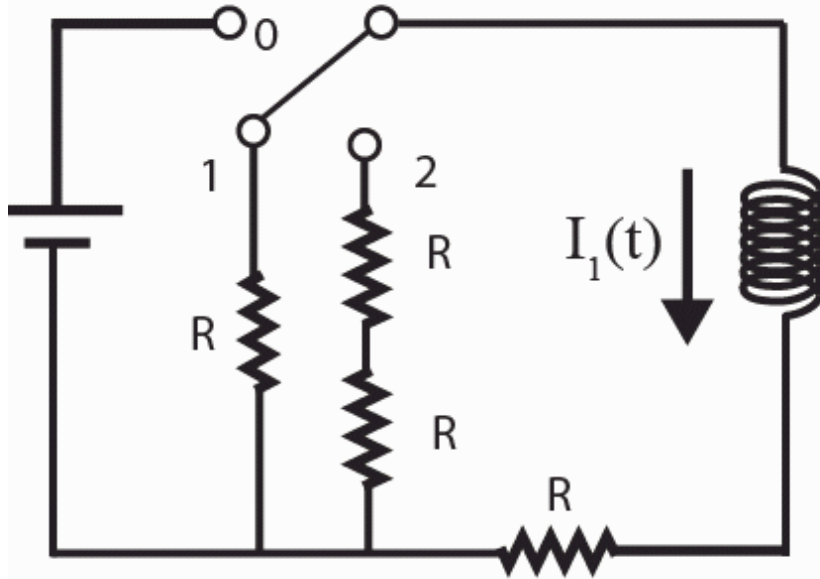

Case 1

After long time at 0, moved to 2

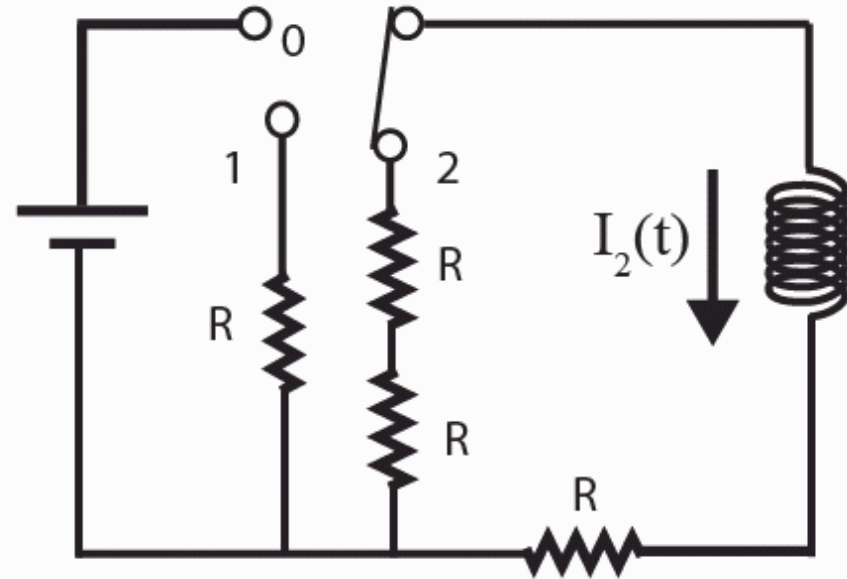


Case 2

After switch moved, which case has larger time constant?

- A) Case 1
- B Case 2
- C) The same


$$\tau_1 = \frac{L}{2R} \quad \tau_2 = \frac{L}{3R}$$

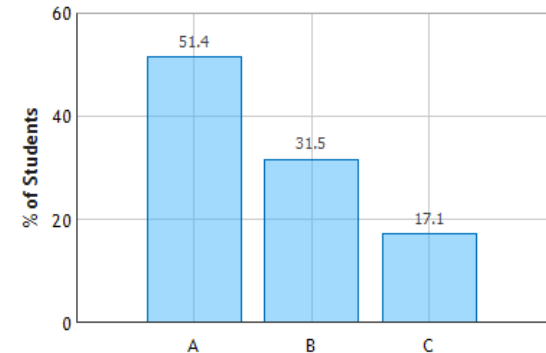

CheckPoint 10




After long time at 0, moved to 1

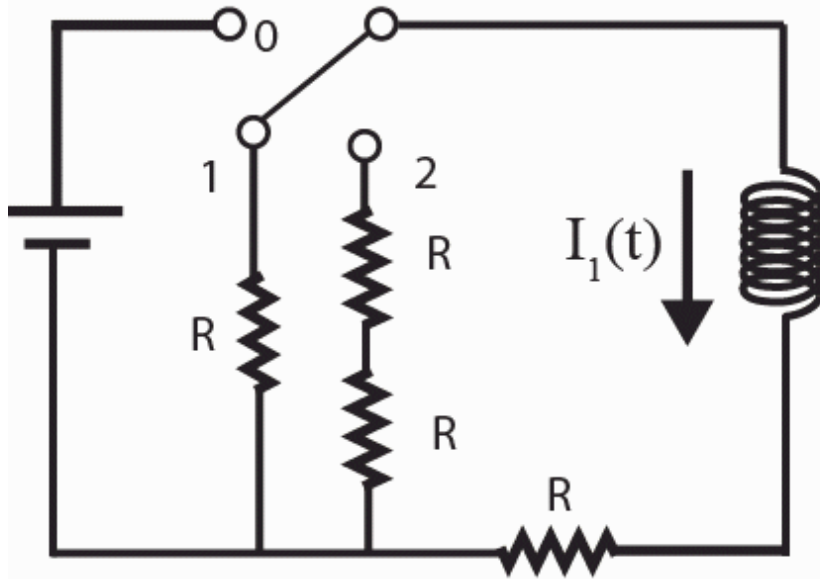

Case 1

After long time at 0, moved to 2

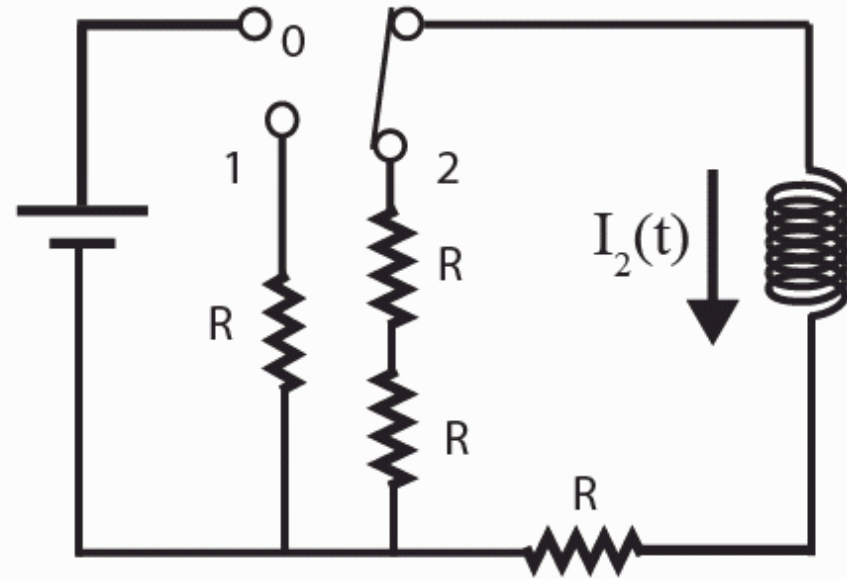

Case 2

Immediately after switch moved, in which case is the **voltage** across the inductor larger?

- A) Case 1
- B) Case 2
- C) The same


Before switch moved: $I = \frac{V}{R}$

After switch moved:

$$V_{L1} = \left(\frac{V}{R}\right)2R$$

$$V_{L2} = \left(\frac{V}{R}\right)3R$$


Compare RL Circuits: Question 3 (N = 194)

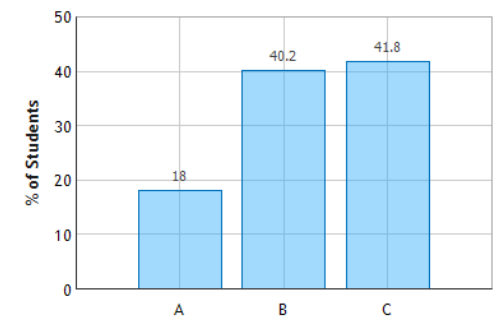

CheckPoint 12




After long time at 0, moved to 1

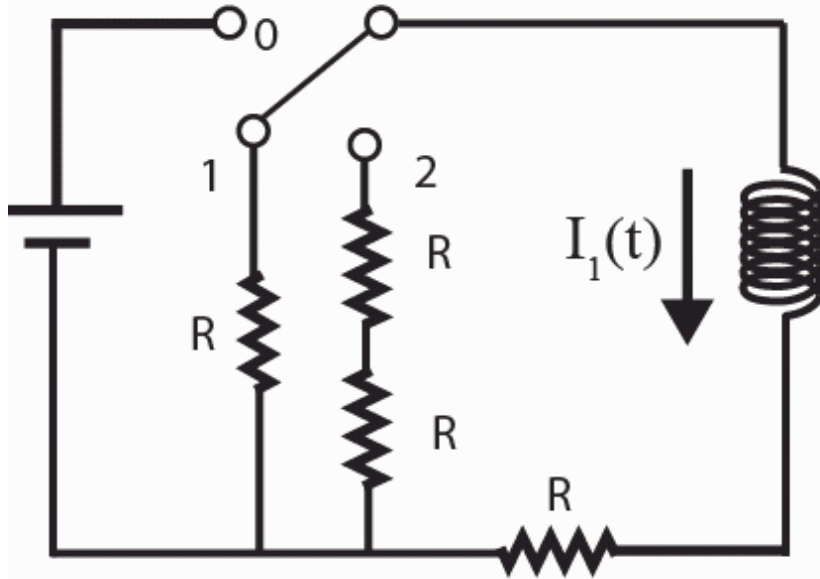

Case 1

After long time at 0, moved to 2

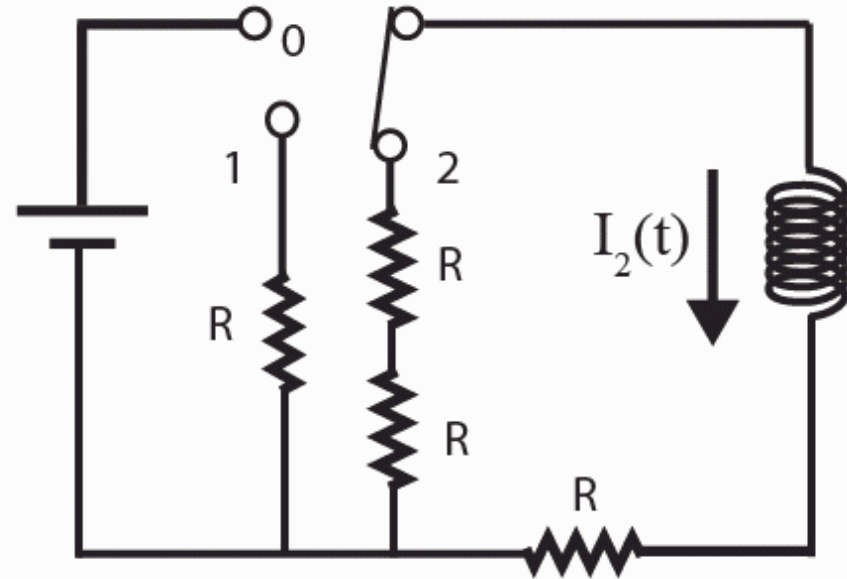

Case 2

After switch moved **for finite time**, in which case is the current through the inductor larger?

- A) Case 1
- B) Case 2
- C) The same

Immediately after: $I_1 = I_2$

After a while ... but not forever


$$I_1 = Ie^{-t/\tau_1}$$

$$I_2 = Ie^{-t/\tau_2}$$

$$\tau_1 > \tau_2$$


Longer time constant to get to zero

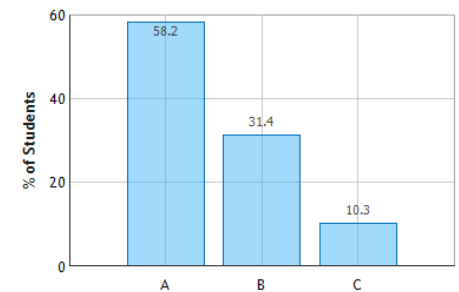Compare RL Circuits: Question 1 (N = 194)



Energy of an Inductor

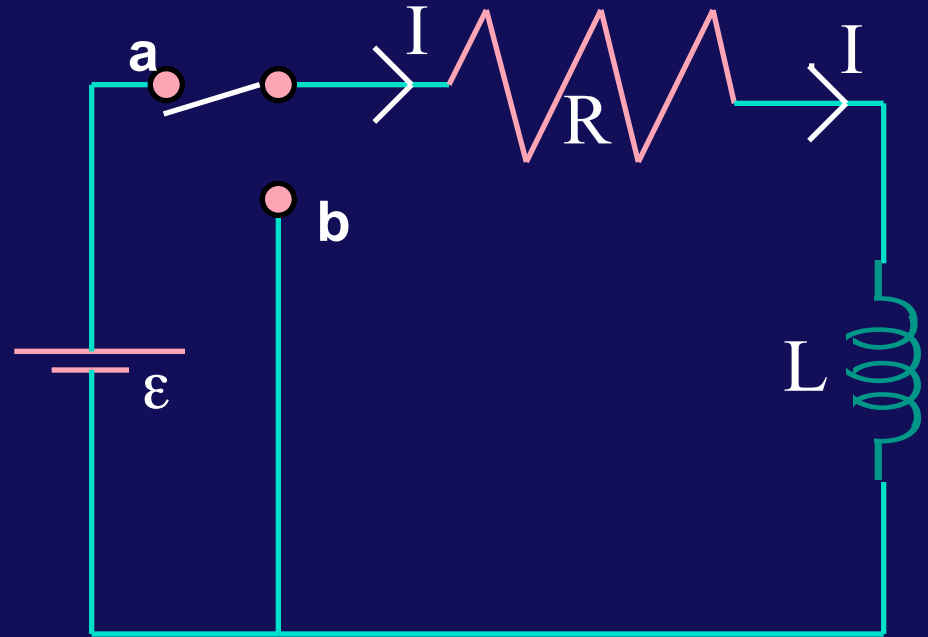- How much energy is stored in an inductor when a current is flowing through it?



- Start with loop rule:

$$\varepsilon = IR + L \frac{dI}{dt}$$

- Multiply this equation by I :

$$\varepsilon I = I^2 R + LI \frac{dI}{dt}$$

- From this equation, we can identify P_L , the rate at which energy is being stored in the inductor:

$$P_L = \frac{dU}{dt} = LI \frac{dI}{dt}$$

- We can integrate this equation to find an expression for U , the energy stored in the inductor when the current = I :

$$U = \int_0^U dU = \int_0^I LI dI$$

\Rightarrow

$$U = \frac{1}{2} LI^2$$


Where is the Energy Stored?

- **Claim:** (without proof) energy is stored *in the Magnetic field itself* (just as in the Capacitor / Electric field case).
- Consider the uniform field inside a long solenoid:

$$B = \mu_0 \frac{N}{l} I$$

- **The inductance L**
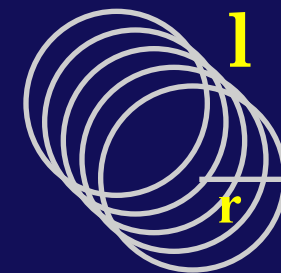
$$L = \mu_0 \frac{N^2}{l} \pi r^2 = \mu_0 \frac{N^2}{l} A$$



N turns

- **Energy U:**

$$U = \frac{1}{2} LI^2 = \frac{1}{2} \left(\mu_0 \frac{N^2}{l} A \right) I^2 = \frac{1}{2} Al \frac{B^2}{\mu_0}$$


- We can turn this into an energy density by dividing by the volume containing the field:

$$u_M = \frac{U}{Al} = \frac{U}{vol} = \frac{1}{2} \frac{B^2}{\mu_0}$$

Recall for E: $u_E = \frac{1}{2} \epsilon_0 E^2$

Bonus material

Some follow-up to spectacular demos

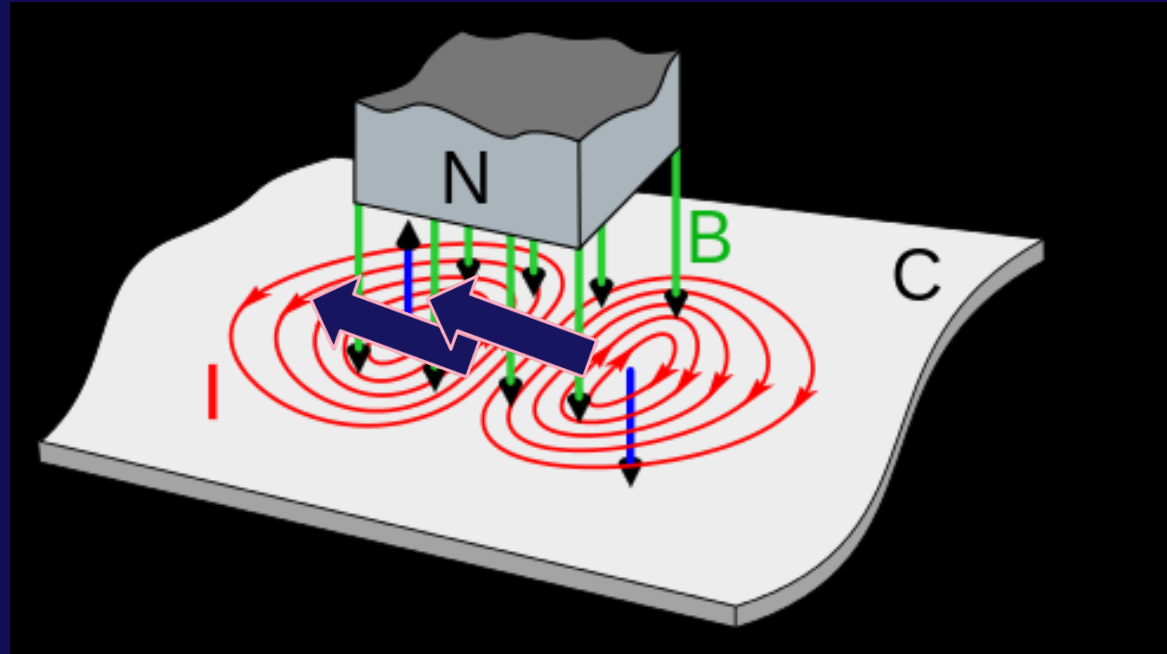

- **When the magnet is moving past the conductors ...**
- **Or when the conductors were moving past the magnets ...**
- **“whirlpools” of current induced. Notice direction of force ... it opposes the change ... causes a “braking” force**

Self-Inductance

- The inductance of an inductor (a set of coils in some geometry ..eg solenoid, toroid) then, like a capacitor, can be calculated from its geometry alone if the device is constructed from conductors and air.
- If extra material (eg iron core) is added, then we need to add some knowledge of materials as we did for capacitors (dielectrics) and resistors (resistivity)

$$L \equiv - \frac{\varepsilon}{(dI / dt)}$$

$$L \equiv \frac{\Phi_B}{I}$$


$$C \equiv \frac{Q}{V}$$

$$C \equiv \kappa C_0$$

$$R = \rho \frac{L}{A}$$




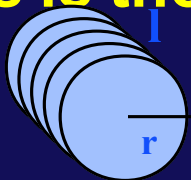- Archetypal inductor is a long solenoid, just as a pair of parallel plates is the archetypal capacitor.



N turns

$$r \ll l$$

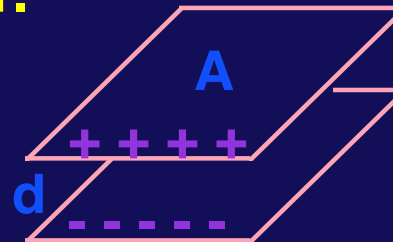



$$d \ll \sqrt{A}$$

A similar CheckPoint

Two solenoids are made with the same cross sectional area and total number of turns. Inductor **B** is twice as long as inductor **A**

$$L_B = \mu_0 n^2 A z$$

\uparrow \uparrow
 $(1/2)^2$ 2

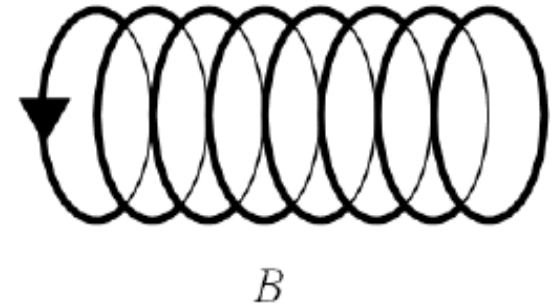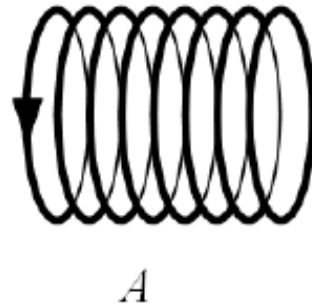


→ $L_B = \frac{1}{2} L_A$

Compare the inductance of the two solenoids

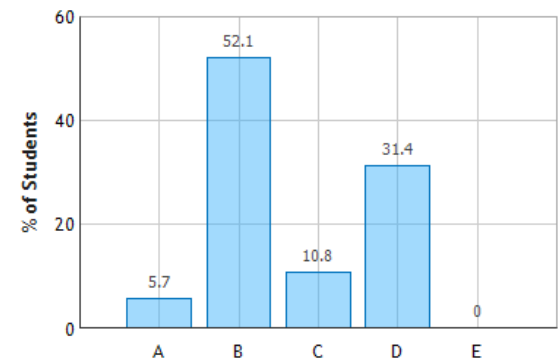- A) $L_A = 4 L_B$
- B) $L_A = 2 L_B$
- C) $L_A = L_B$
- D) $L_A = (1/2) L_B$
- E) $L_A = (1/4) L_B$


Inductance of Solenoids: Question 1 (N = 194)




Clicker (like the prelecture question)

- Consider the two inductors shown:

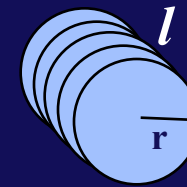- Inductor 1 has length l , N total turns and has inductance L_1 .
- Inductor 2 has length $2l$, $2N$ total turns and has inductance L_2 .
- What is the relation between L_1 and L_2 ?



N turns

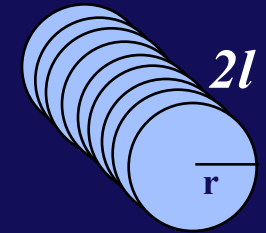

$2N$ turns

(a) $L_2 < L_1$

(b) $L_2 = L_1$

(c) $L_2 > L_1$



$$L = \mu_0 n^2 Al$$

- N/l does not change \rightarrow n is same for both
- l is twice as long for 2nd one
- $L_2 = 2L_1$

Clicker

At $t = 0$, the switch is thrown from position **b** to position **a** as shown:

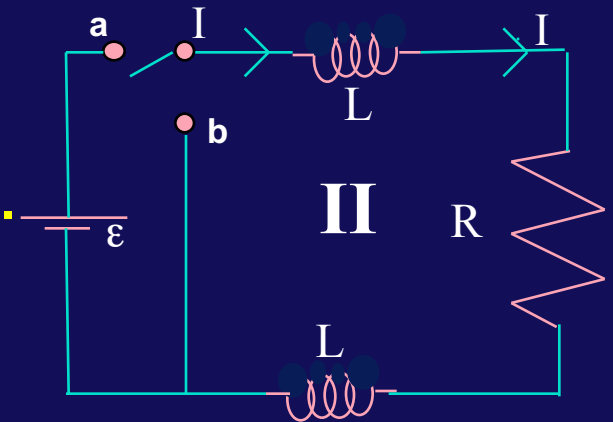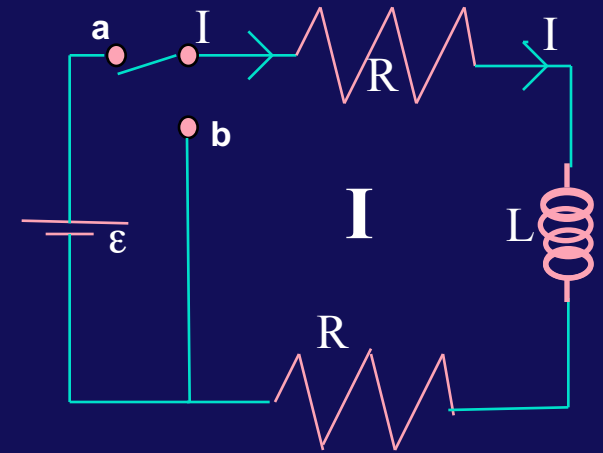- Let t_I be the time for circuit **I** to reach $1/2$ of its asymptotic current.
- Let t_{II} be the time for circuit **II** to reach $1/2$ of its asymptotic current.
- What is the relation between t_I and t_{II} ?



(a) $t_{II} < t_I$ (b) $t_{II} = t_I$ (c) $t_{II} > t_I$

- Determine the time constants of the two circuits.
- Write down the loop eqns:


$$\text{I: } IR + L \frac{dI}{dt} + IR - \varepsilon = 0 \quad \Rightarrow \quad \tau_I = \frac{L}{2R}$$

$$\text{II: } L \frac{dI}{dt} + IR + L \frac{dI}{dt} - \varepsilon = 0 \quad \Rightarrow \quad \tau_{II} = \frac{2L}{R}$$

Can you determine from this Clicker the rule for adding inductors in series?

Classic Calculation

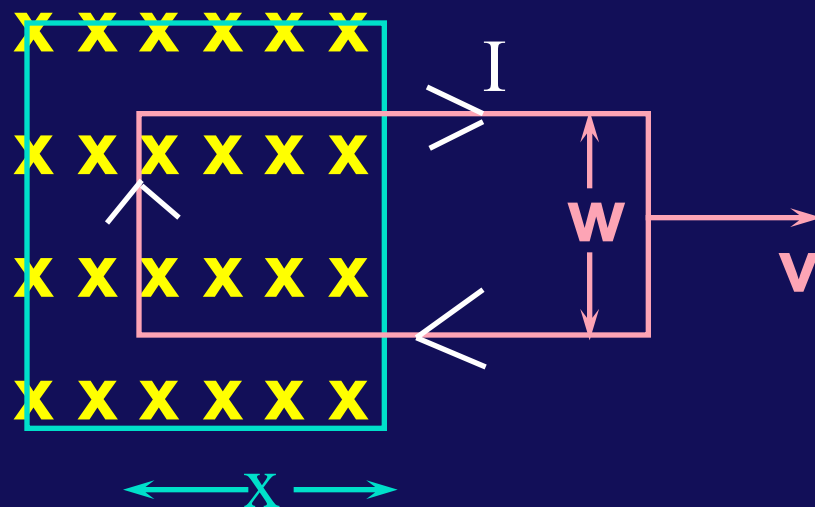- Suppose we pull with velocity v a coil of resistance R through a region of constant magnetic field B .
 - What will be the induced current?
 - » What direction?
 - Lenz' Law \Rightarrow clockwise!!
 - What is the magnitude?



» Magnetic Flux:

$$\Phi_B = xwB$$

» Faraday's Law:

$$\varepsilon = -\frac{d\Phi_B}{dt}$$

$$\therefore \frac{d\Phi_B}{dt} = wB \frac{dx}{dt} = wBv \quad \Rightarrow$$

$$I = \frac{\varepsilon}{R} = \frac{wBv}{R}$$