

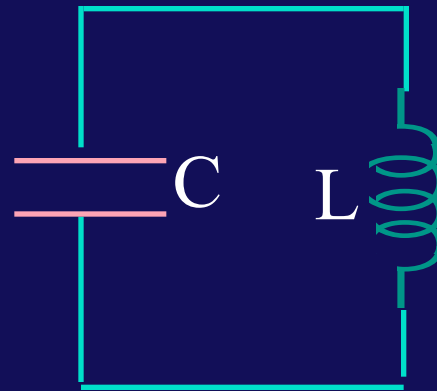
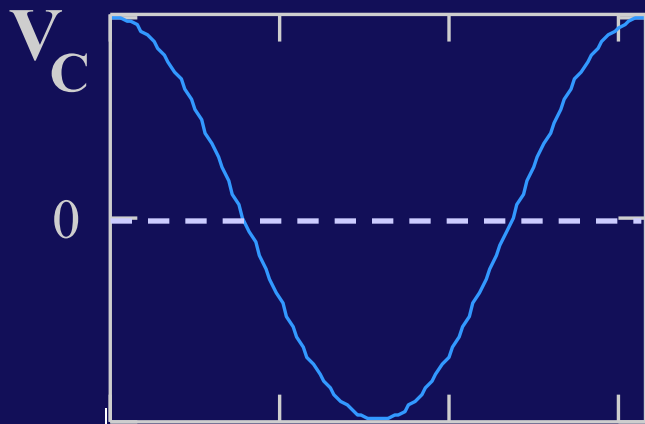
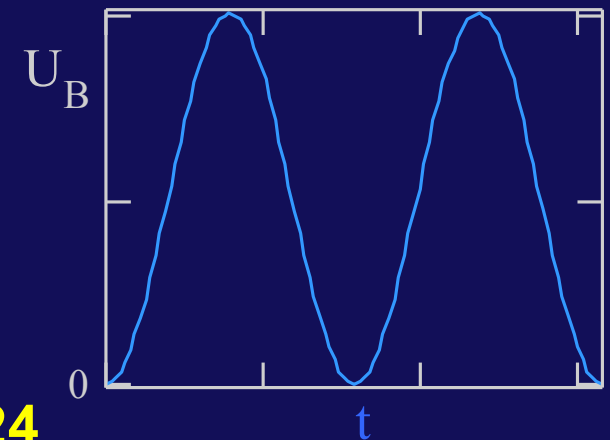


Oscillations

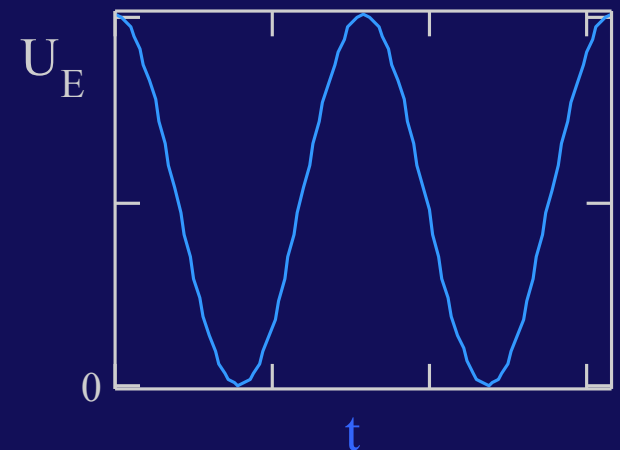

**LC
Circuits**

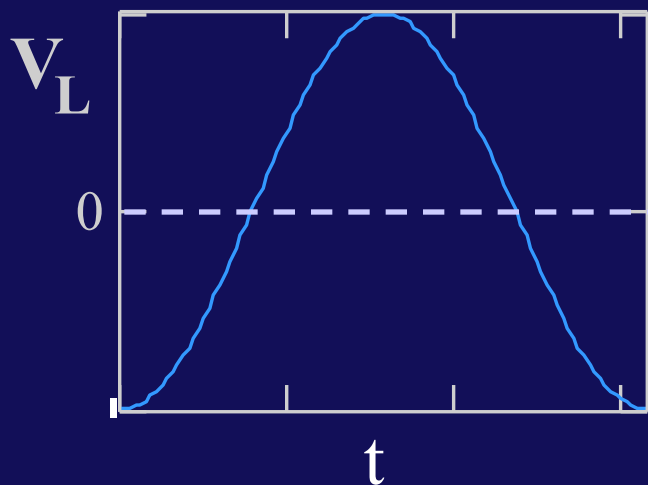


Exam 3

- **Thursday**
- **Covers RC circuits through Faraday's law**

Energy in the *Magnetic* Field

“Power” accounting in a LR circuit...

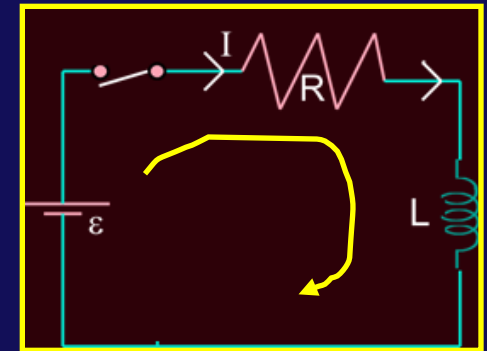

$$\epsilon I = I^2 R + LI \frac{dI}{dt}$$

Loop rule x I ...

$$P_L = \frac{dU}{dt} = LI \frac{dI}{dt}$$


Rate of energy flow into L

$$U = \int_0^U dU = \int_0^I LI dI$$

Total energy flow

$$U = \frac{1}{2} LI^2$$


... energy stored

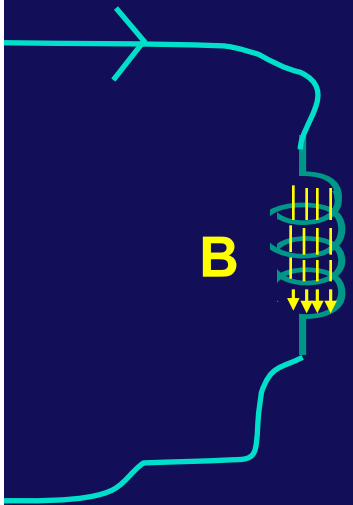

But where is it “Stored”?

- **Claim: energy is stored *in the Magnetic field itself***
- **Consider the uniform field inside a long solenoid:**

$$B = \mu_0 \frac{N}{l} I$$

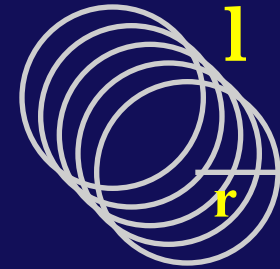

- **The inductance L is:**

$$L = \mu_0 \frac{N^2}{l} A$$

N turns

- **Stored Energy U:**

$$U = \frac{1}{2} LI^2 = \frac{1}{2} \left(\mu_0 \frac{N^2}{l} A \right) I^2 = \frac{1}{2} Al \frac{B^2}{\mu_0}$$


- **Get energy density by dividing by the volume containing the field:**

$$u_M = \frac{U}{Al} = \frac{U}{vol} = \frac{1}{2} \frac{B^2}{\mu_0}$$

Recall & Compare

Energy in the *Electric* Field

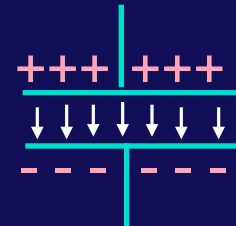Work needed to add charge to capacitor...



$$dW = dq(V) = dq\left(\frac{q}{C}\right)$$

$$W = \frac{1}{C} \int_0^Q q dq = \frac{1}{2} \frac{Q^2}{C} = \frac{1}{2} CV^2 \quad \dots \text{total work} \dots$$

Recall: $C = \epsilon_0 A/d$ & $V = Ed$


$$u = \frac{W}{\text{volume}} = \frac{1}{2} \epsilon_0 E^2 \quad \dots \text{energy density}$$

Energy Density:

$$u_{\text{electric}} = \frac{1}{2} \epsilon_0 E^2$$



$$u_{\text{magnetic}} = \frac{1}{2} \frac{B^2}{\mu_0}$$

RC/LC Circuits

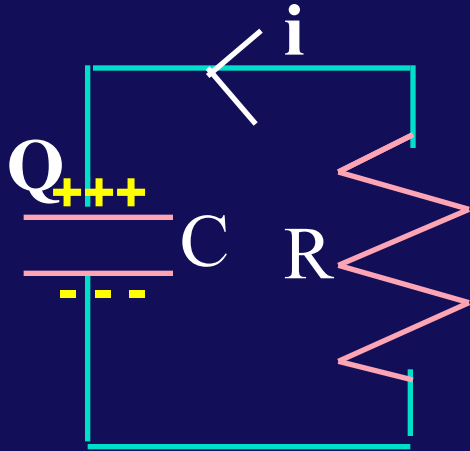


RC or LR:

current decays exponentially

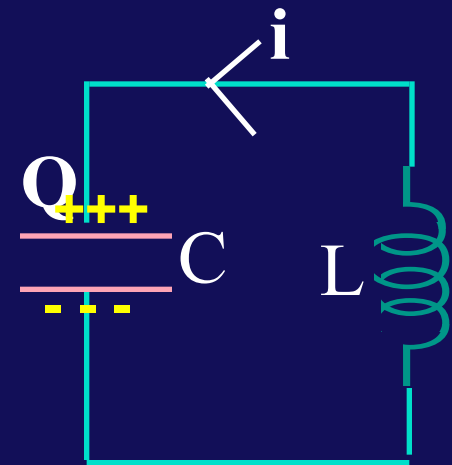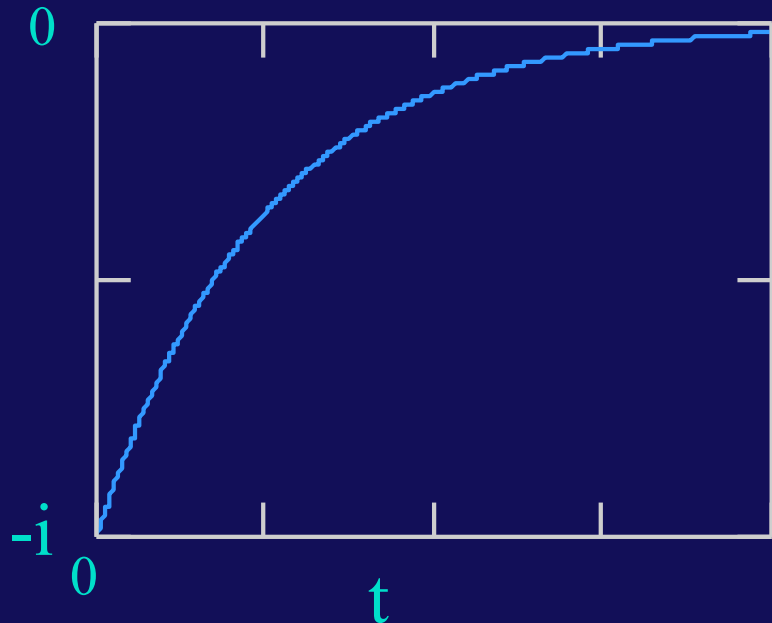


LC:


current oscillates

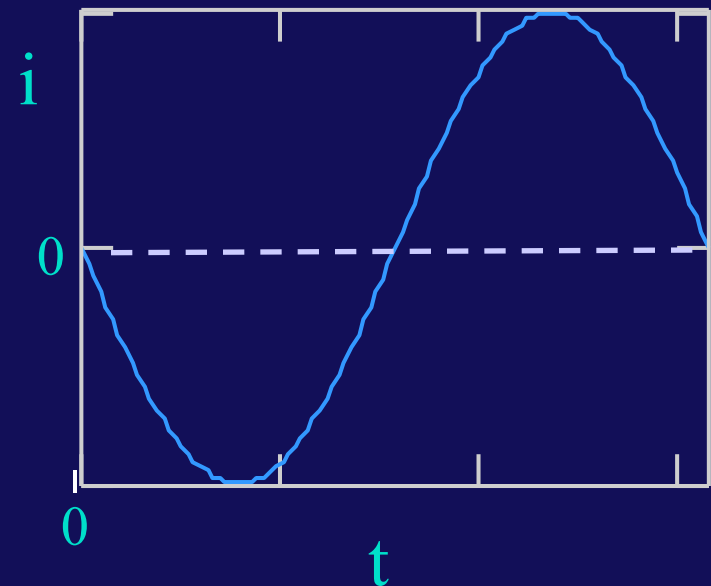

LC Oscillations (qualitative)

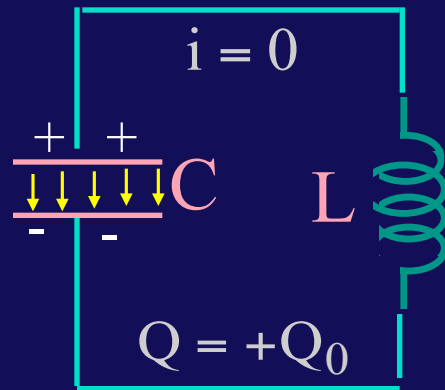


α

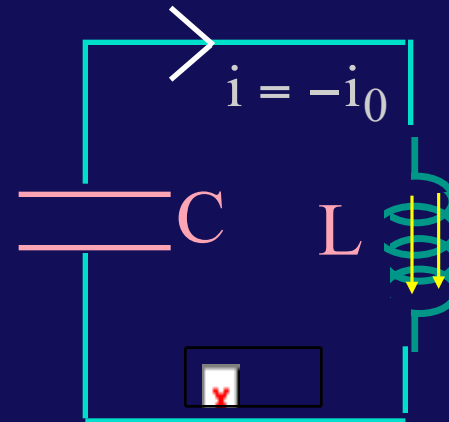


β



γ

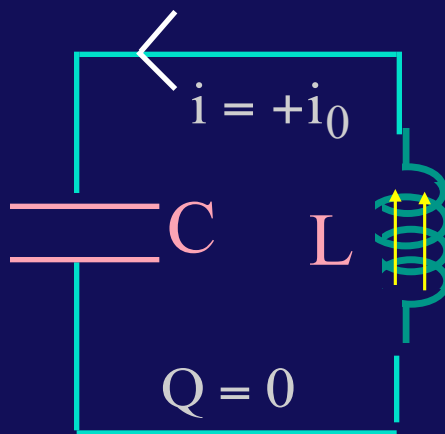

δ

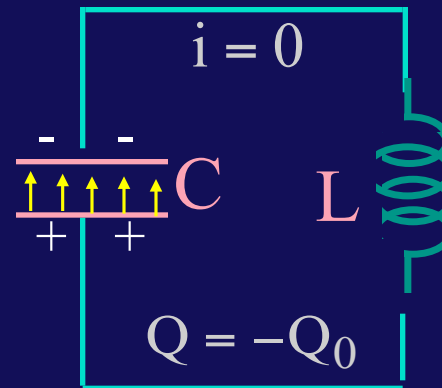

LC Oscillations (qualitative)

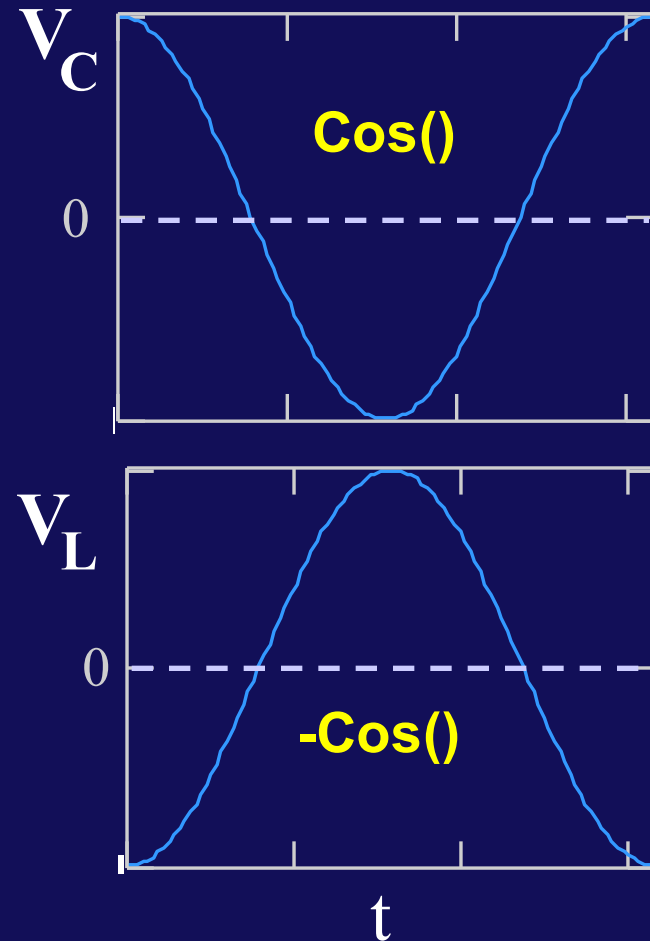
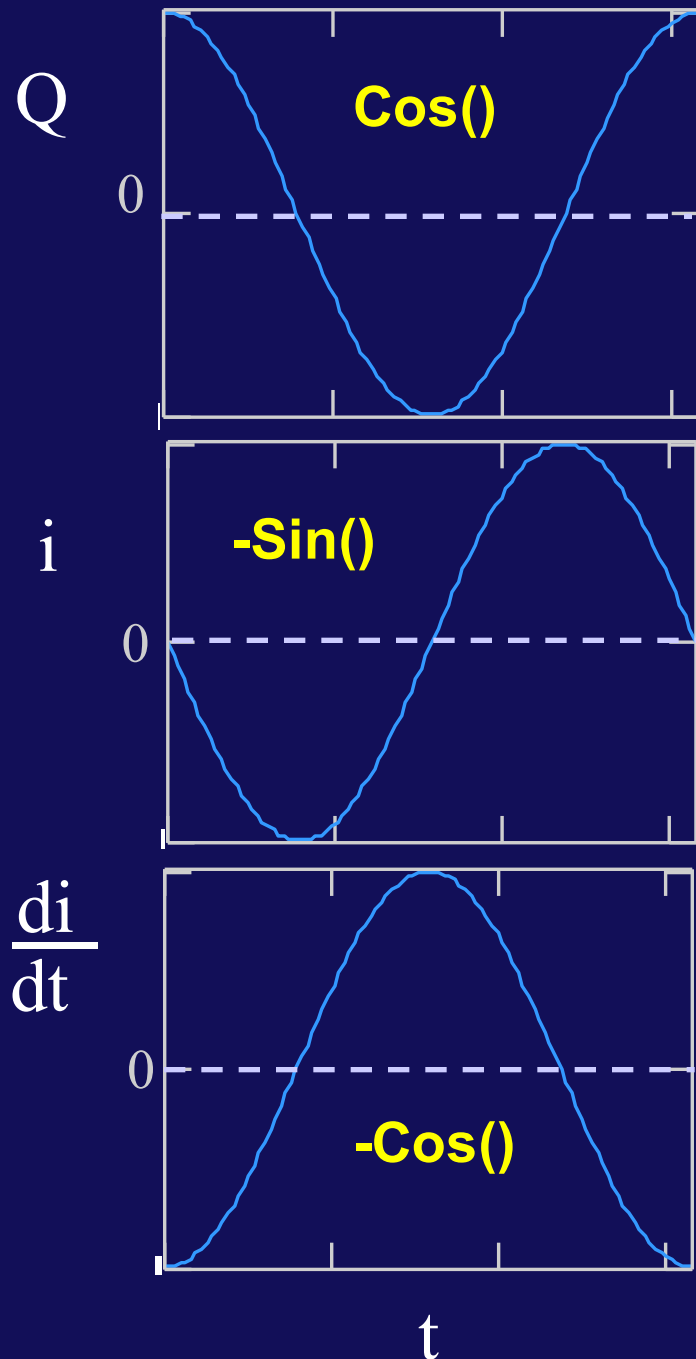


How do these change if L has a finite R?

Clicker

At $t=0$, the capacitor in the LC circuit shown has a total charge Q_0 . At $t = t_1$, the capacitor is uncharged.

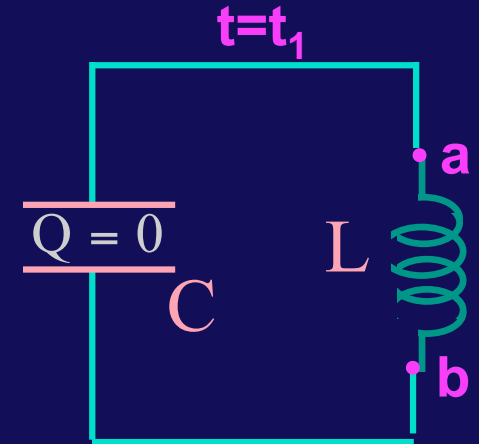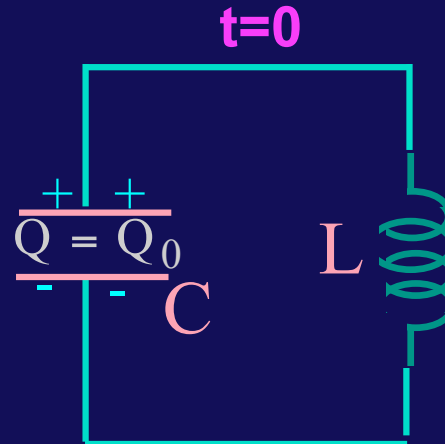- What is the value of V_{ab} , the voltage across the inductor at time t_1 ?



(a) $V_{ab} < 0$


(b) $V_{ab} = 0$

(c) $V_{ab} > 0$

- V_{ab} is the voltage across the inductor, but it is also the voltage across the capacitor!
- Charge on the capacitor is zero, $\rightarrow V_C = 0$
- When $Q = 0$ on capacitor, I is maximum through inductor
 - and dI/dt is zero then so $V_L = 0$ makes sense

Clicker

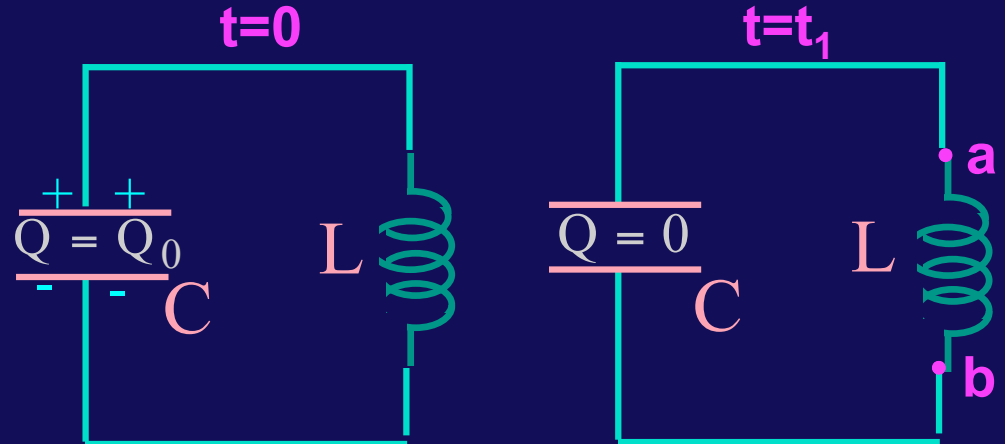At $t = 0$, the capacitor in the LC circuit shown has a total charge Q_0 . At $t = t_1$, the capacitor is uncharged.



What is the relation between U_{L1} , the energy stored in the inductor at $t = t_1$, and U_{C1} , the energy stored in the capacitor at $t = t_1$?

(a) $U_{L1} < U_{C1}$

(b) $U_{L1} = U_{C1}$

(c) $U_{L1} > U_{C1}$

At $t = t_1$, the charge on the capacitor is zero.


$$U_{C1} = \frac{Q_1^2}{2C} = 0$$

At $t = t_1$, the current is a maximum.


$$U_{L1} = \frac{1}{2}LI_1^2 = \frac{Q_0^2}{2C} > 0$$

LC Oscillations (L with finite R)

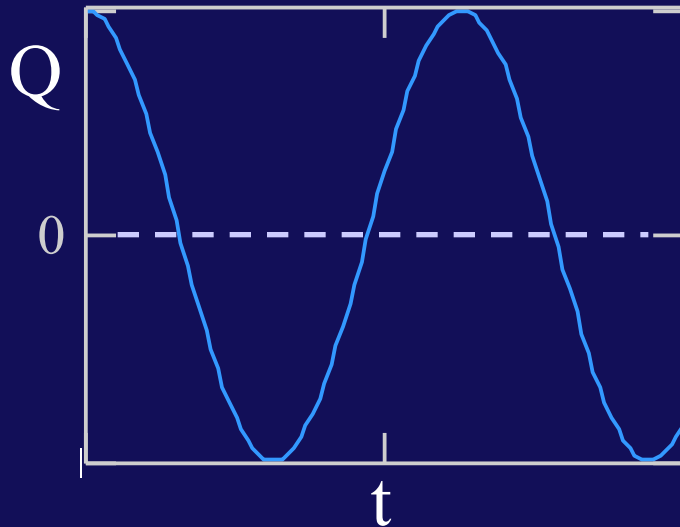- If L has finite Resistance, then
 - energy **will be** dissipated in R **and**
 - **the** oscillations **will** become damped.




$$R = 0$$

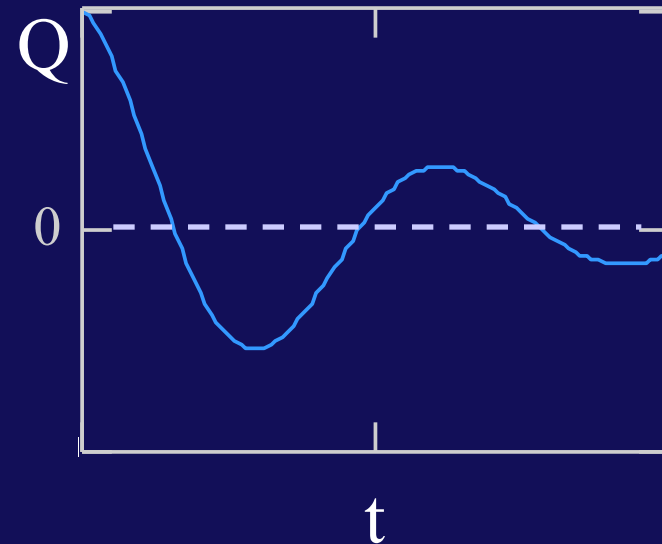

$$R \neq 0$$

Quick checkpoint review

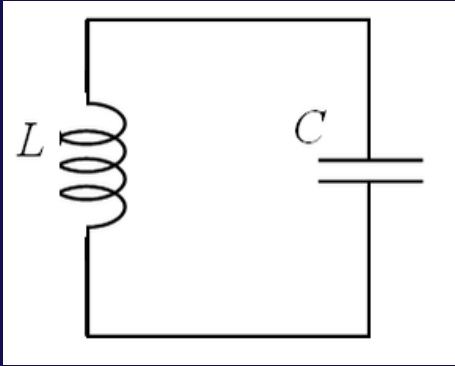At time $t = 0$ the capacitor in the circuit below is fully charged with Q_{\max} , and the current through the circuit is 0.




- What is the potential difference across the inductor at $t = 0$?
 - Ans: $V_L = Q_{\max} / C$ (same as capacitor)
- What is the potential difference across the inductor when current is maximum?
 - Ans: **0**
- How much energy is stored in C when I is max?
 - Ans: **$U = 0$** (it's all in the inductor)

LC Oscillations (quantitative)

- **Begin with the loop rule:**
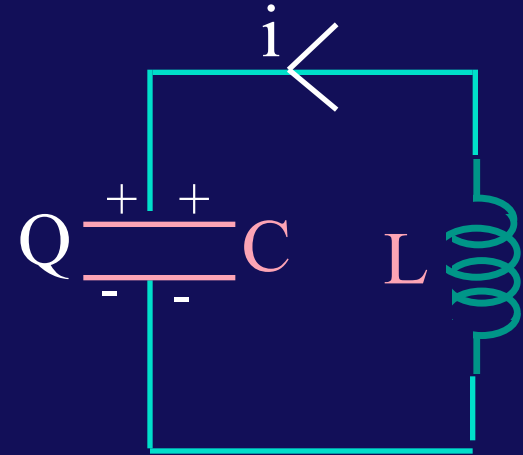
$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0$$



- **Guess solution: (harmonic oscillator)**

$$Q = Q_0 \cos(\omega_0 t + \phi)$$

In mechanics

$$-kx = m \frac{d^2 x}{dt^2}$$

where:

- ω_0 **determined from equation**
- ϕ, Q_0 **determined from initial conditions**
- **Procedure: differentiate above form for Q and substitute into loop equation to find ω_0**

LC Oscillations (quantitative)

- **General solution:**

$$Q = Q_0 \cos(\omega_0 t + \phi)$$

- **Differentiate twice:**

$$\frac{dQ}{dt} = -\omega_0 Q_0 \sin(\omega_0 t + \phi)$$


$$\frac{d^2Q}{dt^2} = -\omega_0^2 Q_0 \cos(\omega_0 t + \phi)$$

- **Substitute into loop eqn:**

$$L\left(-\omega_0^2 Q_0 \cos(\omega_0 t + \phi)\right) + \frac{1}{C}\left(Q_0 \cos(\omega_0 t + \phi)\right) = 0 \quad \text{p} \quad -\omega_0^2 L + \frac{1}{C} = 0$$

∴

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

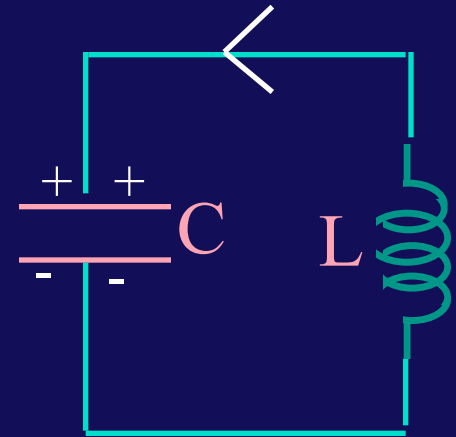

$$L \frac{d^2Q}{dt^2} + \frac{Q}{C} = 0$$

Clicker


At $t = 0$ the capacitor has charge Q_0 ; the resulting oscillations have frequency ω_0 . The maximum current in the circuit during these oscillations has value I_0 .

- What is the relation between ω_0 and ω_2 , the frequency of oscillations when the initial charge = $2Q_0$?

(a) $\omega_2 = 1/2 \omega_0$

(b) $\omega_2 = \omega_0$


(c) $\omega_2 = 2 \omega_0$

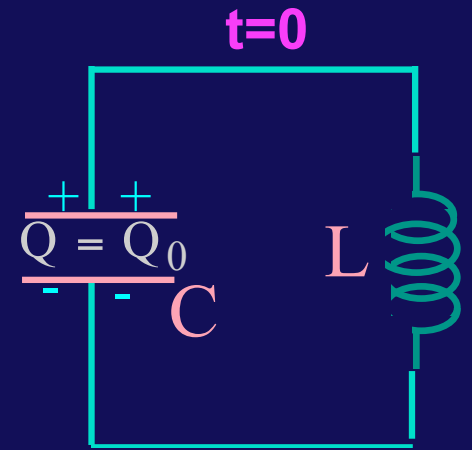

- Q_0 determines the amplitude of the oscillations (initial condition)
- The frequency is determined by the circuit parameters (L,C) only

Clicker

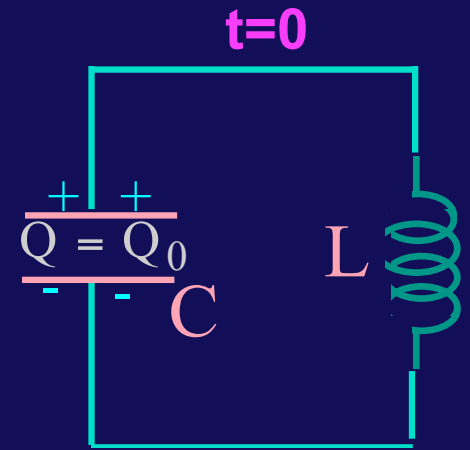- At $t = 0$ the capacitor has charge Q_0 ; the resulting oscillations have frequency ω_0 . The maximum current in the circuit during these oscillations has value I_0 .



What is the relation between I_0 and I_2 , the maximum current in the circuit when the initial charge = $2Q_0$?

(a) $I_2 = I_0$

(b) $I_2 = 2 I_0$

(c) $I_2 = 4 I_0$

- The initial charge determines the total energy : $U_0 = Q_0^2/2C$
- Maximum current occurs when $Q = 0$
- When all the energy is in the inductor: $U = 1/2 L I_0^2$
- Doubling initial charge quadruples total energy.
 - Implies maximum current must double

LC Oscillations

Does solution conserve energy?

YES !!

Energy in E field:

$$U_E(t) = \frac{1}{2} \frac{Q^2(t)}{C} = \frac{1}{2C} Q_0^2 \cos^2(\omega_0 t + \phi)$$

Energy in B field:

$$U_B(t) = \frac{1}{2} Li^2(t) = \frac{1}{2} L \omega_0^2 Q_0^2 \sin^2(\omega_0 t + \phi)$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$U_B(t) = \frac{1}{2C} Q_0^2 \sin^2(\omega_0 t + \phi)$$

$$U_E(t) + U_B(t) = \frac{Q_0^2}{2C}$$


Quick checkpoint review

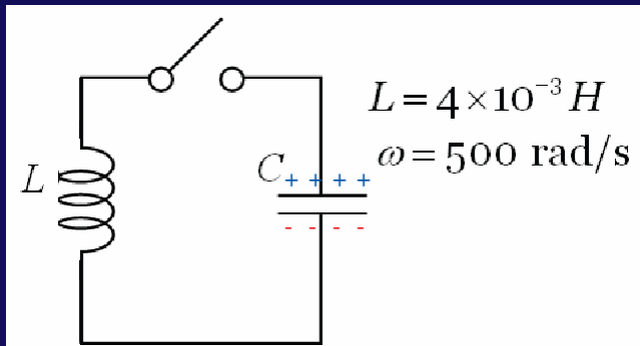The capacitor charged such that the top plate has a charge $+Q_0$ and the bottom plate $-Q_0$. At time $t=0$, the switch is closed ...



- What is the value of the capacitor C ?
 - Ans: $(500)^2 \times L = 1 / C$
 - **$C = 10^{-3} \text{ F}$**


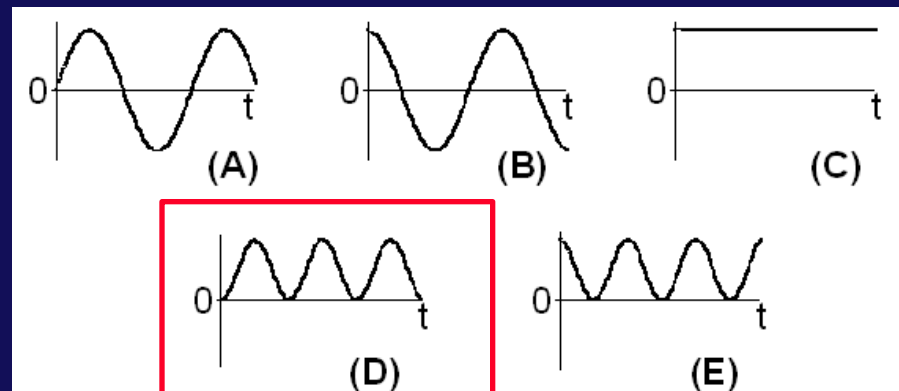
- Which of the following plots best represents the energy in the inductor as a function of time starting just after the switch is closed?



Energy is always **POSITIVE** (proportional to Square of current)

Energy Plotted vs Time


$$U_E(t) + U_B(t) = \frac{Q_0^2}{2C}$$

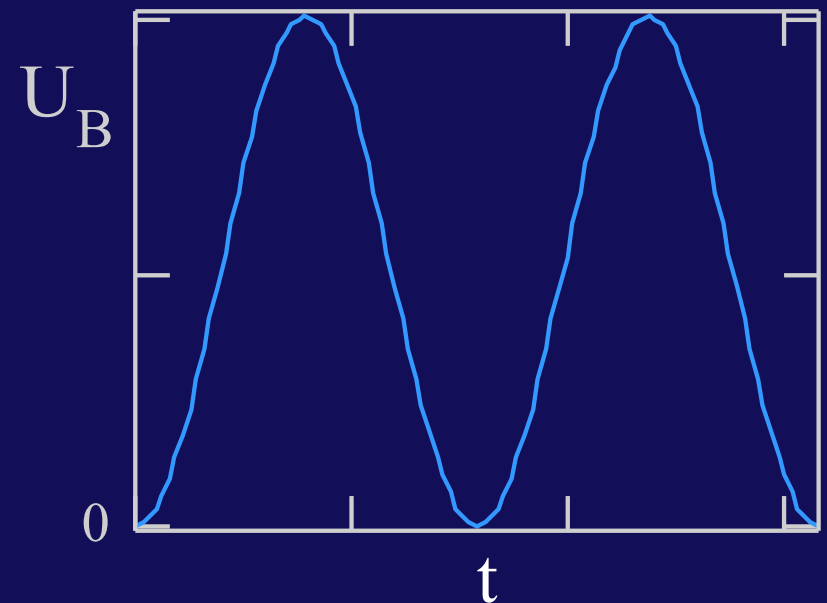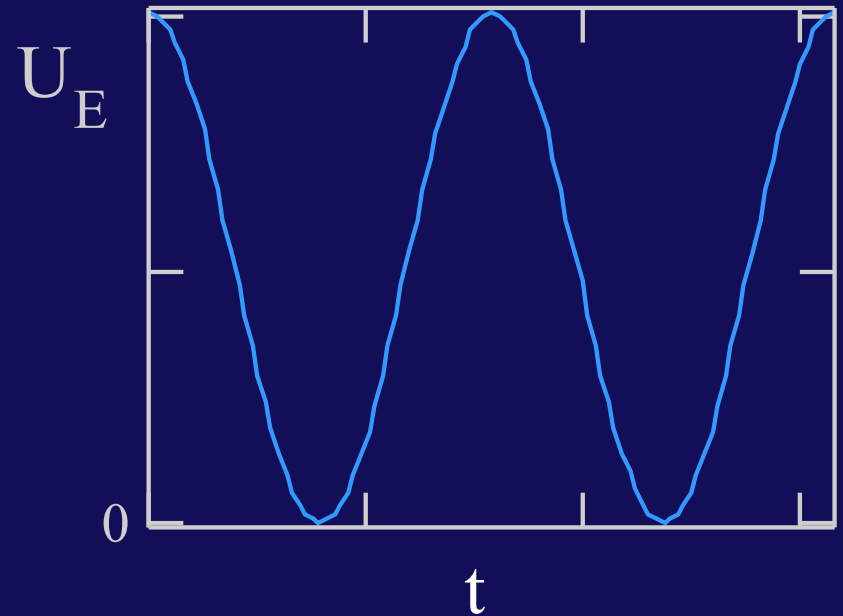

Clicker

At $t = 0$ the current flowing through the circuit is $1/2$ of its maximum value.

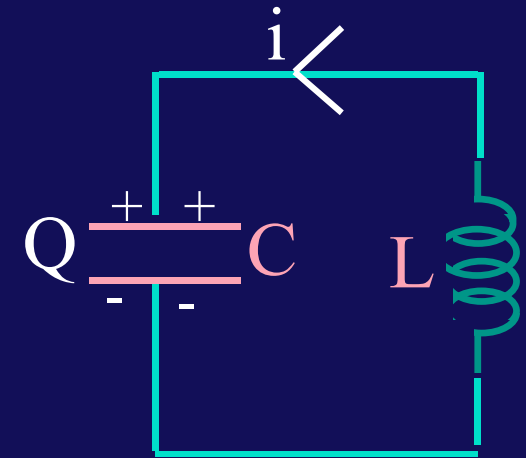- Which of the following is a possible value for the phase ϕ , when the charge on the capacitor is described by: $Q(t) = Q_0 \cos(\omega t + \phi)$.



(a) $\phi = 30^\circ$

(b) $\phi = 45^\circ$

(c) $\phi = 60^\circ$

- We are given a form for the charge on the capacitor as a function of time, but we need to know the current as a function of time.

$$I(t) = \frac{dQ}{dt} = -\omega_0 Q_0 \sin(\omega_0 t + \phi)$$

- At $t = 0$, the current is given by: $I(0) = -\omega_0 Q_0 \sin \phi$





- The maximum value of the current is: $I_{\max} = \omega_0 Q_0$

- Therefore, the phase angle must be given by: $\sin \phi = \pm \frac{1}{2}$ **p** $\phi = \pm 30^\circ$

Clicker

At $t = 0$ the current flowing through the circuit is $1/2$ of its maximum value.

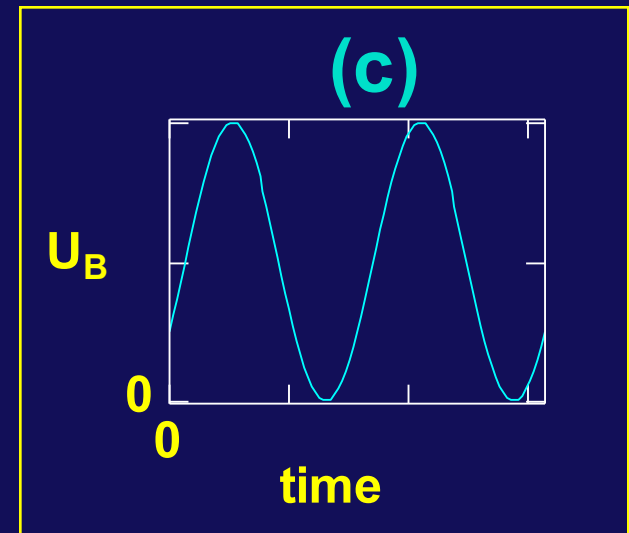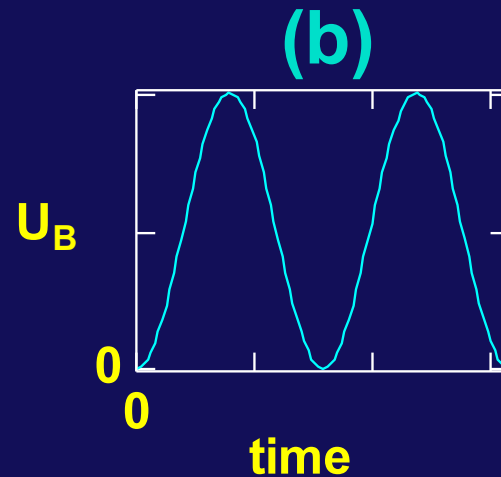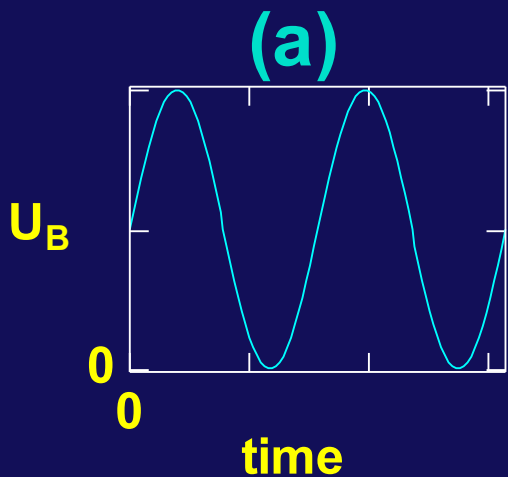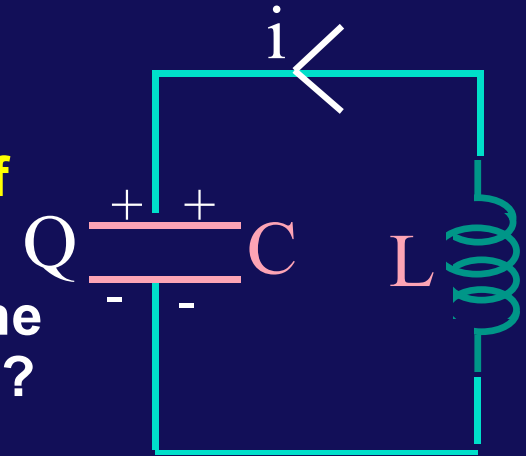Which of the following plots best represents U_B , the energy stored in the inductor as a function of time?




Energy stored in the inductor proportional to the CURRENT SQUARED.

If the current at $t = 0$ is $1/2$ its maximum value, the energy stored in the inductor will be $1/4$ of its maximum value!!

LCR Damping

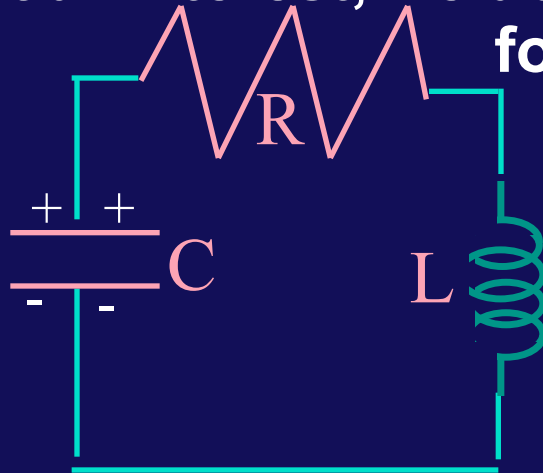
For your interest, we do not derive here, but only illustrate the following behavior



$$Q = Q_0 e^{-\beta t} \cos(\omega'_o t + \phi)$$

$$\beta = \frac{R}{2L}$$
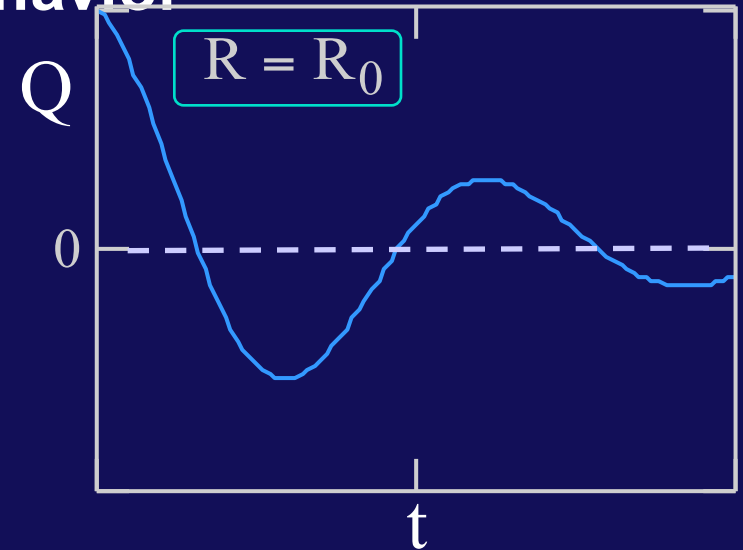
$$\omega'_o = \sqrt{\left(\frac{1}{LC} - \frac{R^2}{4L^2}\right)}$$



In a LRC circuit, ω depends also on R !

