
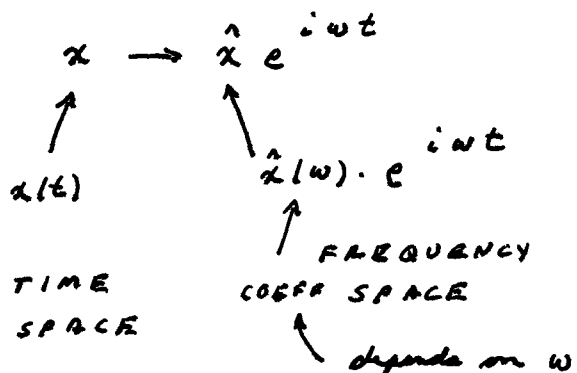



MIT OSCILLATOR VIDEO

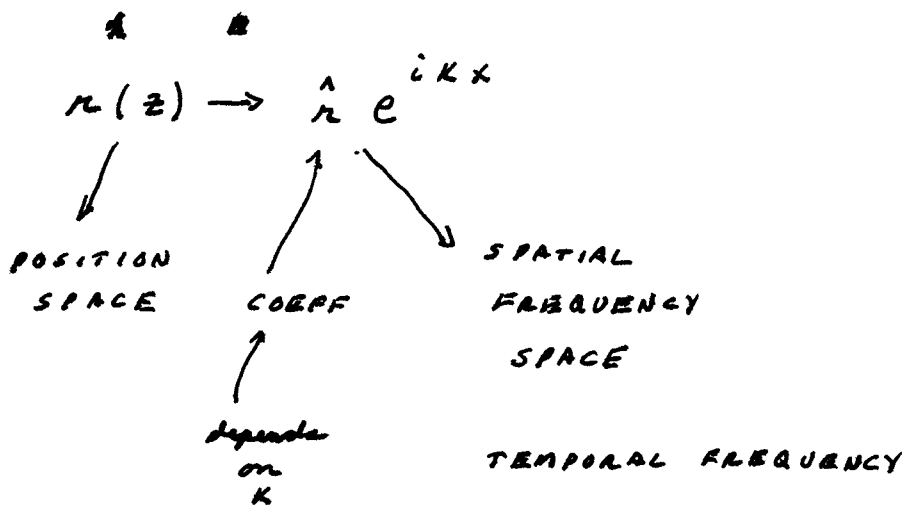

CAN DO EXACTLY THE SAME
 THING FOR SPACE



CAN ALSO DO BOTH

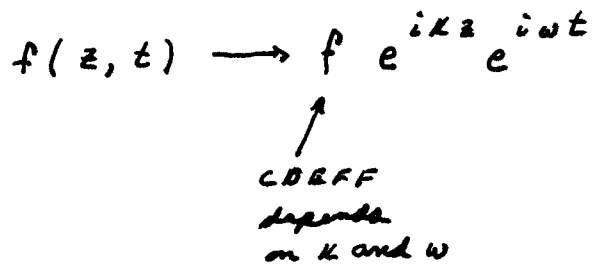

$$x \rightarrow \hat{x} e^{i\omega t}$$

CONVERTED $F = ma$ \Rightarrow ALGEBRAIC
DIFF EQN EQN

FOR THE STEADY STATE SOLUTIONS!

WE SAW YESTERDAY THAT THERE
ARE TRANSIENTS.

FEYNMAN I-24 SHOWS HOW TO DO TRANSIENTS

TODAY I WANT TO SHOW YOU HOW TO USE

$$v(t) \rightarrow \hat{v} e^{i\omega t} \text{ TO SOLVE STEADY STATE}$$

ELECTRICAL CIRCUITS

http://en.wikipedia.org/wiki/Harmonic_oscillator

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/accircon.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/watcir2.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/acohtml.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/imped.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/acres.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/accap.html#c2>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/acind.html#c2>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/accircon.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/phase.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/phase.html#c2>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/impcom.html#c1>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/phase.html#c3>

<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/accircon.html#c1>


<http://hyperphysics.phy-astr.gsu.edu/Hbase/electric/serres.html#c1>

Applets

http://qbx6.ltu.edu/s_schneider/physlets/main/rlc.shtml

<http://mysite.verizon.net/vzeoacw1/impedance.html>

IDEA:

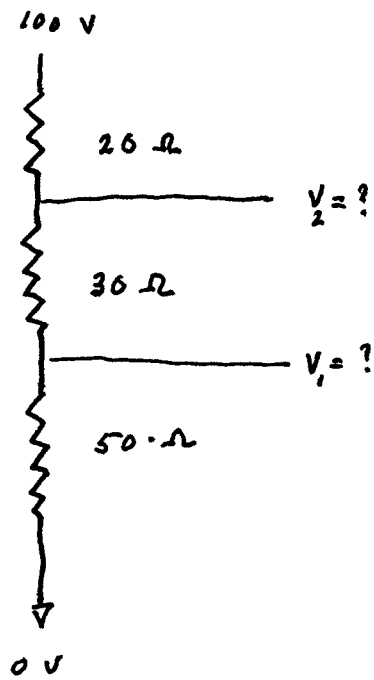

$$R_T = 50 + 30 + 20 = 100 \Omega$$

$$V_1 = \frac{50}{100} (100V) = 50V$$

$$V_2 = \frac{50 + 30}{100} (100V) = 80V$$

CALLED A RESISTIVE DIVIDER

GENERALIZE

RESISTIVE
DIVIDER

⇒

IMPEDANCE
DIVIDER

R

Z

resistance

impedance

$$V = i R$$

$$\hat{V} = \hat{I} Z$$

RESISTORS


RESISTORS

CAPACITORS

INDUCTORS

COMBINING COMPONENTS:


SERIES

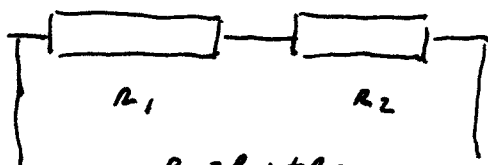

$$R_T = R_1 + R_2$$

$$Z_T = Z_1 + Z_2$$

PARALLEL

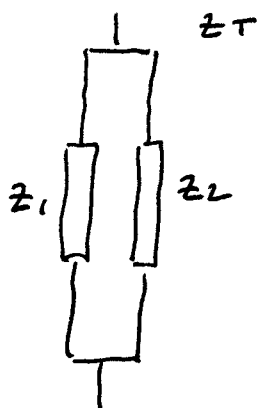


~~$Z_T = Z_1 + Z_2$~~

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\frac{1}{Z_T} = \frac{Z_2 + Z_1}{Z_1 Z_2}$$

$$Z_T = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

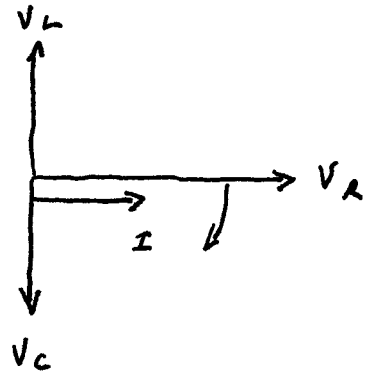

$$V = I R$$

$$V = I Z$$

$$Z_R = R$$


$$Z_L = i \omega L$$

$$Z_C = \frac{1}{i \omega C}$$


V_C LEADS I BY 90°

V_L LAGS I BY 90°

V_R SYNC W I

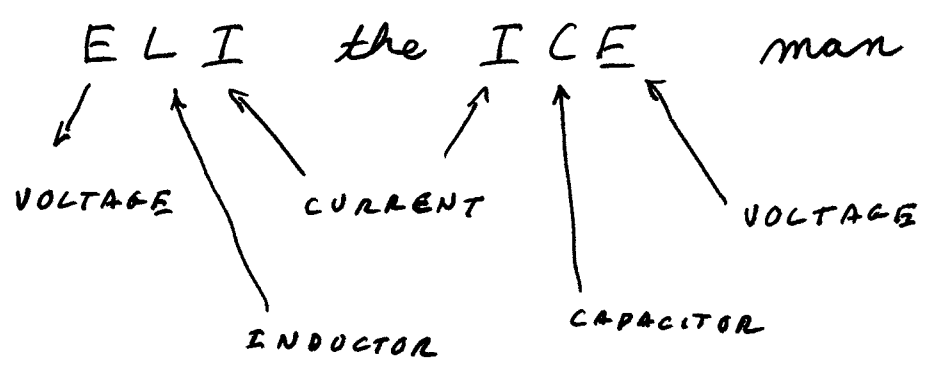

Z DIVIDER

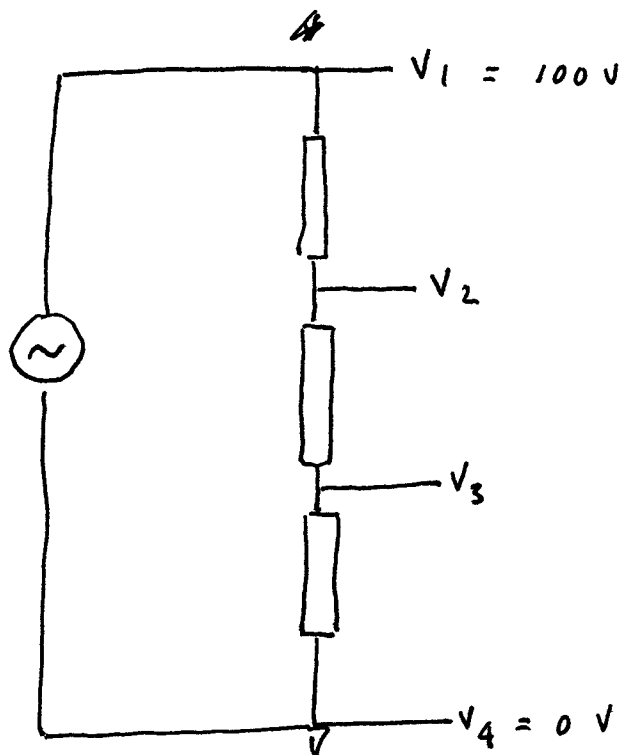

$$V = i R_T$$

$$R_T = R_1 + R_2 + R_3$$

$$V_3 = \frac{R_3}{R_T} V_0$$

$$i = \frac{V}{R_T}$$

$$V_2 = \frac{R_2 + R_3}{R_T} V_0$$

$$V = i Z_T$$



$$Z_T = Z_1 + Z_2 + Z_3$$

$$V_3 = \frac{Z_3}{Z_T} V_0$$

$$V_2 = \frac{Z_2 + Z_3}{Z_T} V_0$$

RESONANCE IN RLC CIRCUITS

SERIES

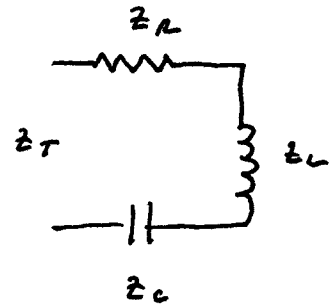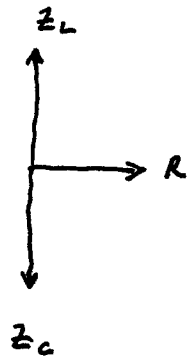

$$Z_L + Z_C = 0 \quad \text{CANCEL}$$

$$Z_T = R$$




MINIMUM IMPEDANCE AT RESONANCE

$$|Z_L| = |Z_C|$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

PARALLEL

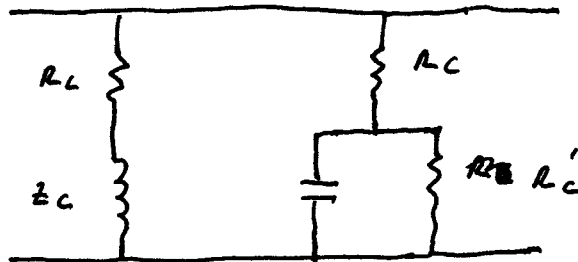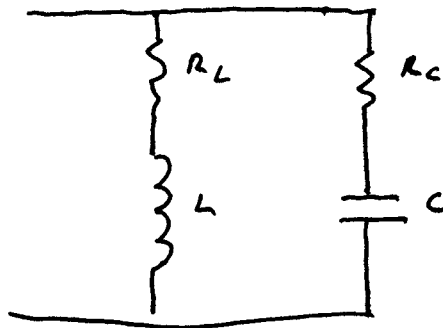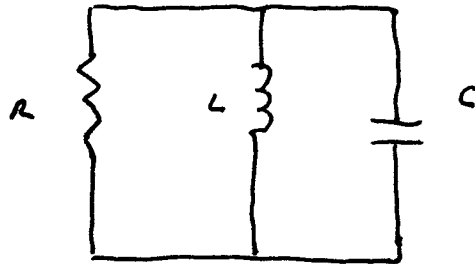

MAXIMUM IMPEDANCE AT RESONANCE

in limit as $R_L, R_C, R_C' \rightarrow 0$

$$\omega_0^2 = \frac{1}{LC}$$